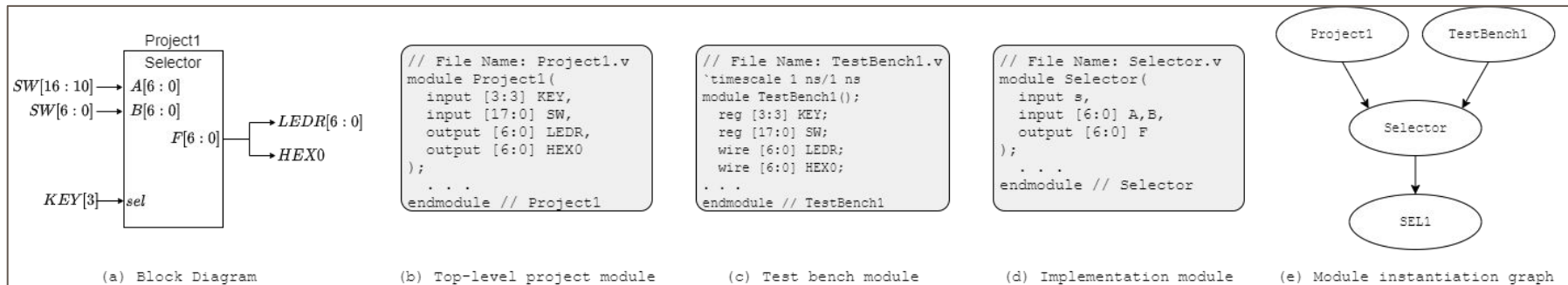


Bit Equality Checker Project

Design Specification


- Going to contain an overview/goal of what we want our project to do
- Will also contain many important diagrams
 - Block Diagram, Top-Level Project Module, Test Bench Module, Module Instantiation Graph
- Ex. Project 1 Design Specification Diagrams



Project 0.5 Design Specification: Goal


- We have 2 sets of switches
- We want to compare each respective switch of both sets
 - If the 2 switches match, we want its respective LED and HEX-bit to light up
 - Otherwise, we do not want the LED and HEX to light up

SW SET 1

 

0 1 0 1 0 1 0
1 1 1 1 0 0 0

LEDs

 



0 1 0 1 1 0 1

**HEX
Display**



Project 0.5 Design Specification: Block Diagram

- We have 2 sets of switches as INPUTS
 - SW [16:10] - Switches explicitly labelled on board {SW16, SW15, ..., SW11, SW10}
 - SW [6:0] - Switches explicitly labelled on board {SW6, SW5, ..., SW1, SW0}
- Outputs
 - LEDR[6:0] - Red LEDs {LEDR[6], ..., LEDR[0]}
 - HEX0 - One of the 7-Segment HEX Displays

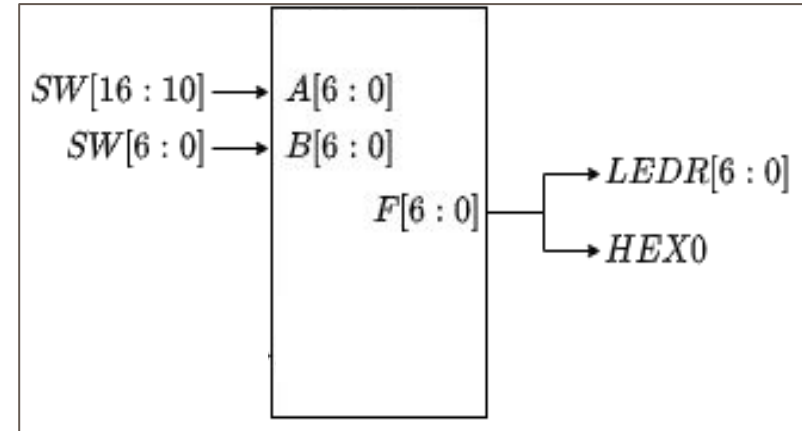 


Project 0.5 Design Specification: Top-Level Module

- Top-Level Module - Main entry point that interfaces w/ external components
 - Allows us to interact with the board's switches, buttons, HEX displays, LEDs, ...
- **MUST BE COPIED EXACTLY AS DEFINED IN THE SPEC**
 - Required for our Autograder to work properly

```
// Declaring a new module with name 'Project05'
module Project05(
    input [16:0] SW,      // Using {SW[16], ..., SW[1], SW[0]} as inputs
    output [6:0] LEDR,    // Using {LEDR[6], ..., LEDR[0]} as outputs
    output [6:0] HEX0     // Using {HEX0[6], ..., HEX[0]} as outputs
);
    // Module implementation
    ...
endmodule // Project 0.5
```

Verilog Modules (Structural)

 - Module - Task that is **INSTANTIATED**
 - Continuously running once instantiated
 - Resources (Logic Elements) allocated only once instantiated
 - IT IS NOT BEING CALLED UPON



```
// a, b are CONTINUOUSLY DRIVEN
// Similar as passing by reference
module updateC(
    input i_a,
    input i_b,
    output o_c
);

    // Continuous assignment
    and a1(o_c, i_a, i_b);
endmodule

module main(
    input [1:0] SW,    // Using SW 1 and 0 as input
    output [0:0] LEDR  // Using LEDR 0 as output
);

    // Internal wires
    wire a, b, c;

    // Assigning a and b CONTINUOUSLY
    buf b1(a, SW[0]);
    buf b1(b, SW[1]);

    // Assigning the output CONTINUOUSLY
    buf b3(LEDR[0], c);

    // Instantiating the updateC module
    // Need to give module some unique name
    updateC uc(.in_a(a), .in_b(b), .in_c(c));
endmodule
```

- REMEMBER:** Verilog is describing the behavior of our parallel system

Verilog Modules Ports (Ignoring Inouts)

- Inputs - Continuously driven by an outside element
 - You CANNOT reassign within the module
- Outputs - Needs to be driven by module
- Inouts - Can be used as input/output
 - Will not be using in 270

```
// a, b are CONTINUOUSLY DRIVEN
// Similar as passing by reference
module updateC(
    input i_a,
    input i_b,
    output o_c
);

    // ILLEGAL ASSIGNMENTS TO INPUTS
    not n1(i_a, 1'b0);
    not n1(i_b, 1'b1);

    // VALID Continuous assignmet
    and a1(o_c, i_a, i_b);
endmodule
```

NOTE: 2 Ways to Write Verilog Module Declarations

Legacy (Verilog-1995 Standard)

- Non-ANSI C Style
- Port declaration type outside list
- You might see this format in lab
 - Good to know that it exists

```
module updateC(i_a, i_b, o_c);  
  input i_a, i_b;  
  output o_c;  
  ...  
endmodule
```

Modern (Verilog-2001 Standard)

- ANSI C Style
- Cleaner to writer usually
 - Leads to less unusual bugs
- Less duplication

```
module updateC(  
  input i_a,  
  input i_b,  
  output o_c  
);  
  ...  
endmodule
```


Bit Vectors in Verilog (Structural)

- Bit Vectors - Multiple bits associated with the value
 - Allows for representation of multi-bit signal
 - By default, variables are 1-bit
- Representation
 - 'wire [most significant bit : least significant bit] name'
 - wire [3:0] a === {a[3], a[2], a[1], a[0]}
 - wire [0:4] b === {b[0], b[1], b[2], b[3], b[4]}
 - Bit range = Absolute value(msb - lsb) + 1

```
// Declaring a new module with name 'Project05'
module Project05(
    input [16:0] SW,      // Using {SW[16], ..., SW[1], SW[0]} as inputs
    output [6:0] LEDR,    // Using {LEDR[6], ..., LEDR[0]} as outputs
    output [6:0] HEX0     // Using {HEX0[6], ..., HEX[0]} as outputs
);
```


Project 0.5 Design Specification: Implementation Module(s)

- We may give you modules we want you to implement in a certain way
 - Sometimes we will test specific modules instead of the whole design
- Project 0.5 Checker Module
 - Inputs: 7-bit A, 7-bit B
 - Outputs: 7-bit F
 - Go through each bit of A and B
 - **If $A[i] == B[i]$, then $F[i] = 1$**
 - **Otherwise, if $A[i] != B[i]$, then $F[i] = 0$**

```
module Checker(  
    input [6:0] A, B,  
    output [6:0] F  
);  
    // Module implementation  
    ...  
endmodule // Checker
```

Project 0.5 Design Specification: Module Instantiation Graph

- Graph to help split up the work we need to accomplish for our design
- 'Project05' instantiates 'Checker'
- 'Checker' instantiates 'CHECK1'
- CHECK1 is a low-level helper function
 - Want to separate work as much as possible

 

Project 0.5: Giving Away CHECK1 Helper Function

- Project 0.5 CHECK1 Module
 - Inputs: 1-bit a, 1-bit b
 - Outputs: 1-bit f
 - Check 'a' and 'b' bit value
 - **If a == b, then f = 1**
 - **Otherwise, if a != b, then f = 0**

```
module CHECK1(  
    input a, b,  
    output f  
);  
    // Module implementation  
    ...  
endmodule // CHECK1
```

Start Small

(Building the CHECK1 Circuit)

Figuring Out CHECK1 Module (Step 1. Truth Table)

- Project 0.5 CHECK1 Module
 - If $a == b$, then $f = 1$
 - Otherwise, if $a != b$, then $f = 0$

a	b	f
----------	----------	----------

How many rows do we need for this truth table?

Figuring Out CHECK1 Module (Step 1. Truth Table)

- Project 0.5 CHECK1 Module
 - If $a == b$, then $f = 1$
 - Otherwise, if $a != b$, then $f = 0$
- # Rows = $2^{(\# \text{ Inputs})}$
 - 2 Inputs \rightarrow 4 Combinations / Rows

What are the inputs to this truth table?

a	b	f

Figuring Out CHECK1 Module (Step 1. Truth Table)

- Project 0.5 CHECK1 Module
 - If $a == b$, then $f = 1$
 - Otherwise, if $a != b$, then $f = 0$
- # Rows = $2^{(\# \text{ inputs})}$
 - 2 Inputs \rightarrow 4 Combinations / Rows

**What are the outputs
of this truth table?**

a	b	f
0	0	
0	1	
1	0	
1	1	

Figuring Out CHECK1 Module (Step 1. Truth Table)

- Project 0.5 CHECK1 Module
 - If $a == b$, then $f = 1$
 - Otherwise, if $a != b$, then $f = 0$
- # Rows = $2^{(\# \text{ inputs})}$
 - 2 Inputs \rightarrow 4 Combinations / Rows

a	b	f
0	0	1
0	1	0
1	0	0
1	1	1

Figuring Out CHECK1 Module (Step 2. Equation)

Now Build an Equation for 'f'

a	b	f
0	0	1
0	1	0
1	0	0
1	1	1

Figuring Out CHECK1 Module (Step 2. Equation)

1. Determine which rows resulted in 'f' being True (1)

a	b	f
0	0	1
0	1	0
1	0	0
1	1	1

Figuring Out CHECK1 Module (Step 2. Equation)

1. Determine which row resulted in 'f' being True (1)
2. Generate an Expression for Each Combination
 - a. Only that combination should result in output being true

For combination (0, 0) $\rightarrow a' \&\& b'$

The only time this expression is True is when (0, 0) is passed

For combination (1, 1) $\rightarrow a \&\& b$

The only time this expression is True is when (1, 1) is passed

a	b	f
0	0	1
0	1	0
1	0	0
1	1	1

Figuring Out CHECK1 Module (Step 2. Equation)

1. Determine which row resulted in 'f' being True (1)
2. Generate an Expression for Each Combination
 - a. Only that combination should result in output being true

For combination (0, 0) → $a' \&\& b'$

The only time this expression is True is when (0, 0) is passed

For combination (1, 1) → $a \&\& b$


The only time this expression is True is when (1, 1) is passed

3. OR each of the combinations

$$f = (a' \&\& b') \parallel (a \&\& b)$$


a	b	f
0	0	1
0	1	0
1	0	0
1	1	1

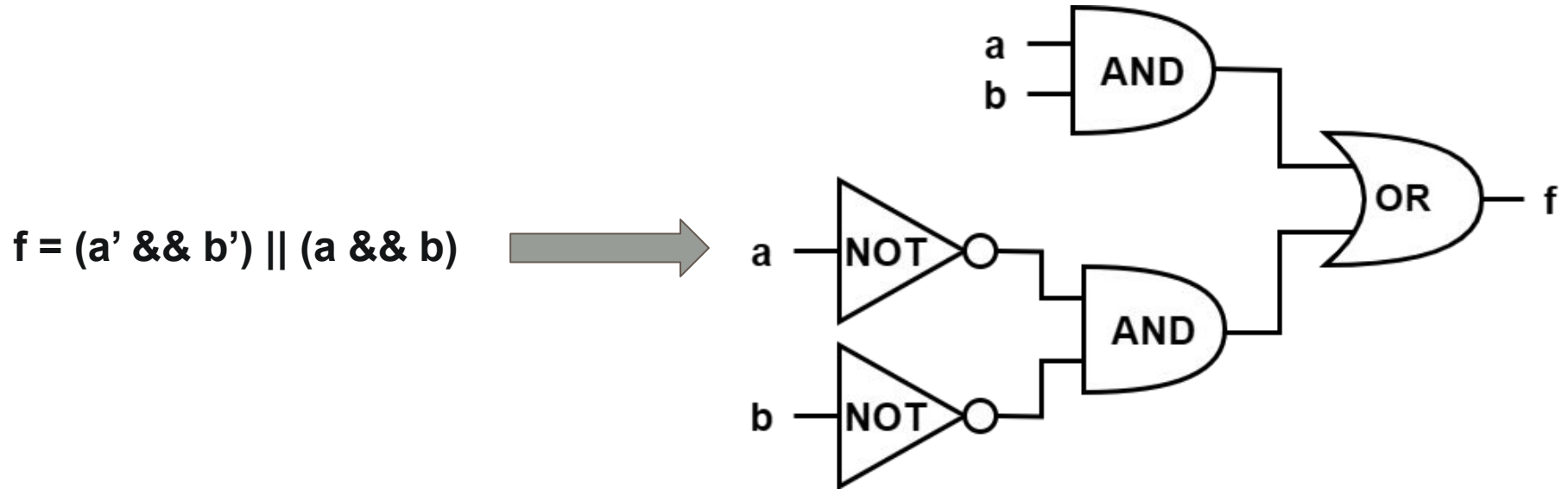Figuring Out CHECK1 Module (Step 3. Logic Gate Diagram)




Implementing Verilog

Overview of the Tools

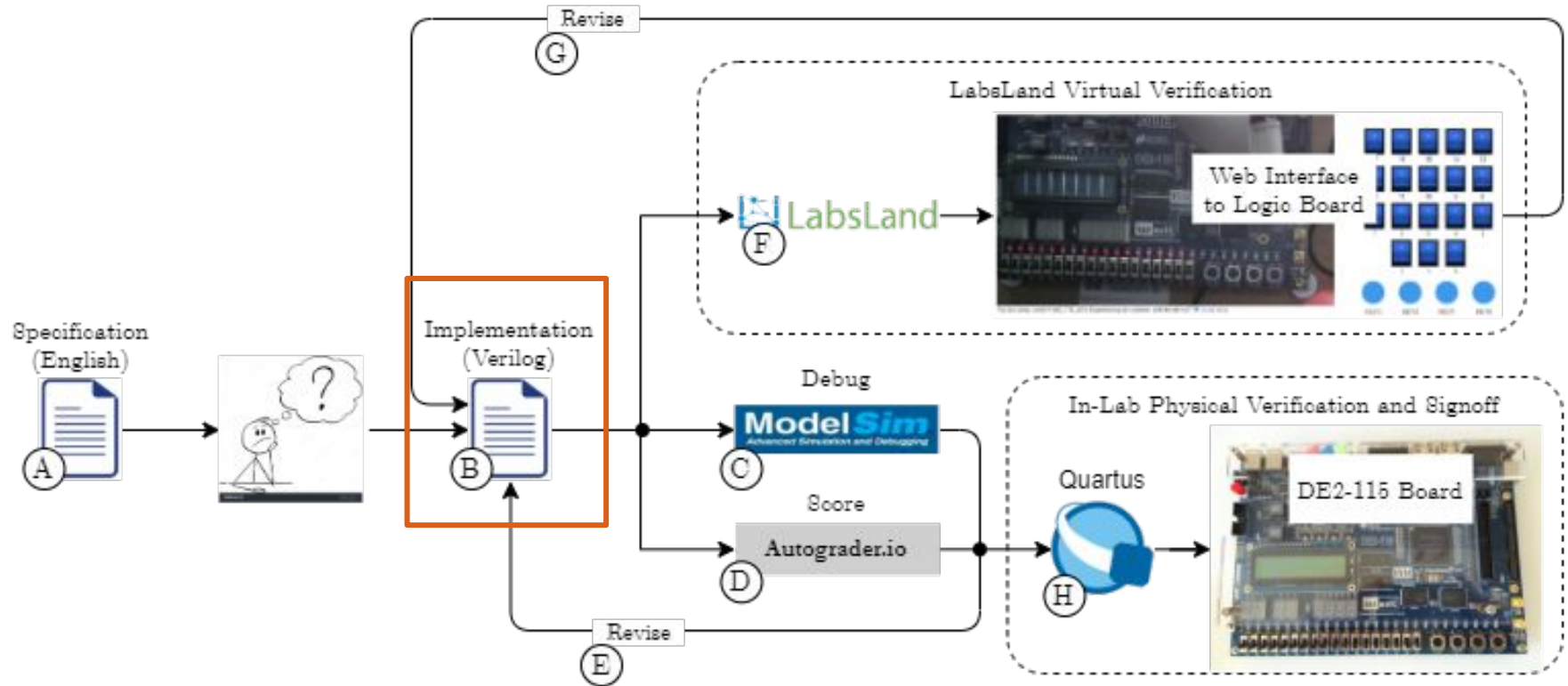

Text Editor Recommendation for Verilog Coding

 - Can use whatever you want to write Verilog
 - I've seen notepad, notepad++, Quartus Prime, ... used as text editors
- My Recommendation - Use **VS Code**
 - Use Intellisense Extension below





- Please please please don't use ModelSim as a text editor
 - It has led to many issues

Implementing Verilog (Implementing the CHECK1 Module)


Verilog Wire Data Type

- Wire - Used to model physical connections between components in digital circuits
 - **They do not store values**
 - **They are continuously driven (assigned)**
 - The value is continuously determined by the entity driving the net
 - **If nothing is driving it, it holds no value (Undefined 'Z')**
- **Wire** - The only Net data type we will be using in class
 - Can be thought of as actual physical wires

  

NOTE: Inputs and Outputs
are implicitly declared as
wires already

Determining Circuit Wires

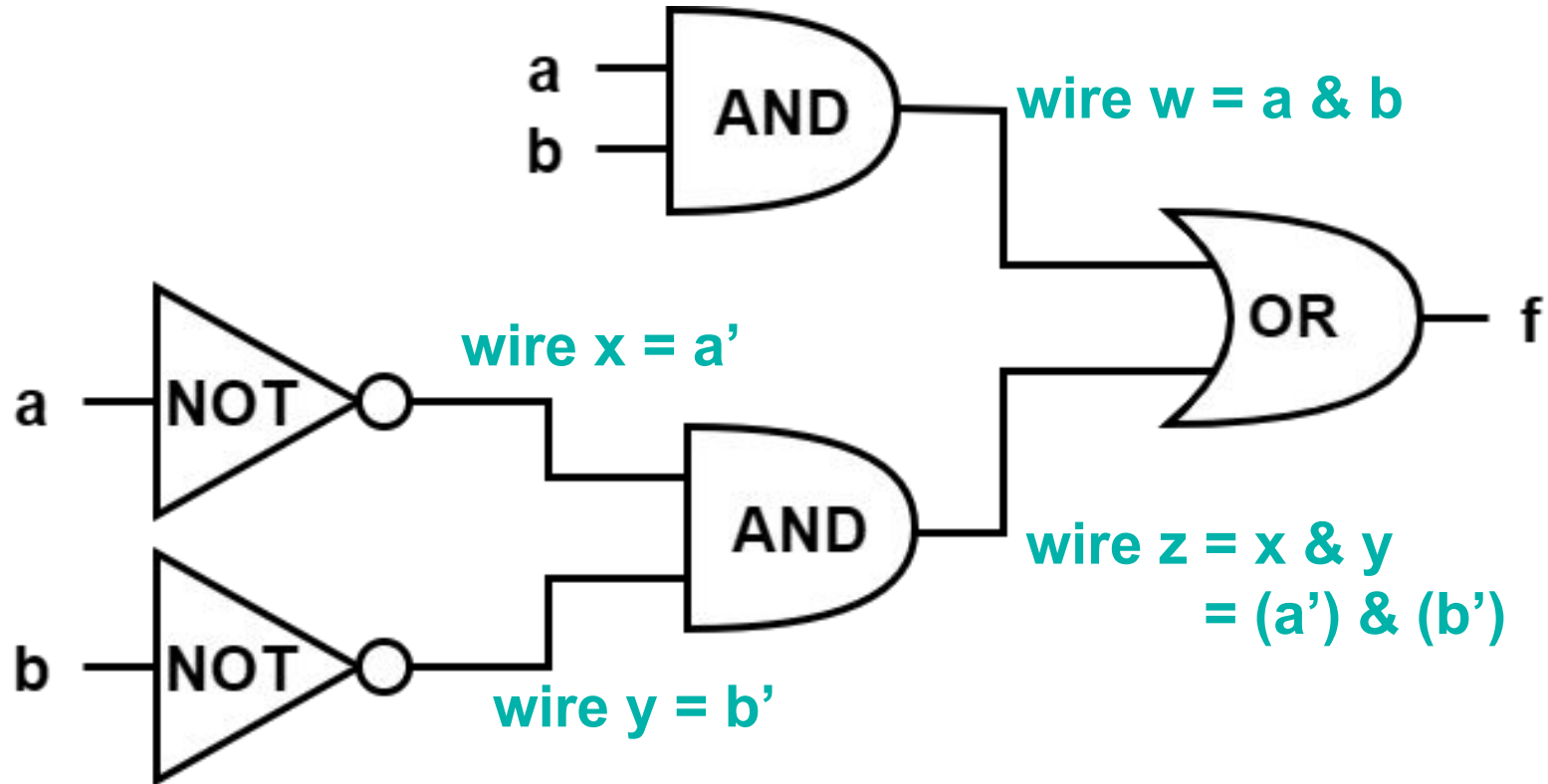

Verilog's Many Levels of Abstraction

**“BEHAVIORAL
VERILOG”**

Behavioral Level

Project 3B - 7

Dataflow Level

**“STRUCTURAL
VERILOG”**

Gate Level

Projects 0 - 3A

Switch Level




Will Discuss Later

USE STRUCTURAL VERILOG FOR Projects 0-3A!!!

- **You SHOULD NOT be using**
 - Continuous 'assign' statements
 - Procedural statements 'always' or 'initial'
- These abstractural statements are used in "Behavioral" Verilog
 - Will be using in Projects 3B - 7
- **You SHOULD ONLY be using**
 - Primitive gate instantiations as described in [this slide](#)
 - Module instantiations as described in [this slide](#)

Structural Verilog (Gate Level Modeling)

   - One of the lowest levels of Verilog abstraction!
- Describing your circuit with primitive gates
 - Creating a one-to-one mapping between logic circuit diagram \longleftrightarrow Verilog Description



```
wire OUT, IN1, IN2;
```

```
// basic gate instantiations.  
and a1(OUT, IN1, IN2);  
nand na1(OUT, IN1, IN2);  
or or1(OUT, IN1, IN2);
```


<gate type> <instance name>(<output name> <input list>)

Implementation in Verilog (Declaring Wires)

```
module CHECK1(  
    input a, b,  
    output f  
);
```

```
    // Step 1. Declare Your Wires  
    ...
```


```
endmodule // CHECK1
```

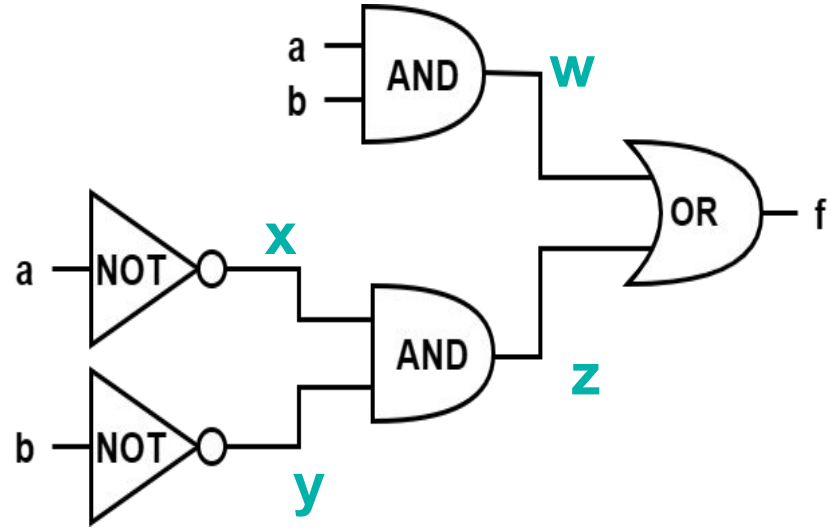

```
wire OUT, IN1, IN2;
```


Implementation in Verilog (Instantiating Gates)

 
```
module CHECK1(  
    input a, b,  
    output f  
);  
  
    // Step 1. Declare Your Wires  
    // Declaring 1-bit wires w, x, y, z  
    wire w, x, y, z;  
  
    // Step 2. Instantiate the gates  
    ...  
  
endmodule // CHECK1
```



```
// basic gate instantiations.  
and al(OUT, IN1, IN2);  
nand na1(OUT, IN1, IN2);  
or or1(OUT, IN1, IN2);
```

Implementation in Verilog (DONE!!!)
 
```
module CHECK1(  
    input a, b,  
    output f  
);  
  
    // Step 1. Declare Your Wires  
    // Declaring 1-bit wires w, x, y, z  
    wire w, x, y, z;  
  
    // Step 2. Instantiate the gates  
    and a1(w, a, b);  
    not n1(x, a);  
    not n2(y, b);  
    and a2(z, x, y);  
    or o1(f, w, z);  
  
endmodule // CHECK1
```



Implementing Verilog (Implementing the Checker Module)

Checker Module (Overview)

- Inputs: 7-bit A, 7-bit B
- Outputs: 7-bit F
- Go through each bit of A and B
- **If $A[i] == B[i]$, then $F[i] = 1$**
- **Otherwise, if $A[i] != B[i]$, then $F[i] = 0$**


```
module Checker(  
    input [6:0] A, B,  
    output [6:0] F  
);  
    // Module implementation  
    ...  
endmodule // Checker
```

**How can we use CHECK1 to
implement the Checker module?**

Checker Module (Building the Logical Circuit)

- If $A[i] == B[i]$, then $F[i] = 1$
- Otherwise, if $A[i] != B[i]$, then $F[i] = 0$

 **Build the Checker logical circuit
using CHECK1**










```
module Checker(  
    input [6:0] A, B,  
    output [6:0] F  
);  
    // Module implementation  
    ...  
endmodule // Checker
```

Checker Module (Building the Logical Circuit)

- If $A[i] == B[i]$, then $F[i] = 1$
- Otherwise, if $A[i] != B[i]$, then $F[i] = 0$
- 7 Instances of CHECK1
- Each checking on their own bit pair

Now Implement Checker in Verilog!


```
CHECK1 c0(A[0], B[0], F[0]);
```

       

Checker Module (almost DONE!!)

- If $A[i] == B[i]$, then $F[i] = 1$
- Otherwise, if $A[i] != B[i]$, then $F[i] = 0$

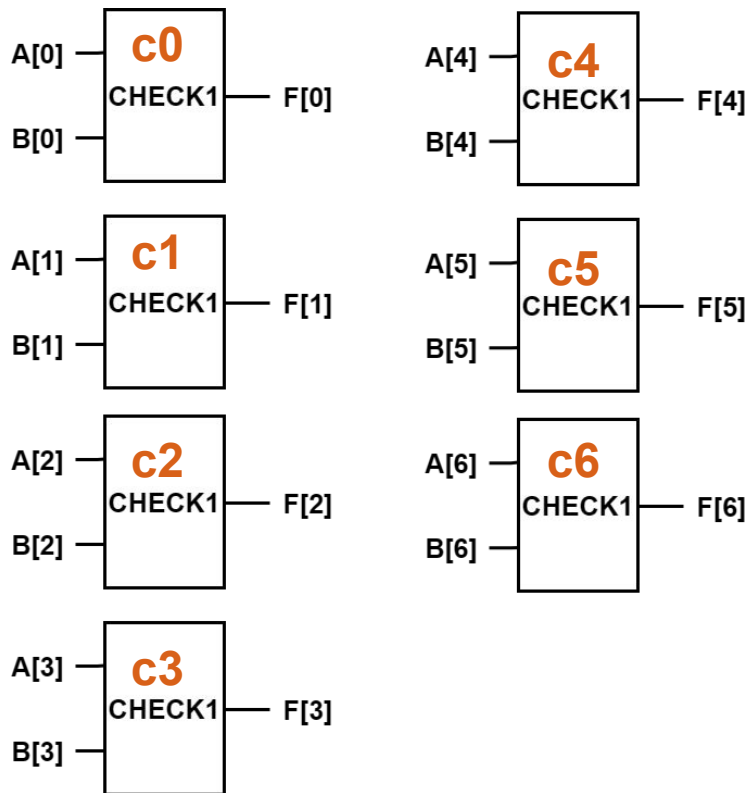
```
module Checker(  
    input [6:0] A, B,  
    output [6:0] F  
);  
  
    // Instantiate CHECK1 module for each bit pair  
    CHECK1 c0(A[0], B[0], F[0]);  
    CHECK1 c1(A[1], B[1], F[1]);  
    CHECK1 c2(A[2], B[2], F[2]);  
    CHECK1 c3(A[3], B[3], F[3]);  
    CHECK1 c4(A[4], B[4], F[4]);  
    CHECK1 c5(A[5], B[5], F[5]);  
    CHECK1 c6(A[6], B[6], F[6]);  
  
endmodule // Checker
```



Checker Module (Shortcut Implementation with Array)

- Can create an array of instantiations!
- Shortcut implementation of previous
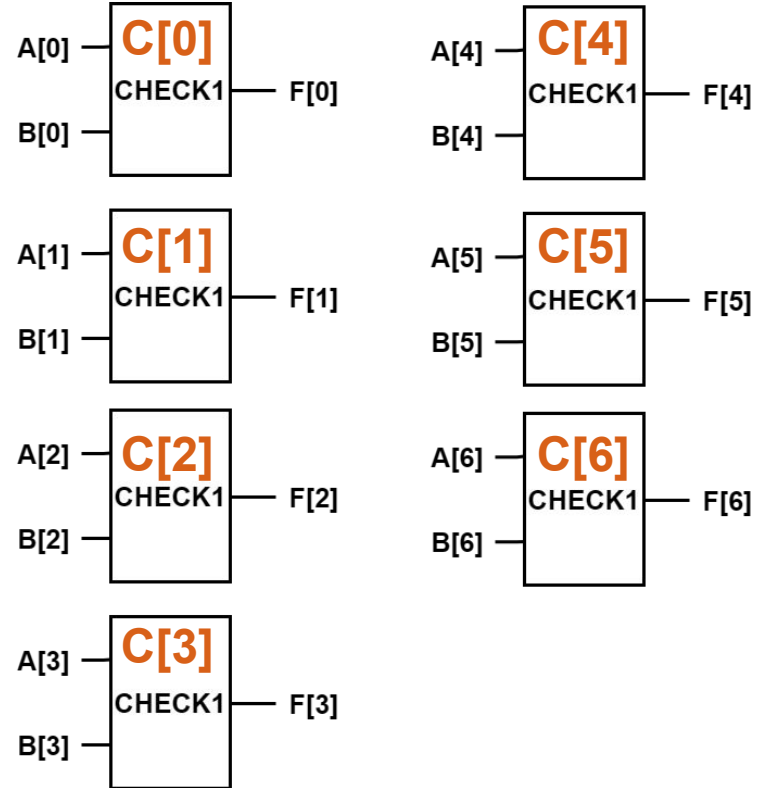
```
module Checker(  
    input [6:0] A, B,  
    output [6:0] F  
);  
  
    // Instantiate CHECK1 module for each bit pair  
    CHECK1 C[6:0](A, B, F);  
  
endmodule // Checker
```



Implementing Verilog (Implementing the Top-Level Module)

Project 0.5 Design Specification: Top-Level Module

- Top-Level Module - Main entry point that interfaces w/ external components
 - Allows us to interact with the board's switches, buttons, HEX displays, LEDs, ...
- **MUST BE COPIED EXACTLY AS DEFINED IN THE SPEC**
 - Required for our Autograder to work properly

```
// Declaring a new module with name 'Project05'
module Project05(
    input [16:0] SW,      // Using {SW[16], ..., SW[1], SW[0]} as inputs
    output [6:0] LEDR,   // Using {LEDR[6], ..., LEDR[0]} as outputs
    output [6:0] HEX0    // Using {HEX0[6], ..., HEX[0]} as outputs
);
    // Module implementation
    ...
endmodule // Project 0.5
```

Goal of Project05 Top-Level Module

- Handle the incoming Switch inputs values
- Instantiate Checker module to handle computation
- Drive HEX0 and LEDR outputs

```
// Declaring a new module with name 'Project05'
module Project05(
    input [16:0] SW,      // Using {SW[16], ..., SW[1], SW[0]} as inputs
    output [6:0] LEDR,    // Using {LEDR[6], ..., LEDR[0]} as outputs
    output [6:0] HEX0     // Using {HEX0[6], ..., HEX[0]} as outputs
);
    // Module implementation
    ...
endmodule // Project 0.5
```

Active Low vs. Active High

- Active High - ON = 1 and OFF = 0
- Active Low - ON = 0 and OFF = 1

FOR PUSH-BUTTONS (ACTIVE LOW)



Unpressed
Logical High (1)



Pressed
Logical Low (0)

Component	Standard Name	Active High/Low
Slider Switches	SW[17:0]	High
Push-Button Keys	KEY[3:0]	Low
Red LEDs	LEDR[17:0]	High
Green LEDs	LEDG[8:0]	High
HEX Displays	HEX7[6:0], . . . ,HEX0[6:0]	Low
50 MHz Clock	CLOCK_50	N/A

Active Low vs. Active High

For Switches / LED (ACTIVE HIGH)



Switch / LED Off
Logical Low (0)



Switch / LED On
Logical High (1)



For HEX Displays (ACTIVE LOW)




Segment On
Logical Low (0)



Segment Off
Logical High (1)


Component	Standard Name	Active High/Low
Slider Switches	SW[17:0]	High
Push-Button Keys	KEY[3:0]	Low
Red LEDs	LEDR[17:0]	High
Green LEDs	LEDG[8:0]	High
HEX Displays	HEX7[6:0], . . . ,HEX0[6:0]	Low
50 MHz Clock	CLOCK_50	N/A

Project05 Logical Gate Diagram

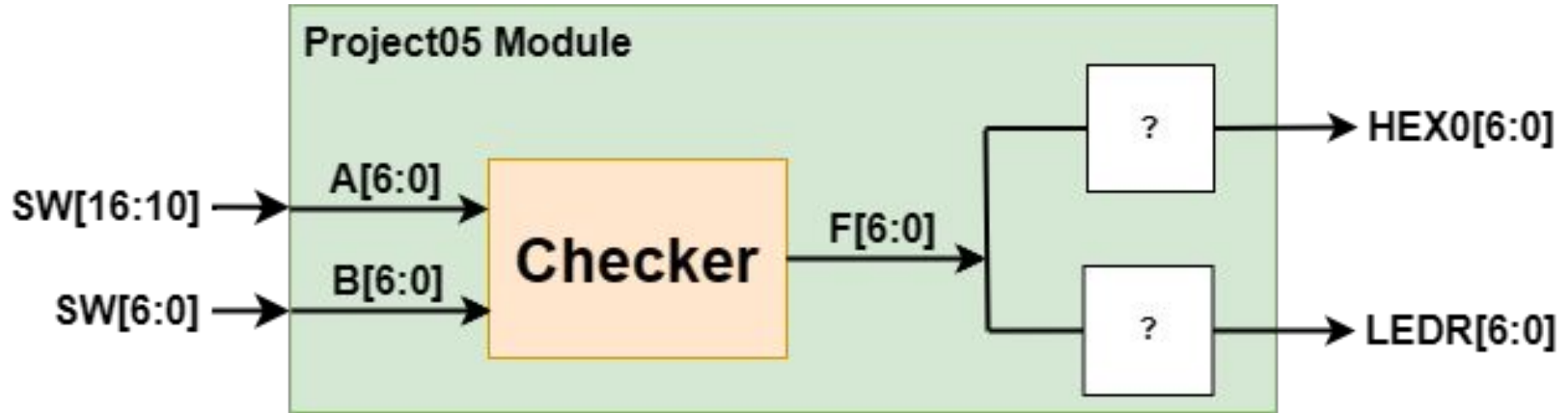

**What logical gate should we connect
each of the outputs from F?
HINT: They won't be the same**

Project05 Logical Gate Diagram

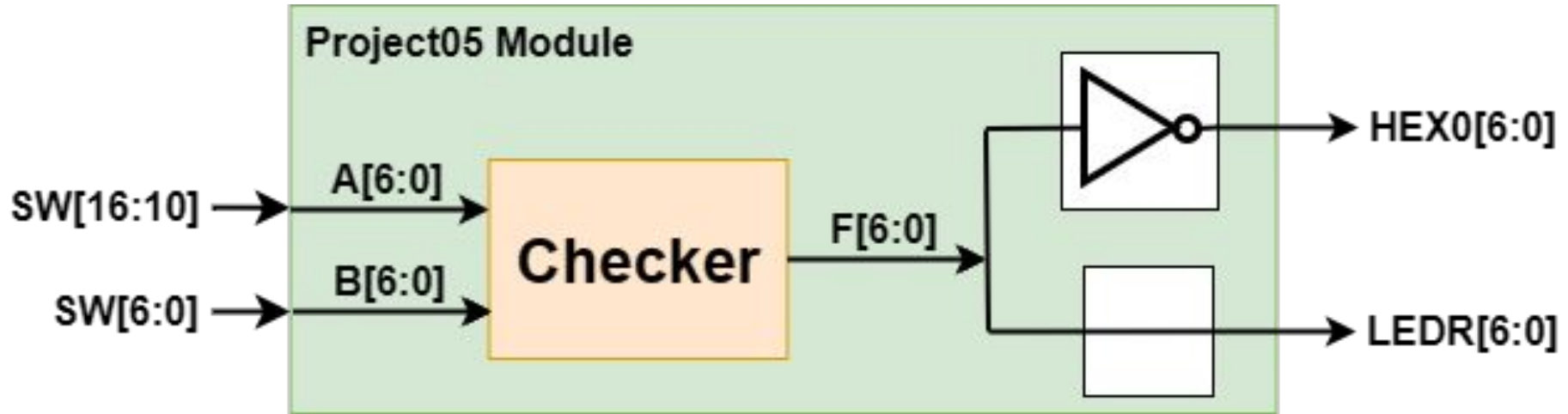

What are the internal wires of the Project05 Module?

Implementing Project05 Module

```
module Project05(  
    input [16:0] SW,      // Using {SW[16], ..., SW[1], SW[0]} as inputs  
    output [6:0] LEDR,    // Using {LEDR[6], ..., LEDR[0]} as outputs  
    output [6:0] HEX0     // Using {HEX0[6], ..., HEX[0]} as outputs  
);  
  
    // Step 1. ???  
    ...  
  
endmodule // Project 0.5
```


Implementing Project05 Module

```
module Project05(  
    input [16:0] SW,      // Using {SW[16], ..., SW[1], SW[0]} as inputs  
    output [6:0] LEDR,    // Using {LEDR[6], ..., LEDR[0]} as outputs  
    output [6:0] HEX0     // Using {HEX0[6], ..., HEX[0]} as outputs  
);  
  
    // Step 1. Declare your internal wires  
    ...  
  
endmodule // Project 0.5
```


Implementing Project05 Module

```
module Project05(  
    input [16:0] SW,      // Using {SW[16], ..., SW[1], SW[0]} as inputs  
    output [6:0] LEDR,    // Using {LEDR[6], ..., LEDR[0]} as outputs  
    output [6:0] HEX0     // Using {HEX0[6], ..., HEX[0]} as outputs  
);  
  
    // Step 1. Declare your internal wires  
    wire [6:0] A, B, F;  
  
    // Step 2. ???  
    ...  
  
endmodule // Project 0.5
```

Implementing Project05 Module

```
module Project05(  
    input [16:0] SW,      // Using {SW[16], ..., SW[1], SW[0]} as inputs  
    output [6:0] LEDR,    // Using {LEDR[6], ..., LEDR[0]} as outputs  
    output [6:0] HEX0     // Using {HEX0[6], ..., HEX[0]} as outputs  
);  
  
    // Step 1. Declare your internal wires  
    wire [6:0] A, B, F;  
  
    // Step 2. Assign internal wires A and B to the inputs  
    ...  
  
endmodule // Project 0.5
```

Buffer (Pass-Through) Logical Gate

 

A	OUT
0	0
1	1

Pass-Through Operator

```
module Project05(  
    input [16:0] SW,    // Using {SW[16], ..., SW[1], SW[0]} as inputs  
    output [6:0] LEDR,  // Using {LEDR[6], ..., LEDR[0]} as outputs  
    output [6:0] HEX0   // Using {HEX0[6], ..., HEX[0]} as outputs  
);  
  
    // Step 1. Declare your internal wires  
    wire [6:0] A, B, F;  
  
    // Step 2. Assign internal wires A and B to the inputs  
    // Instantiating 2 buffer arrays, each with 7 buffers  
    // Each array will give the value of Switches directly to A and B  
    buf b0[6:0](A, SW[16:10]);  
    buf b1[6:0](B, SW[6:0]);  
  
endmodule // Project 0.5
```



Implementing Project05 Module (Finished)

```
module Project05(  
    input [16:0] SW,      // Using {SW[16], ..., SW[1], SW[0]} as inputs  
    output [6:0] LEDR,    // Using {LEDR[6], ..., LEDR[0]} as outputs  
    output [6:0] HEX0     // Using {HEX0[6], ..., HEX[0]} as outputs  
);  
  
    // Step 1. Declare your internal wires  
    wire [6:0] A, B, F;  
  
    // Step 2. Assign internal wires A and B to the inputs  
    // Instantiating 2 buffer arrays, each with 7 buffers  
    // Each array will give the value of Switches directly to A and B  
    buf b0[6:0](A, SW[16:10]);  
    buf b1[6:0](B, SW[6:0]);  
  
    // Step 3. Instantiating Checker module  
    // Passing A, B as inputs and F as output  
    Checker c(A, B, F);  
  
    // Step 4. Pass F to Outputs  
    buf b2[6:0](LEDR[6:0], F);  
    not n1[6:0](HEX0[6:0], F);  
  
endmodule // Project 0.5
```

Final Verilog


```
module Project05(  
    input [16:0] SW,      // Using {SW[16], ..., SW[1], SW[0]} as inputs  
    output [6:0] LEDR,    // Using {LEDR[6], ..., LEDR[0]} as outputs  
    output [6:0] HEX0     // Using {HEX0[6], ..., HEX0[0]} as outputs  
);  
  
    // Step 1. Declare your internal wires  
    wire [6:0] A, B, F;  
  
    // Step 2. Assign internal wires A and B to the inputs  
    // Instantiating 2 buffer arrays, each with 7 buffers  
    // Each array will give the value of Switches directly to A and B  
    buf b0[6:0](A, SW[16:10]);  
    buf b1[6:0](B, SW[6:0]);  
  
    // Step 3. Instantiating Checker module  
    // Passing A, B as inputs and F as output  
    Checker c(A, B, F);  
  
    // Step 4. Pass F to Outputs  
    buf b2[6:0](LEDR[6:0], F);  
    not n1[6:0](HEX0[6:0], F);  
  
endmodule // Project 0.5
```

```
module CHECK1(  
    input a, b,  
    output f  
);  
  
    // Step 1. Declare Your Wires  
    // Declaring 1-bit wires w, x, y, z  
    wire w, x, y, z;  
  
    // Step 2. Instantiate the gates  
    and a1(w, a, b);  
    not n1(x, a);  
    not n2(y, b);  
    and a2(z, x, y);  
    or o1(f, w, z);  
  
endmodule // CHECK1
```

```
module Checker(  
    input [6:0] A, B,  
    output [6:0] F  
);  
  
    // Instantiate CHECK1 module for each bit pair  
    CHECK1 C[6:0](A, B, F);  
  
endmodule // Checker
```

Let's Try It Out (LabsLand)

Overview of the Tools

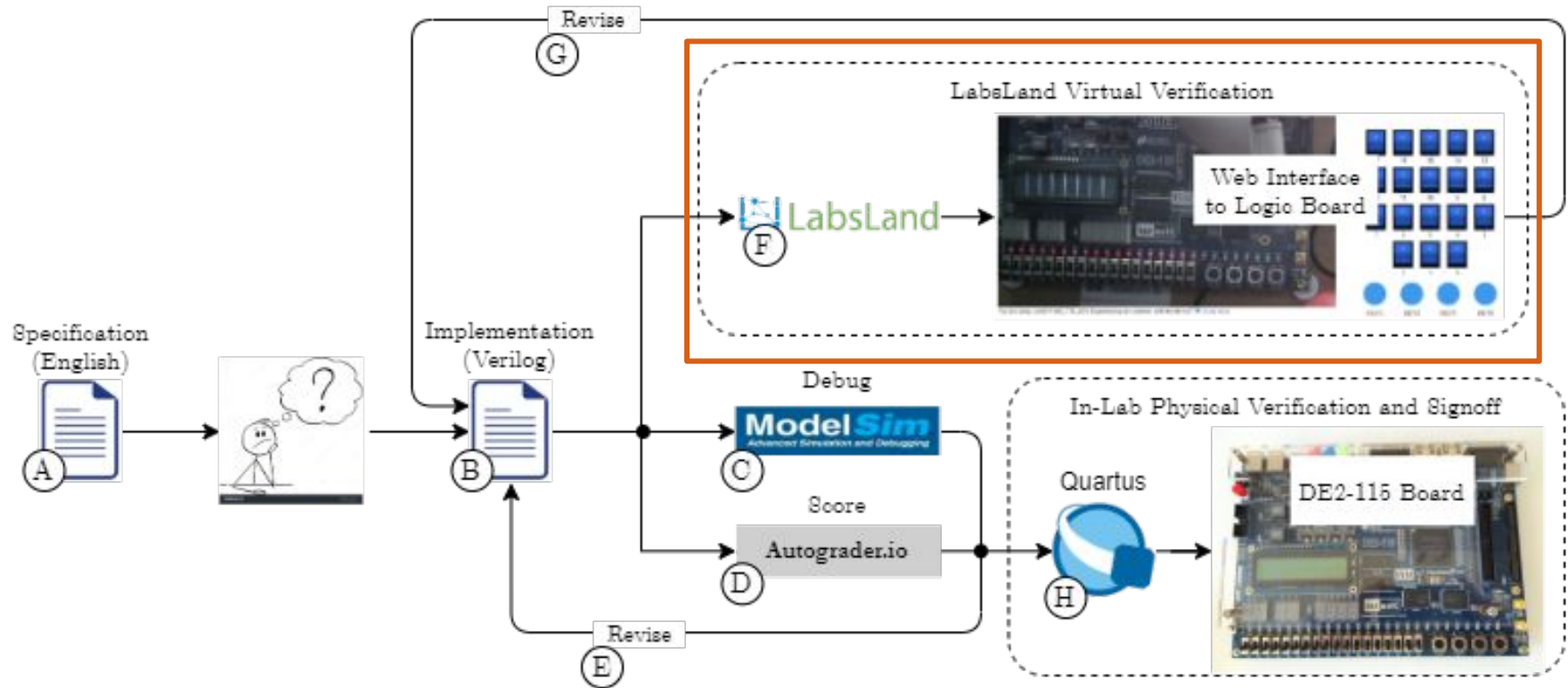

LabsLand - Virtually Connection to the Boards

[Link to LabsLand Site](#)

- Ability to connect to an FPGA board virtually!
 1. Create a new account (Possibly)
 2. Access the DE2-115 IDE Verilog Option (Not VHDL)
- WARNING: There is a per day capacity on how many times you can flash onto the board (Not sure how many times)

Textual Solution to Project 0.5 (For Copy-Paste)


```
module Project05(  
    input [16:0] SW, // Using {SW[16], ..., SW[1], SW[0]} as inputs  
    output [6:0] LEDR, // Using {LEDR[6], ..., LEDR[0]} as outputs  
    output [6:0] HEX0 // Using {HEX0[6], ..., HEX0[0]} as outputs  
);  
  
// Step 1. Declare your internal wires  
wire [6:0] A, B, F;  
  
// Step 2. Assign internal wires A and B to the inputs  
// Instantiating 2 buffer arrays, each with 7 buffers  
// Each array will give the value of Switches directly to A and B  
buf b0[6:0](A, SW[16:10]);  
buf b1[6:0](B, SW[6:0]);  
  
// Step 3. Instantiating Checker module  
// Passing A, B as inputs and F as output  
Checker c(A, B, F);  
  
// Step 4. Pass F to Outputs  
buf b2[6:0](LEDR[6:0], F);  
not n1[6:0](HEX0[6:0], F);  
  
endmodule // Project 0.5
```

```
module Checker(  
    input [6:0] A, B,  
    output [6:0] F  
);  
  
// Instantiate CHECK1 module for each bit pair  
CHECK1 C[6:0](A, B, F);  
  
endmodule // Checker
```

```
module CHECK1(  
    input a, b,  
    output f  
);  
  
// Step 1. Declare Your Wires  
// Declaring 1-bit wires w, x, y, z  
wire w, x, y, z;  
  
// Step 2. Instantiate the gates  
and a1(w, a, b);  
not n1(x, a);  
not n2(y, b);  
and a2(z, x, y);  
or o1(f, w, z);  
  
endmodule // CHECK1
```


Let's Simulate (ModelSim)

Overview of the Tools

 

ModelSim - Debugging and Simulating Testbenches

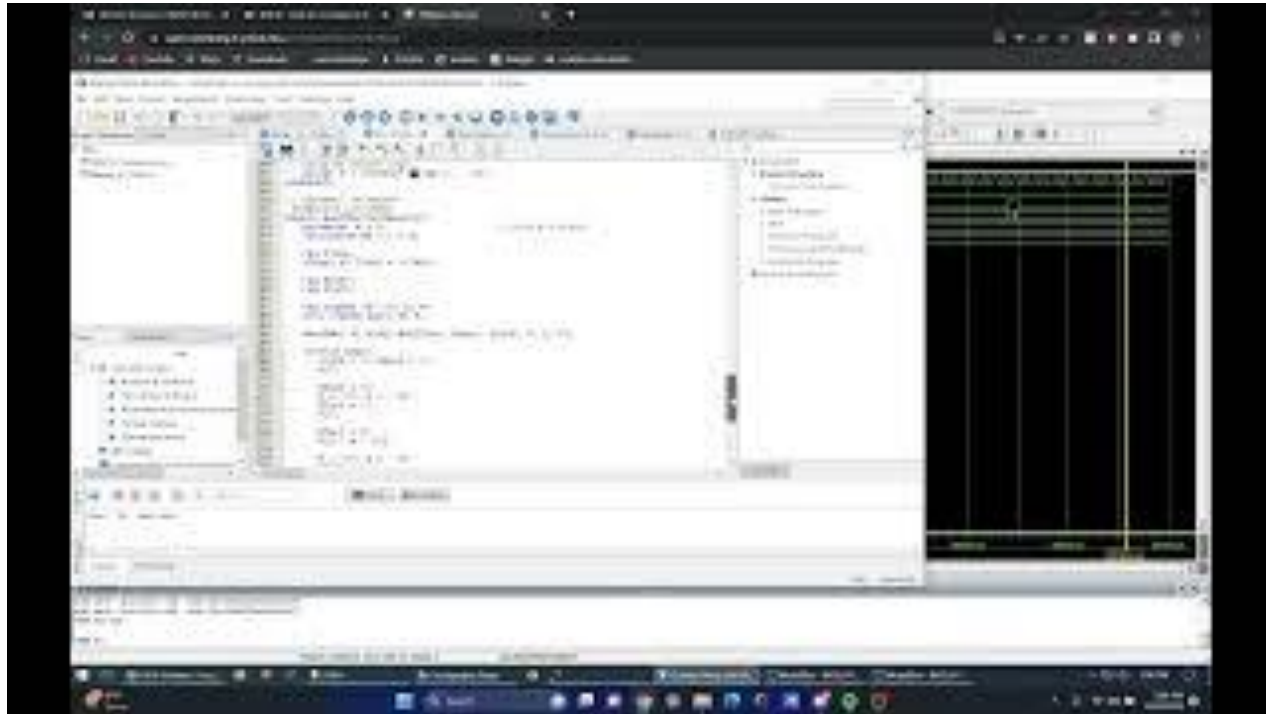- Great ModelSim tutorial created by previous GSI Ryan!



General Structure of a Testbench (Overview)

```
// Timescale on the top
// `timescale <time_unit>/<time_precision>
// My preference, use 1ns/1ns
`timescale 1ns/1ns

// Testbench module has no inputs/outputs
module Testbench;

    // All controllable inputs to DUT declared as reg
    reg [6:0] A, B;

    // All outputs of DUT declared as wire
    wire [6:0] F;

    // Instantiate module we want to test
    // DUT - Device Under Testing
    Checker dut(A, B, F);

    // Initial statement use to control inputs
    // Initial means right at t = 0
    initial begin

        // Controlling input here

    end // initial
endmodule // Testbench
```

```
// Initial statement use to control inputs
// Initial means right at t = 0
initial begin

    // assign A and B to some value at t=0
    A = 7'b0000000;
    B = 7'b0000000;

    // Wait statement
    // Waiting 5 time units --> 5 ns
    #5;

    A[1] = 1'b0;

    #5;

    B[3] = 1'b0;

    #5;

    A[1] = 1'b1;
    A[3] = 1'b0;

end // initial
```

Number Specification in Verilog

- You can specify sized number in Verilog through {size}'{base format}{number}
 - Size - Number of bits associated with the number
 - Base Format - Can be decimal (D or d), Binary (B or b), Hex (H or h), Octal (O or o)
 - Number - Number specified in the provided base format

Ex. 4'b1001 → **4-bit** number with **binary** value **1001** (9 in decimal)

Ex. 5'd13 → **5-bit** number with **decimal** value **13** (**01101** in binary)

Ex. 8'hAA → **8-bit** number with **hex** value **AA** (**1010_1010** in binary)

- Valid to use underscores anywhere for readability → 12'b0110_1001_0011
- Valid to leave number unsized (**BUT NOT ADVISED**) → 'b1001, 'd32
- If no size or base format specified, default is decimal → 123

Textual Testbench for Project 0.5

```
// Timescale on the top
// `timescale <time_unit>/<time_precision>
// My preference, use 1ns/1ns
`timescale 1ns/1ns

// Testbench module has no inputs/outputs
module Testbench;

    // All controlable inputs to DUT declared as reg
    reg [6:0] A, B;

    // All outputs of DUT declared as wire
    wire [6:0] F;

    // Instantiate module we want to test
    // DUT - Device Under Testing
    Checker dut(A, B, F);

    // Initial statement use to control inputs
    // Initial means right at t = 0
    initial begin

        // assign A and B to some value at t=0
        A = 7'b1111111;
        B = 7'b1111111;

        // Wait statement
        // Waiting 5 time units --> 5 ns
        #5;

        A[1] = 1'b0;

        #5;

        B[3] = 1'b0;

        #5;

        A[1] = 1'b1;
        A[3] = 1'b0;

    end // initial

endmodule // Testbench
```