

# Minority Combinational Project


# Capture, Create, Implement Process (Recap)

1. **Capture** the behavior of the function
  - a. Either through a truth table or equation (Whichever is easier)
2. **Create** equations (If you haven't already)
  - a. Canonical Sums-of-Products
3. **Implement** a gate-based circuit for each output
  - a. Can then translate that gate directly into Verilog
 
# Minority Function Implementation

- **Minority Function**

- Inputs: 3 1-bit inputs (A, B, C)
- Outputs: 1-bit output (F)
- **F will go high if there are one or fewer logical high across the 3 inputs**



# Capture the Function Behavior (Truth Table)

A	B	C	F
---	---	---	---

- **Minority Function**
  - Inputs: 3 1-bit inputs (A, B, C)
  - Outputs: 1-bit output (F)
  - **F will go high if there are one or fewer logical high across the 3 inputs**

# Capture the Function Behavior (Truth Table)

- **Minority Function**
  - Inputs: 3 1-bit inputs (A, B, C)
  - Outputs: 1-bit output (F)
  - **F will go high if there are one or fewer logical high across the 3 inputs**

A	B	C	F

# Capture the Function Behavior (Truth Table)

- **Minority Function**
  - Inputs: 3 1-bit inputs (A, B, C)
  - Outputs: 1-bit output (F)
  - **F will go high if there are one or fewer logical high across the 3 inputs**

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

# Create Your Equation(s)

The 3-step process produces a Canonical SOP!!

1. Determine which rows resulted in 'F' being True (1)
2. Generate an minterm for Each Combination
  - a. Only that combination should result in output being true

**For combination (0, 0, 0)  $\rightarrow A' \bullet B' \bullet C'$**

The only time this expression is True is when (0, 0, 0) is passed

**For combination (0, 0, 1)  $\rightarrow A' \bullet B' \bullet C$**

The only time this expression is True is when (0, 0, 1) is passed

3. OR each of the minterms

**F = ?**

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

# Create Your Equation(s)

The 3-step process produces a Canonical SOP!!

1. Determine which rows resulted in 'F' being True (1)
2. Generate an minterm for Each Combination
  - a. Only that combination should result in output being true

**For combination (0, 0, 0)  $\rightarrow A' \bullet B' \bullet C'$**

The only time this expression is True is when (0, 0, 0) is passed

**For combination (0, 0, 1)  $\rightarrow A' \bullet B' \bullet C$**

The only time this expression is True is when (0, 0, 1) is passed

3. OR each of the minterms


A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

$$F = (A' \bullet B' \bullet C') + (A' \bullet B' \bullet C) + (A' \bullet B \bullet C') + (A \bullet B' \bullet C')$$



 
# Implement Your Gate-Based Circuit

$$F =$$
$$(A' \bullet B' \bullet C') +$$
$$(A' \bullet B' \bullet C) +$$
$$(A' \bullet B \bullet C') +$$
$$(A \bullet B' \bullet C')$$


 
# Implementation in **STRUCTURAL** Verilog



```
module Minority(  
    input a, b, c,  
    output out  
);  
  
    // Step 1. Declare your wires  
    wire na, nb, nc;  
    wire w, x, y, z;  
  
    // Step 2. Drive some not a, b, c signals  
    not n1(na, a); // a'  
    not n2(nb, b); // b'  
    not n3(nc, c); // c'  
  
    // Step 3. Drive w, x, y, z  
    and a1(w, na, nb, nc); // a' & b' & c'  
    and a2(x, na, nb, c);  // a' & b' & c  
    and a3(y, na, b, nc);  // a' & b & c'  
    and a4(z, a, nb, nc);  // a & b' & c'  
  
    // Step 4. Drive our output  
    or o1(out, w, x, y, z);  
  
endmodule
```

# Implementation in **BEHAVIORAL** Verilog

Can just use your  
boolean equation

$$F = (A' \bullet B' \bullet C') + (A' \bullet B' \bullet C) + (A' \bullet B \bullet C') + (A \bullet B' \bullet C')$$

```
module Minority(  
    input a, b, c,  
    output out  
);  
    assign out = (~a & ~b & ~c) |  
                 (~a & ~b & c) |  
                 (~a & b & ~c) |  
                 (a & ~b & ~c);  
endmodule
```

# Simplifying Boolean Equation (w/ Behavioral Verilog)

## OLD

$$F = (A' \bullet B' \bullet C') + \\ (A' \bullet B' \bullet C) + \\ (A' \bullet B \bullet C') + \\ (A \bullet B' \bullet C')$$

```
module Minority(  
  input a, b, c,  
  output out  
);  
  assign out = (~a & ~b & ~c) |  
               (~a & ~b & c) |  
               (~a & b & ~c) |  
               (a & ~b & ~c);  
endmodule
```

## NEW

$$F = ?$$

# Simplifying Boolean Equation (w/ Behavioral Verilog)

## OLD

$$F = (A' \bullet B' \bullet C') + (A' \bullet B' \bullet C) + (A' \bullet B \bullet C') + (A \bullet B' \bullet C')$$

```
module Minority(  
    input a, b, c,  
    output out  
);  
    assign out = (~a & ~b & ~c) |  
                (~a & ~b & c) |  
                (~a & b & ~c) |  
                (a & ~b & ~c);  
endmodule
```

## NEW (Distribution)

$$F = [(A' \bullet B') \bullet (C' + C)] + (A' \bullet B \bullet C') + (A \bullet B' \bullet C')$$

```
module Minority(  
    input a, b, c,  
    output out  
);  
    assign out = (~a & ~b & (~c | c)) |  
                (~a & b & ~c) |  
                (a & ~b & ~c);  
endmodule
```

# Simplifying Boolean Equation (w/ Behavioral Verilog)

## OLD

$$F = [(A' \bullet B') \bullet (C' + C)] + (A' \bullet B \bullet C') + (A \bullet B' \bullet C')$$

```
module Minority(  
  input a, b, c,  
  output out  
);  
  assign out = (~a & ~b & (1)) |  
               (~a & b & ~c) |  
               (a & ~b & ~c);  
  
endmodule
```

## NEW (Complements & Null)

$$F = (A' \bullet B') + (A' \bullet B \bullet C') + (A \bullet B' \bullet C')$$

```
module Minority(  
  input a, b, c,  
  output out  
);  
  assign out = (~a & ~b) |  
               (~a & b & ~c) |  
               (a & ~b & ~c);  
  
endmodule
```

# Simplifying Boolean Equation (w/ Behavioral Verilog)

## OLD

$$F = (A' \bullet B') + (A' \bullet B \bullet C') + (A \bullet B' \bullet C')$$

```
module Minority(  
    input a, b, c,  
    output out  
);  
    assign out = (~a & ~b & (1)) |  
                (~a & b & ~c) |  
                (a & ~b & ~c);  
endmodule
```

## NEW (Distribution)

$$F = [(A' \bullet (B' + (B \bullet C')))] + (A \bullet B' \bullet C')$$

```
module Minority(  
    input a, b, c,  
    output out  
);  
    assign out = (~a & (~b | (b & ~c))) |  
                (a & ~b & ~c);  
endmodule
```

# Simplifying Boolean Equation (w/ Behavioral Verilog)

## OLD

$$F = [(A' \bullet (B' + (B \bullet C')))] + (A \bullet B' \bullet C')$$

```
module Minority(  
    input a, b, c,  
    output out  
);  
    assign out = (~a & (~b | (b & ~c))) |  
                (a & ~b & ~c);  
endmodule
```

## NEW (“No Name” & Distribution)

$$F = (A' \bullet B') + (A' \bullet C') + (A \bullet B' \bullet C')$$

```
module Minority(  
    input a, b, c,  
    output out  
);  
    assign out = (~a & ~b) |  
                (~a & ~c) |  
                (a & ~b & ~c);  
endmodule
```



# Simplifying Boolean Equation (w/ Behavioral Verilog)

## OLD

$$F = (A' \bullet B') + (A' \bullet C') + (A \bullet B' \bullet C')$$

```
module Minority(  
    input a, b, c,  
    output out  
);  
    assign out = (~a & ~b) |  
                (~a & ~c) |  
                (a & ~b & ~c);  
endmodule
```

## NEW (Distribution)

$$F = (A' \bullet B') + [(C' \bullet (A' + (A \bullet B')))]$$

```
module Minority(  
    input a, b, c,  
    output out  
);  
    assign out = (~a & ~b) |  
                (~c & (~a | (a & ~b)));  
endmodule
```

# Simplifying Boolean Equation (w/ Behavioral Verilog)

## OLD

$$F = (A' \bullet B') + [(C' \bullet (A' + (A \bullet B')))]$$

```
module Minority(  
    input a, b, c,  
    output out  
);  
    assign out = (~a & ~b) |  
                 (~c & (~a | (a & ~b)));  
endmodule
```

## NEW (Distribution)

$$F = (A' \bullet B') + (A' \bullet C') + (B' \bullet C')$$

```
module Minority(  
    input a, b, c,  
    output out  
);  
    assign out = (~a & ~b) |  
                 (~a & ~c) |  
                 (~b & ~c);  
endmodule
```

# FINAL Implementation in **BEHAVIORAL** Verilog

$$F = (A' \bullet B') + (A' \bullet C') + (B' \bullet C')$$

```
module Minority(  
    input a, b, c,  
    output out  
);  
    assign out = (~a & ~b) | (~a & ~c) | (~b & ~c);  
endmodule
```