

EECS 270 W25

Discussion 11

April 3rd, 2025
By: Mick Gordinier



AGENDA

1. ModelSim and Debugging
2. Sequential Circuit Projects Recap
3. Register Transfer Level (RTL)
Design Introduction
4. Project 7 Checkpoint Discussion
5. Going through FFC Starter Code

ModelSim and Debugging


Please Use ModelSim (Don't Use AG as Debugger)

- If you have not already done so watch these ModelSim discussions:
 - [Discussion 2: Introduction to ModelSim \(+Understanding Delays\)](#)
 - [Discussion 5: Advanced ModelSim with Looking at Buggy Code](#)
 - UNDERSTANDING .do file, .mpf file, and RADICES - 18:30 to 28:30
- [Please follow the steps of getting a working Verilog Linter](#)
 - Will allow you to quickly find small Verilog syntax errors

Sequential Circuit Projects Recap


Combinational Circuits Recap (Projects 1 - 4)

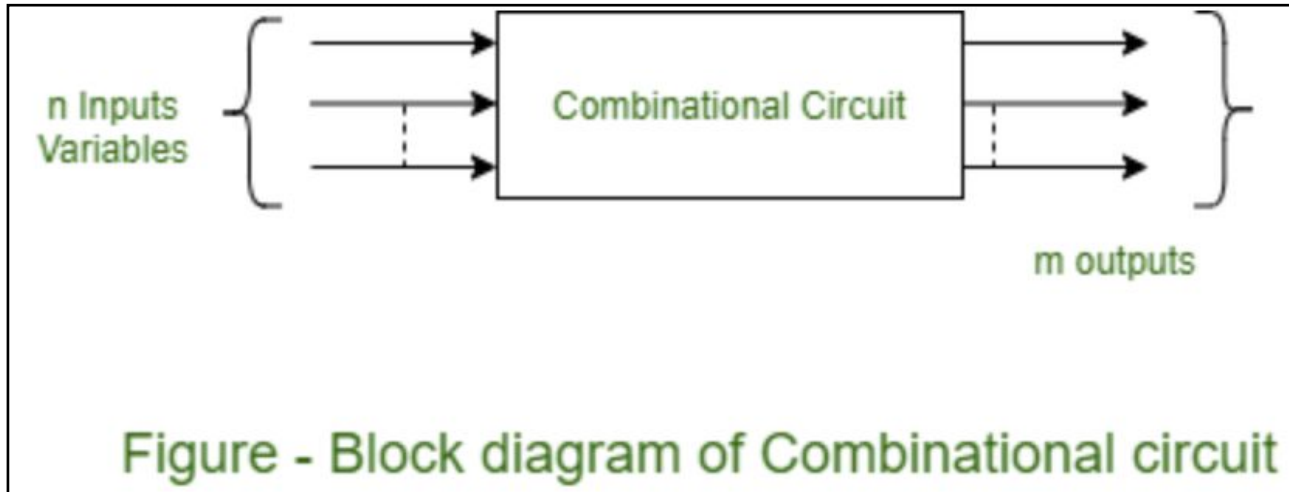- Outputs depend ONLY on present combination of current inputs
- Stateless / No Memory
- Verilog 'assign' - Continuous assignment to a wire data type
- Verilog 'always @*' - Procedural "combinational" block



Sequential Circuits Recap (Project 5 - 7)

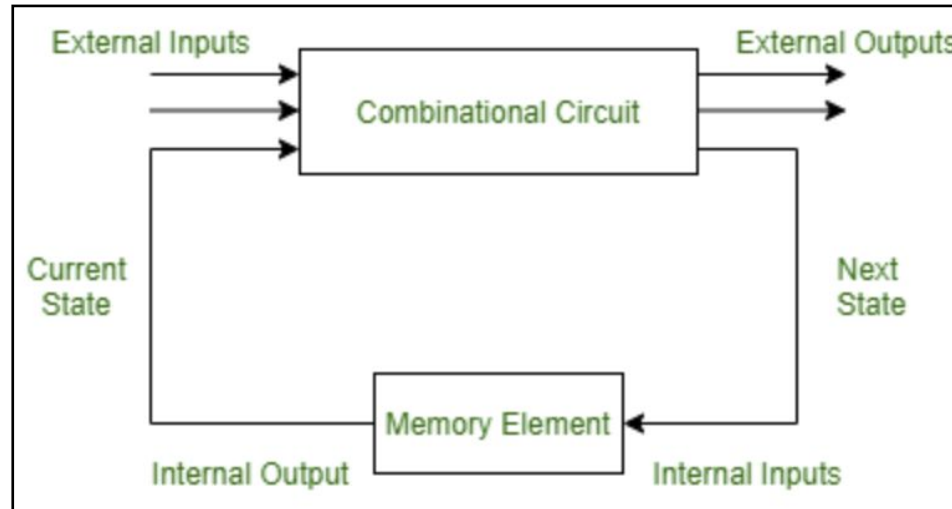- Combinational Circuit + **Memory Element**
- Outputs depend on present combination of inputs and current state
- Use of memory to store previous state/output
- **NOTE: SEQUENTIAL CIRCUITS != SEQUENTIAL EXECUTION**



Sequential Circuit Terminology Recap

- **Synchronous Systems**

- State changes simultaneously occur **ONLY** on an individual clock edge
- **There should only be one global clock that your system uses**

- **Asynchronous Systems**

- State changes can occur **AT ANY TIME**, not necessarily on a clock edge
- Inputs or external events trigger state transitions **immediately**
- Ex: Ripple Counters
 - The first flip-flop toggles on the clock edge
 - Each subsequent flip-flop is **triggered by the previous one's output.**

What is the Behavior Being Shown?

```
module ForgivingLock(  
    input CLK,  
    input Reset,  
    input In,  
    output Unlocked  
);  
  
reg [3:0] Code, Next_Code;  
initial Code = 4'b0000;  
  
always @* begin  
    Next_Code[3] = Code[2];  
    Next_Code[2] = Code[1];  
    Next_Code[1] = Code[0];  
    Next_Code[0] = In;  
end  
  
always @(negedge CLK) begin  
    Code = (Reset) ? 4'b0000 : Next_Code;  
end  
  
assign Unlocked = (~Code[3] & Code[2] & ~Code[1]) |  
                  (Code[2] & ~Code[1] & Code[0]) |  
                  (Code[3] & ~Code[2] & Code[1]) |  
                  (~Code[2] & Code[1] & ~Code[0]);  
  
endmodule
```

Combinational / Sequential
Asynchronous / Synchronous

Combinational / Sequential
Asynchronous / Synchronous

What is the Behavior Being Shown?

```
module ForgivingLock(  
    input CLK,  
    input Reset,  
    input In,  
    output Unlocked  
);  
  
reg [3:0] Code, Next_Code;  
initial Code = 4'b0000;  
  
always @* begin  
    Next_Code[3] = Code[2];  
    Next_Code[2] = Code[1];  
    Next_Code[1] = Code[0];  
    Next_Code[0] = In;  
end  
  
always @(negedge CLK) begin  
    Code = (Reset) ? 4'b0000 : Next_Code;  
end  
  
assign Unlocked = (~Code[3] & Code[2] & ~Code[1]) |  
                  (Code[2] & ~Code[1] & Code[0]) |  
                  (Code[3] & ~Code[2] & Code[1]) |  
                  (~Code[2] & Code[1] & ~Code[0]);  
  
endmodule
```


Combinational
Asynchronous

Sequential
Synchronous

State change **ONLY** occurs on the
edge of a shared clock

What is the Behavior Being Shown?

```
module ForgivingLock(  
    input CLK,  
    input Reset,  
    input In,  
    output Unlocked  
);  
  
    reg [3:0] Code, Next_Code;  
    initial Code = 4'b0000;  
  
    always @* begin  
        Next_Code[3] = Code[2];  
        Next_Code[2] = Code[1];  
        Next_Code[1] = Code[0];  
        Next_Code[0] = In;  
    end  
  
    always @(negedge CLK or posedge Reset) begin  
        Code = (Reset) ? 4'b0000 : Next_Code;  
    end  
  
    assign Unlocked = (~Code[3] & Code[2] & ~Code[1]) |  
        | (Code[2] & ~Code[1] & Code[0]) |  
        | (Code[3] & ~Code[2] & Code[1]) |  
        | (~Code[2] & Code[1] & ~Code[0]);  
  
endmodule
```



Combinational / Sequential
Asynchronous / Synchronous

What is the Behavior Being Shown?

```
module ForgivingLock(  
    input CLK,  
    input Reset,  
    input In,  
    output Unlocked  
);  
  
    reg [3:0] Code, Next_Code;  
    initial Code = 4'b0000;  
  
    always @* begin  
        Next_Code[3] = Code[2];  
        Next_Code[2] = Code[1];  
        Next_Code[1] = Code[0];  
        Next_Code[0] = In;  
    end  
  
    always @(negedge CLK or posedge Reset) begin  
        Code = (Reset) ? 4'b0000 : Next_Code;  
    end  
  
    assign Unlocked = (~Code[3] & Code[2] & ~Code[1]) |  
                     (Code[2] & ~Code[1] & Code[0]) |  
                     (Code[3] & ~Code[2] & Code[1]) |  
                     (~Code[2] & Code[1] & ~Code[0]);  
  
endmodule
```

Sequential

Asynchronous / Synchronous

What is the Behavior Being Shown?

```
module ForgivingLock(  
    input CLK,  
    input Reset,  
    input In,  
    output Unlocked  
);  
  
    reg [3:0] Code, Next_Code;  
    initial Code = 4'b0000;  
  
    always @* begin  
        Next_Code[3] = Code[2];  
        Next_Code[2] = Code[1];  
        Next_Code[1] = Code[0];  
        Next_Code[0] = In;  
    end  
  
    always @(negedge CLK or posedge Reset) begin  
        Code = (Reset) ? 4'b0000 : Next_Code;  
    end  
  
    assign Unlocked = (~Code[3] & Code[2] & ~Code[1]) |  
                     (Code[2] & ~Code[1] & Code[0]) |  
                     (Code[3] & ~Code[2] & Code[1]) |  
                     (~Code[2] & Code[1] & ~Code[0]);  
  
endmodule
```

Sequential
ASYNCHRONOUS

State change **CAN** occur when
reset goes high
(Ignoring the clock)

PLEASE DO NOT USE ASYNCHRONOUS RESETS

```
module ForgivingLock(  
    input CLK,  
    input Reset,  
    input In,  
    output Unlocked  
);  
  
    reg [3:0] Code, Next_Code;  
    initial Code = 4'b0000;  
  
    always @* begin  
        Next_Code[3] = Code[2];  
        Next_Code[2] = Code[1];  
        Next_Code[1] = Code[0];  
        Next_Code[0] = In;  
    end  
  
    always @(negedge CLK or posedge Reset) begin  
        Code = (Reset) ? 4'b0000 : Next_Code;  
    end  
  
    assign Unlocked = (~Code[3] & Code[2] & ~Code[1]) |  
                     (Code[2] & ~Code[1] & Code[0]) |  
                     (Code[3] & ~Code[2] & Code[1]) |  
                     (~Code[2] & Code[1] & ~Code[0]);  
  
endmodule
```

“My friend told me
to add it”



Sequential
ASYNCHRONOUS

State change **CAN** occur when
reset goes high
(Ignoring the clock)

Register Transfer Level (RTL) Design Introduction

Verilog's Many Levels of Abstraction

**“BEHAVIORAL
VERILOG”**

Behavioral Level

Project 3B - 7

Dataflow Level

**“STRUCTURAL
VERILOG”**

Gate Level

Projects 0 - 3A

Switch Level

**Because of Shannon,
we can ignore**

Verilog's Many Levels of Abstraction

**“BEHAVIORAL
VERILOG”**

Behavioral Level

Project 3B - 7

Register Transfer Level (RTL)

Dataflow Level

**“STRUCTURAL
VERILOG”**

Gate Level

Projects 0 - 3A


Switch Level

**Because of Shannon,
we can ignore**

RTL Design Overview

- Splitting up design in Controller and Datapath
- **Controller** - Controls and orchestrates the Datapath operations
- **Datapath** - Computation on the signals
 - Arithmetic - Add/Subtract/Multiple/Count/...
 - Logical - Shift Left / Shift Right / Arithmetic Shift / bitwise Ops
 - Other - Clear / Load / Hold

RTL Sequential Circuit

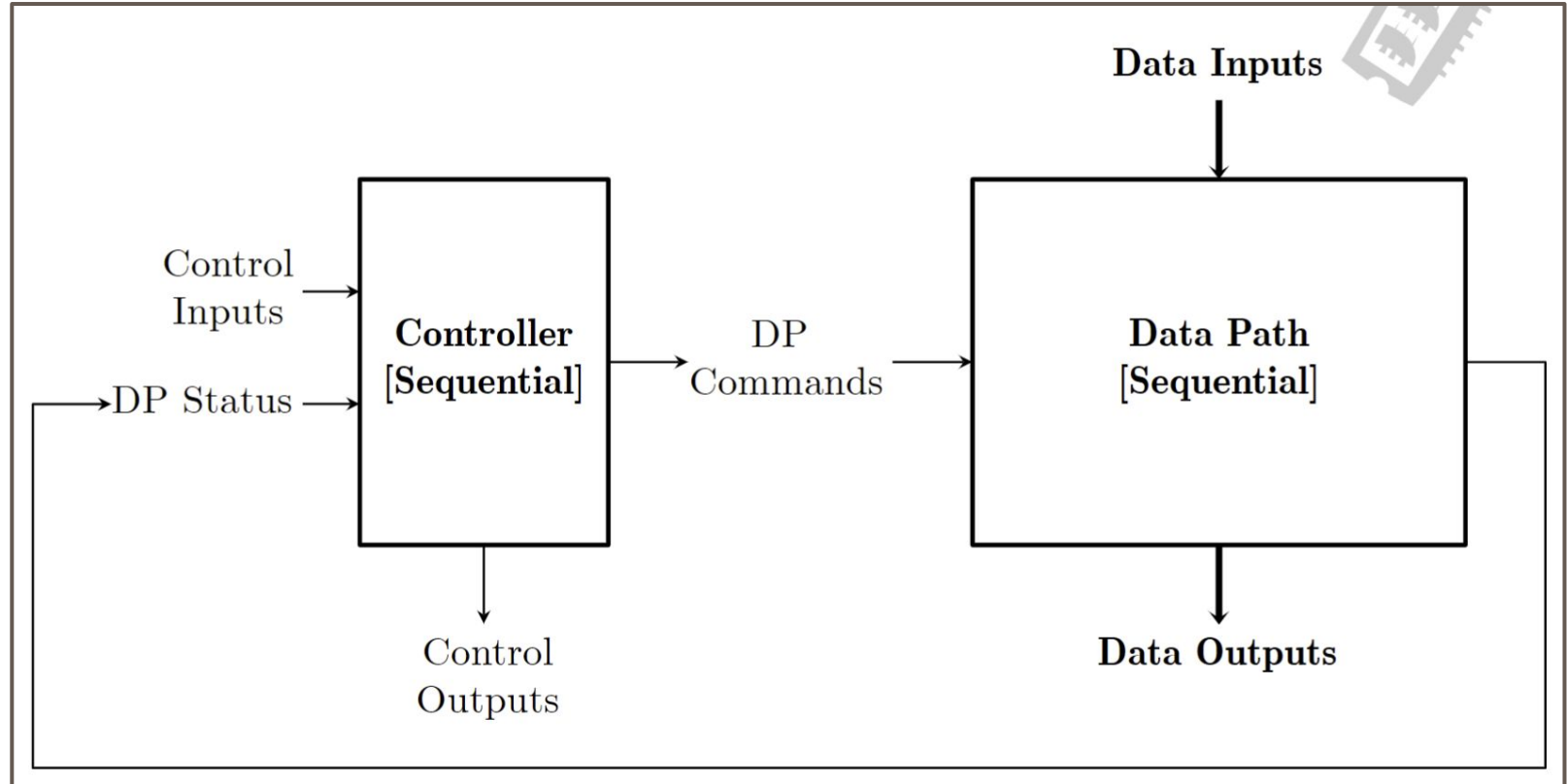

Main Differences with Behavioral / RTL Design

| Feature | Behavioral Verilog | RTL Verilog |
|--|---|--------------------------------|
| Abstraction Level | Very High (Nearly Software) | Medium (Closer to Hardware) |
| Synthesizable | Sometimes (Not everything can be synthesized to hardware) | Always |
| Main Use Case | Simulation and quick modeling | Actual hardware implementation |
| Need to Explicitly Describe Underlying Gates/Hardware | No | No |


Project 7 Checkpoint Discussion (Sequential Calculator)

Project 7 Deadlines

- Project 7 Checkpoint (Due: 4/15)
 - Implemented Adding and Subtracting in your Four Func Calculator
 - **Worth 10% of your grade**
 - Will require a testbench for adding and subtracting
 - **Allows us to run your project on FPGA to ensure no timing issues**
- Project 7 Final (Due: 4/25)
 - Implementing Multiplication and Division in your Four Func Calculator
 - Requires full testbench
 - **Worth 90% of your grade**
- **NOTE: THERE IS NO IN-PERSON SIGN OFFS FOR THIS PROJECT**


Four Function Calculation (Checkpoint) Overview

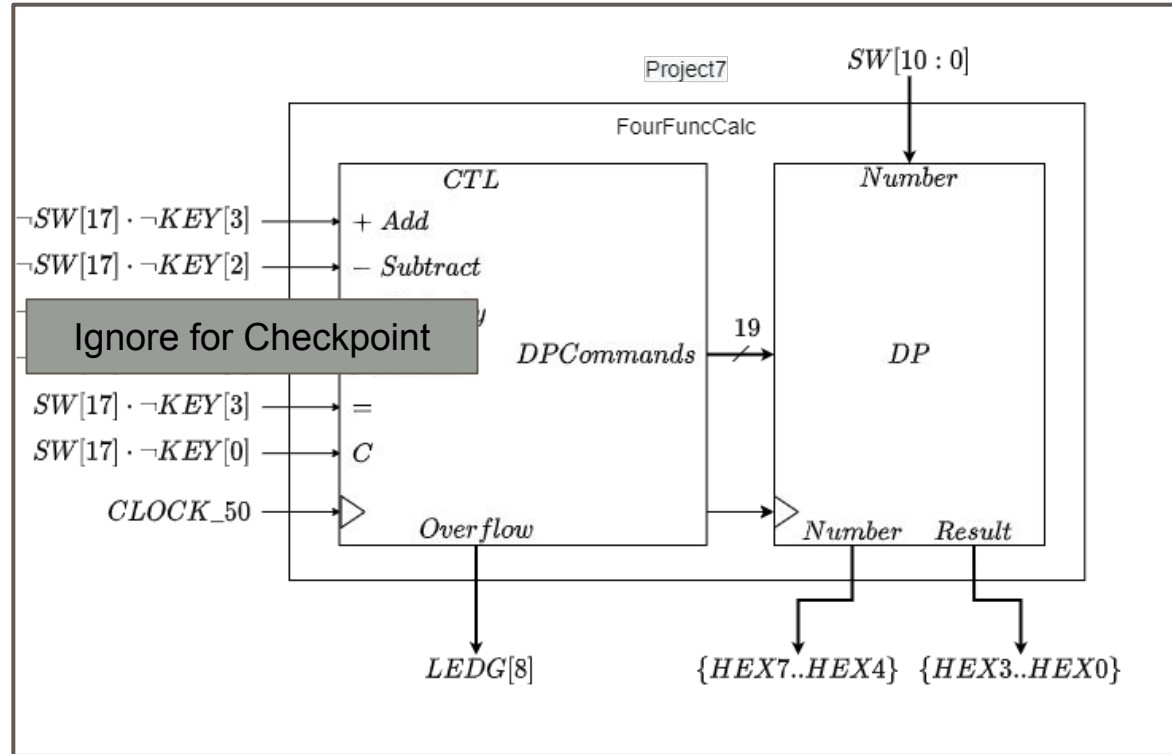- Controller Input
 - **+**, **-**, **=**, **C**
 - 50 MHz Clock
- Datapath Input
 - DPCommands
 - Number
- Outputs
 - HEX Displays
 - Overflow bit




FFC Datapath (CP)

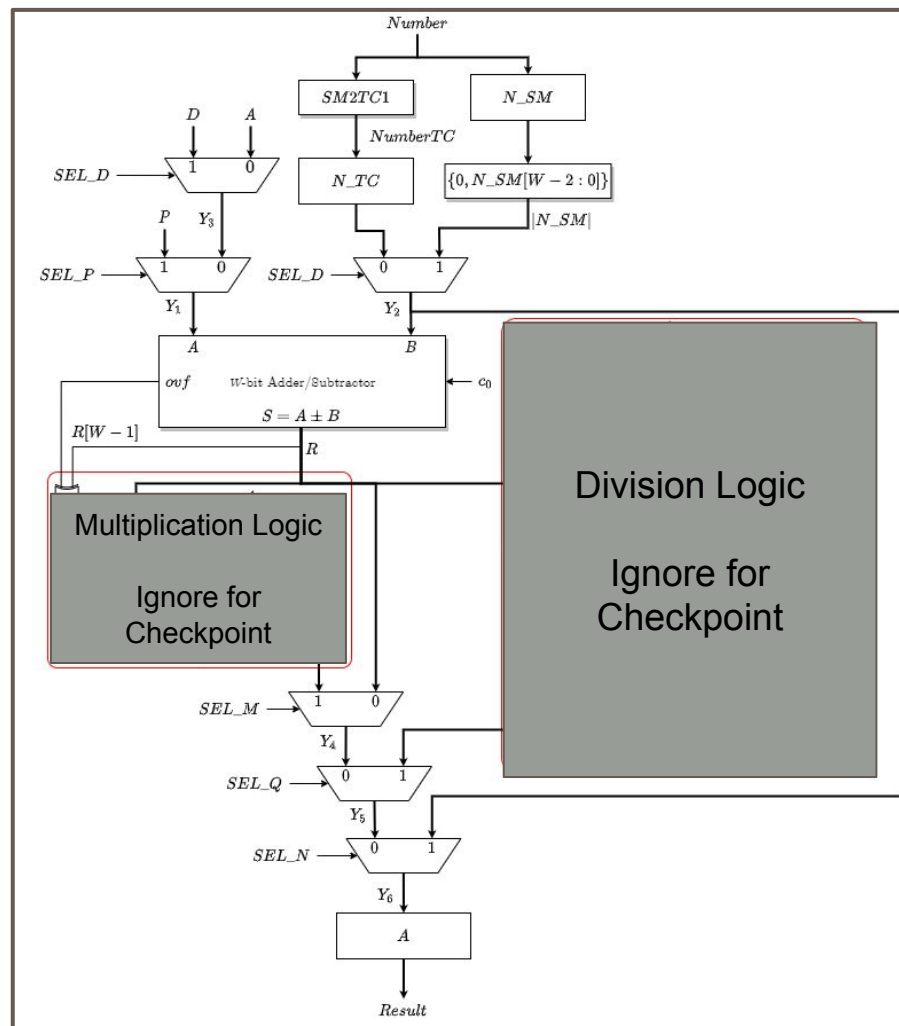- Only need to focus on implementing add/sub datapaths
- **NOTE:** Must only have 1 instantiation of the AddSub modules



I/O Interface Notes

 - Dealing with 11-bit numbers
- **Number SWs inputted as Signed-Magnitude**
- But computation in datapath assumes 2's complement
- **Overflow - Outside 11-bit 2C range**
 - [-1024, 1023]
- **vs. Display "----" if can't be displayed**
 - [-999, 999]




I/O Interface

Figure 1 shows the datapath/control decomposition and the DE2-115 interface of the calculator.

- **Entering and displaying numbers:** Signed-magnitude numbers, in the range $[-1023, 1023]$, can be entered using SW[10:0] and should be displayed on {HEX7, HEX6, HEX5, HEX4}. Operation results should be displayed on {HEX3, HEX2, HEX1, HEX0}. Numbers outside the range $[-999, 999]$ should be displayed as ---- indicating "can't be displayed".
- **Entering operations:** The four arithmetic operations can be entered by pressing a pushbutton KEY with SW[17] set to 0. Refer to the mapping in Figure 1.
- **Entering commands:** Besides entering numbers, two KEYs are used to enter the following commands when SW[17] is set to 1:
 - = (equals): Pressing KEY[3] displays the result of the operation on {HEX3, HEX2, HEX1, HEX0}.
 - C (clear): Pressing KEY[0] clears the result display and returns the calculator to its initial state.
- **Overflow indicator:** Overflow should be indicated by LEDG[8] if any operation result is outside the range of 11-bit two's complement numbers, i.e., $[-1024, 1023]$ (would have been better if this was a red LED because of its location between the HEX displays!)

FFC High-Level FSM

 - When turned on, should display 0 as result
 - Can either load in a value or perform operation from initialization
- Then, you perform many OP → “Number =”
- Clearing should take you straight back to 0



| | |
|---------|----|
| Turn On | 0 |
| 5 = | 5 |
| − | 5 |
| + | 5 |
| × | 5 |
| 7 = | 35 |
| + | 35 |
| − | 35 |
| 5 = | 30 |
| / | 30 |
| 4 = | 7 |
| C | 0 |

Timing Errors in Project 7

- EECS 270 does not focus on how to handle timing errors
 - **Take EECS 470 to dive deeper into timing issues**
- If you occur timing errors
 - Use Clock_Div module
 - **Slow down the clock**

Going through FourFuncCalc starter code

FourFuncCalc Starter Code


- **Module that handles both the controller and datapath logic**
- Instantiated by the top level module “Project7”
- **IT IS NOT COMPLETED**

```
File Name: FourFuncCalc.v
module FourFuncCalc
  #(parameter W = 11)           // Default bit width
  (
    input Clock,
    input Clear,                 // C button
    input Equals,               // = button: displays result so far
    input Add,                  // + button
    input Subtract,            // - button
    input Multiply,            // x button (times)
    input Divide,              // / button (division quotient)
    input [W-1:0] Number,      // Must be entered in signed-magnitude on SW[W-1:0]
    output signed [W-1:0] Result, // Calculation result in two's complement
    output Overflow             // Indicates result can't be represented in W bits
  );
  localparam WW = 2 * W;       // Double width for Booth multiplier
  localparam BoothIter = $clog2(W); // Width of Booth Counter
```

Datapath Components (1)

```
//-----
// Registers
// For each register, declare it along with the controller commands that
// are used to update its state following the example for register A
//-----

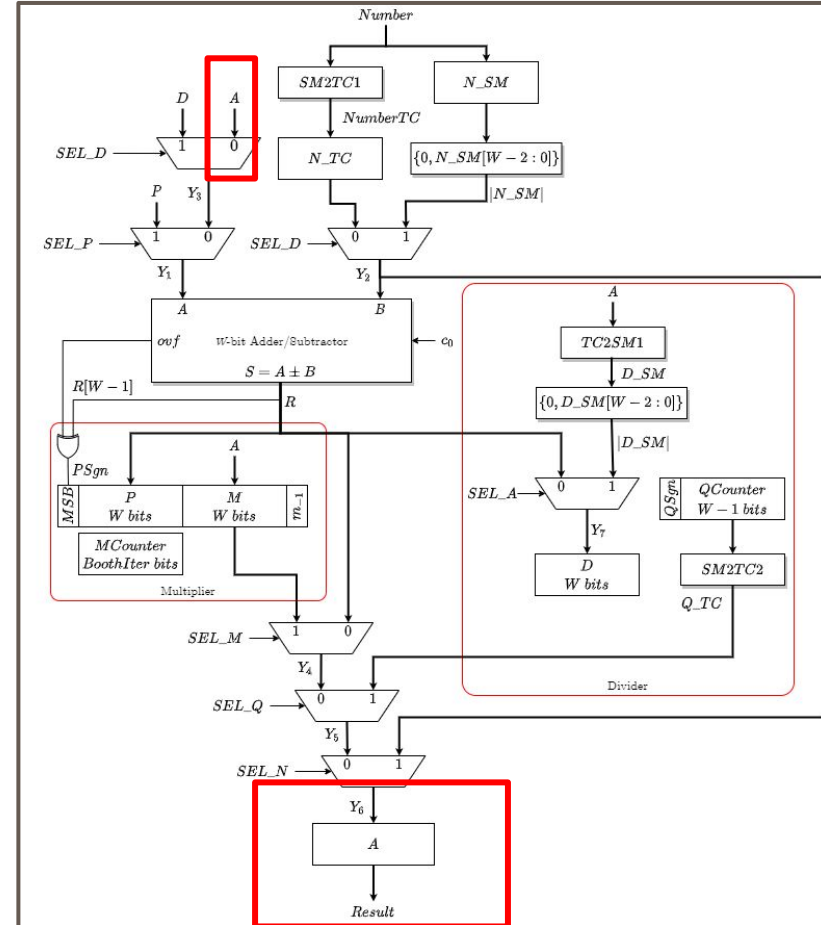reg signed [W-1:0] A;                                // Accumulator
wire CLR_A, LD_A;                                     // CLR_A: A <= 0; LD_A: A <= Q
```




Datapath Components (2)

```
//-----
// Number Converters
// Instantiate the three number converters following the example of SM2TC1
//-----

wire signed [W-1:0] NumberTC;           // Two's complement of Number
SM2TC #(.width(W)) SM2TC1(Number, NumberTC);
```

REMEMBER: Number is coming in as Signed Magnitude representation

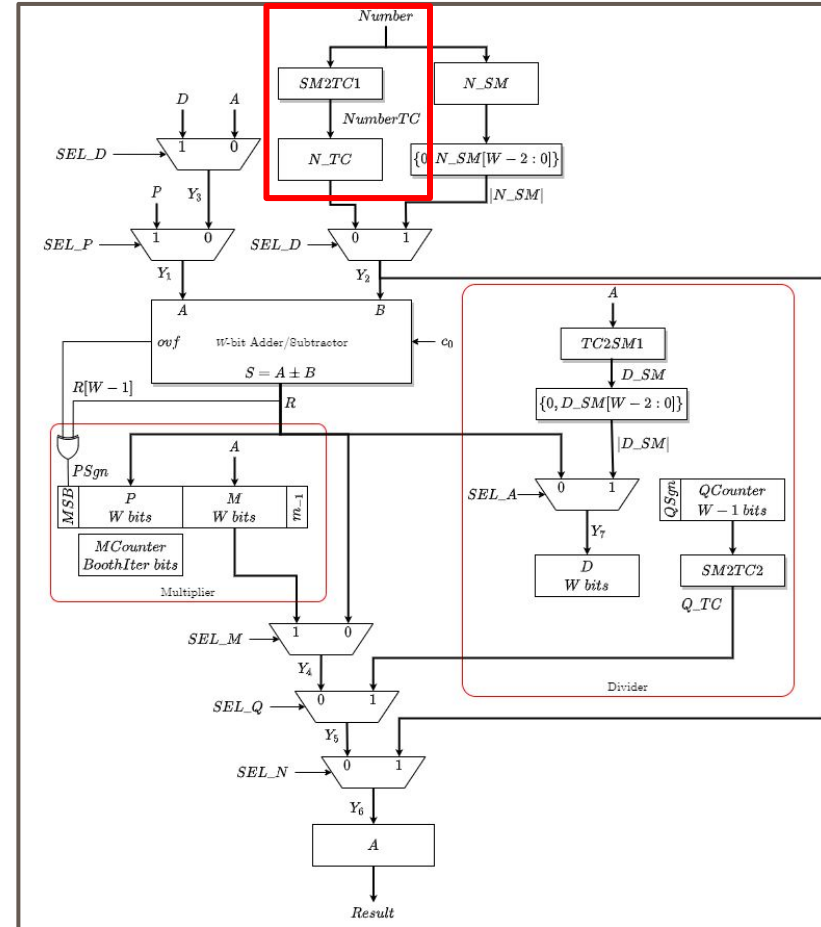REMEMBER: Adder/Subtractor does computation on 2C representation



Datapath Components (3)

```
//-----
// Adder/Subtractor
//-----

wire c0;                                // 0: Add, 1: Subtract
wire ovf;                                // Overflow
AddSub #(.W(W)) AddSub1(Y1, Y2, c0, R, ovf);
wire PSgn = R[W-1] ^ ovf;                // Corrected P Sign on Adder/Subtractor overflow
```

```
// Full Adder
module FullAdder
(
    input a, b, cin,
    output s, cout
);

    assign s = a ^ b ^ cin;
    assign cout = a & b | cin & (a ^ b);
endmodule // FullAdder
```


```
module AddSub
#(parameter W = 16)
(
    input [W-1:0] A, B,
    input c0,
    output [W-1:0] S,
    output ovf
);

    wire [W:0] c;
    assign c[0] = c0;

    // Instantiate and "chain" W full adders
    genvar i;
    generate
        for (i = 0; i < W; i = i + 1)
            begin: RCAddSub
                FullAdder FA(A[i], B[i] ^ c[i], c[i], S[i], c[i+1]);
            end
    endgenerate

    // Overflow
    assign ovf = c[W-1] ^ c[W];
endmodule // AddSub
```

AddSub has been implemented for you

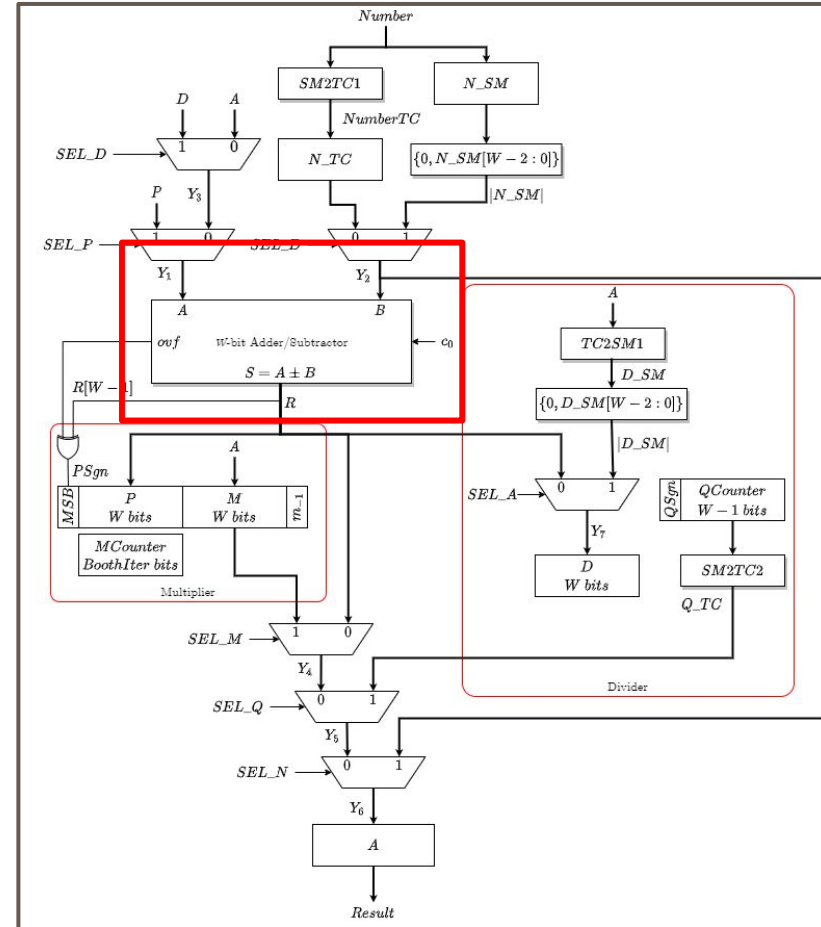

Controller State Assignment

```
/**
 * Datapath Controller
 * Suggested Naming Convention for Controller States:
 *   All names start with X (since the traditional Q connotes quotient in this project)
 *   XAdd, XSub, XMul, and XDiv label the start of these operations
 *   XA: Prefix for addition states (that follow XAdd)
 *   XS: Prefix for subtraction states (that follow XSub)
 *   XM: Prefix for multiplication states (that follow XMul)
 *   XD: Prefix for division states (that follow XDiv)
 */
/**
 *-----
 * Controller State and State Labels
 * Replace ? with the size of the state registers X and X_Next after
 * you know how many controller states are needed.
 * Use localparam declarations to assign labels to numeric states.
 * Here are a few "common" states to get you started.
 *-----
 */

reg [?:0] X, X_Next;

localparam XInit      = 'd0; // Power-on state (A == 0)
localparam XClear     = ;     // Pick numeric assignments
localparam XLoadA     = ;
localparam XResult    = ;
```

You need to determine all the states to your FFC Controller.

We have given you a few states to first consider. Can change and add your own.

Controller State Transition (Next State Logic)

```
//-----  
// Controller State Transitions  
// This is the part of the project that you need to figure out.  
// It's best to use ModelSim to simulate and debug the design as it evolves.  
// Check the hints in the lab write-up about good practices for using  
// ModelSim to make this "chore" manageable.  
// The transitions from XInit are given to get you started.  
//-----  
  
always @*  
case (X)  
    XInit:  
        if (Clear)  
            X_Next <= XInit;  
        else if (Equals)  
            X_Next <= XLoadA;  
        else if (Add)  
            X_Next <= XAdd;  
        else if (Subtract)  
            X_Next <= XSub;  
        else if (Multiply)  
            X_Next <= XMul;  
        else if (Divide)  
            X_Next <= XDiv;  
        else  
            X_Next <= XInit;  
    endcase
```

You need to determine all the controller transitions of your FFC Controller.

REMEMBER: Controller inputs are:

- 1. State of the datapath and**
- 2. User inputs**

Controller State Command Bits (Output Logic)

```
//-----  
// Controller Commands to Datapath  
// No freebies here!  
// Using assign statements, you need to figure when the various controller  
//      commands are asserted in order to properly implement the datapath  
// operations.  
//-----
```

You need to determine which controller command bits goes high given what controller state you are in

Assume the controller bits are Moore outputs

Controller State Update (Memory Logic)

```
//-----  
// Controller State Update  
//-----  
  
    always @(posedge Clock)  
        if (Clear)  
            X <= XClear;  
        else  
            X <= X_Next;
```


Datapath State Update (Memory Logic)

```
//-----  
// Datapath State Update  
// This part too is your responsibility to figure out.  
// But there is a hint to get you started.  
//-----  
  
    always @(posedge Clock)  
    begin  
        N_TC <= LD_N ? NumberTC : N_TC;  
  
    end
```


Must Finish

Calculator Outputs
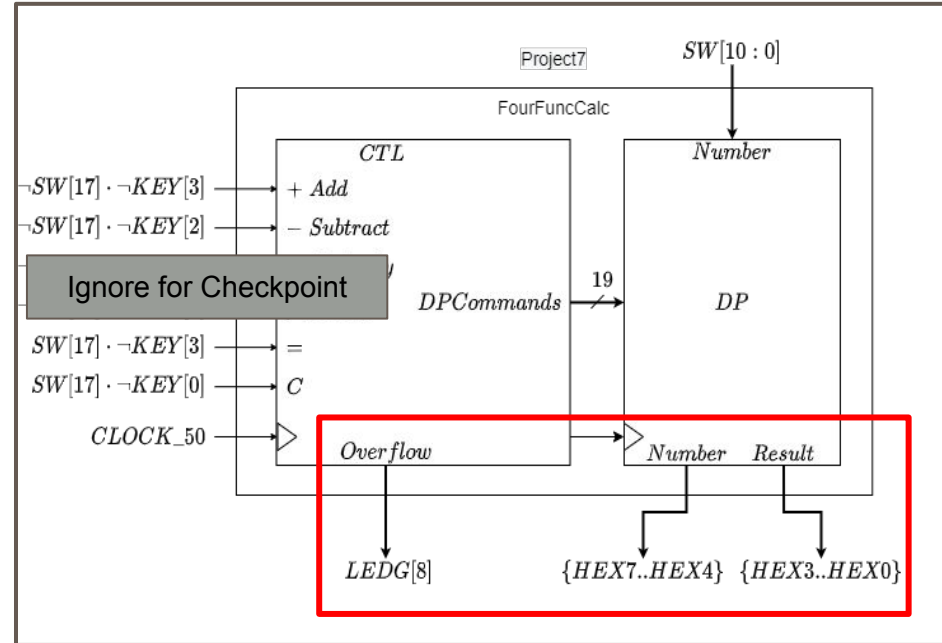
```
//-----  
// Calculator Outputs  
// The two outputs are Result and Overflow, get it?  
//-----
```



Understanding RTL Example

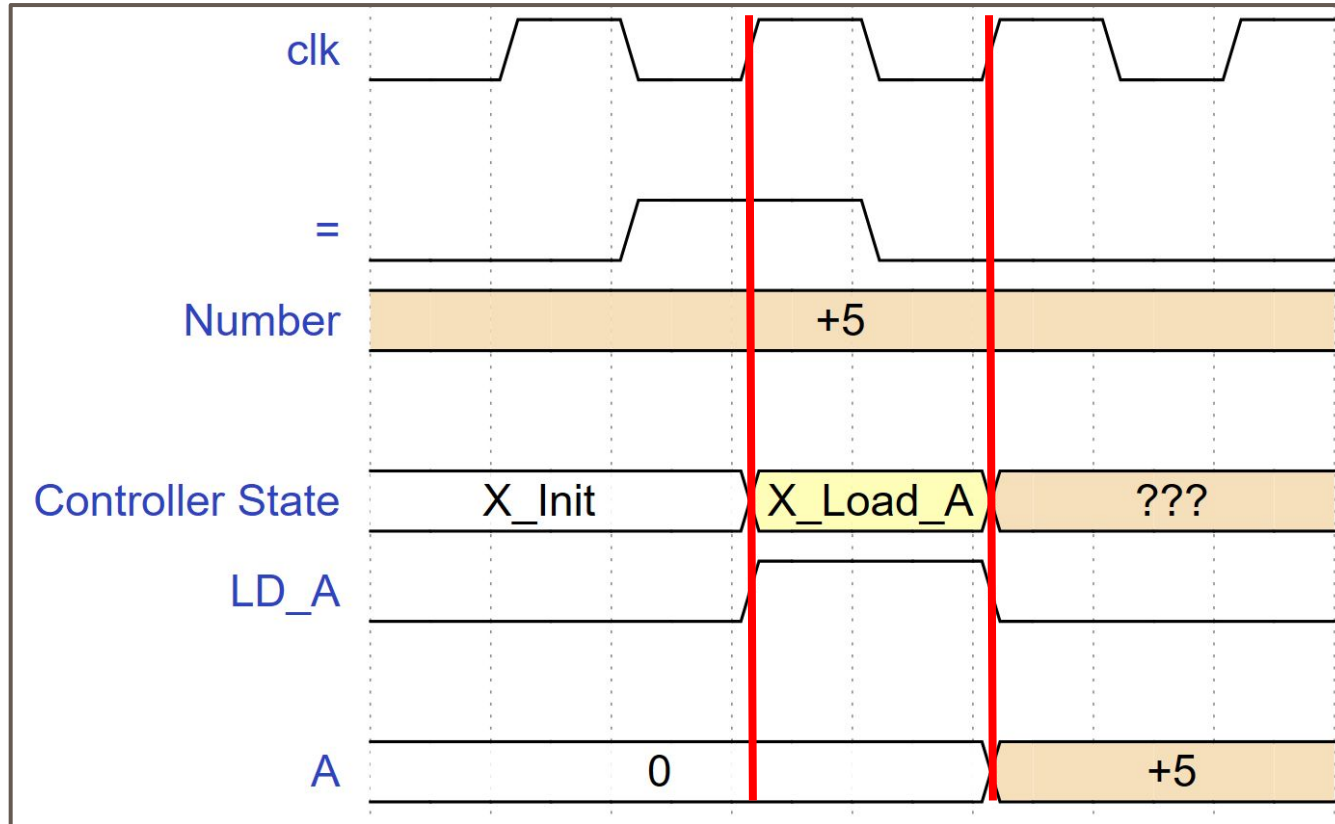

NOTE: Not showing N_TC register

A is loaded on the cycle AFTER the Load_A controller state

THANK YOU

