

EECS 270 W25

Discussion 12

April 10th, 2025
By: Mick Gordinier



AGENDA

1. Course Evaluations
2. RTL Design Recap
3. Project 7 Full Discussion
4. P7 Example XInit → Loading Value
5. P7 Booth Multiplication
6. ModelSim Demo of Booth Mul
7. P7 Division

Course Evaluations

Please Do Course Evaluations!!

- We are always continuing to improve upon the course and give the best 270 experience possible!
- We want to hear from you, understand your 270 experience, and want to know what worked and didn't
- For discussion comment/improvements, please let me know under 'Additional comments for Mick Gordinier'

Register Transfer Level (RTL) Design Recap

Verilog's Many Levels of Abstraction

**“BEHAVIORAL
VERILOG”**

Behavioral Level

Project 3B - 7

Dataflow Level

**“STRUCTURAL
VERILOG”**

Gate Level

Projects 0 - 3A

Switch Level

**Because of Shannon,
we can ignore**

Verilog's Many Levels of Abstraction

**“BEHAVIORAL
VERILOG”**

Behavioral Level

Project 3B - 7

Register Transfer Level (RTL)

Dataflow Level

**“STRUCTURAL
VERILOG”**

Gate Level

Projects 0 - 3A


Switch Level

**Because of Shannon,
we can ignore**

RTL Design Overview

- Splitting up design in Controller and Datapath
- **Controller** - Controls and orchestrates the Datapath operations
- **Datapath** - Computation on the signals
 - Arithmetic - Add/Subtract/Multiple/Count/...
 - Logical - Shift Left / Shift Right / Arithmetic Shift / bitwise Ops
 - Other - Clear / Load / Hold

RTL Sequential Circuit

 

Main Differences with Behavioral / RTL Design

| Feature | Behavioral Verilog | RTL Verilog |
|--|---|--------------------------------|
| Abstraction Level | Very High (Nearly Software) | Medium (Closer to Hardware) |
| Synthesizable | Sometimes (Not everything can be synthesized to hardware) | Always |
| Main Use Case | Simulation and quick modeling | Actual hardware implementation |
| Need to Explicitly Describe Underlying Gates/Hardware | No | No |


Project 7 Full Discussion (Sequential Calculator)

Project 7 Deadlines

- Project 7 Checkpoint (Due: 4/15)
 - Implemented Adding and Subtracting in your Four Func Calculator
 - **Worth 10% of your grade**
 - Will require a testbench for adding and subtracting
 - **Allows us to run your project on FPGA to ensure no timing issues**
- Project 7 Final (Due: 4/25)
 - Implementing Multiplication and Division in your Four Func Calculator
 - Requires full testbench
 - **Worth 90% of your grade**
- **NOTE: THERE IS NO IN-PERSON SIGN OFFS FOR THIS PROJECT**


Four Function Calculation (Checkpoint) Overview

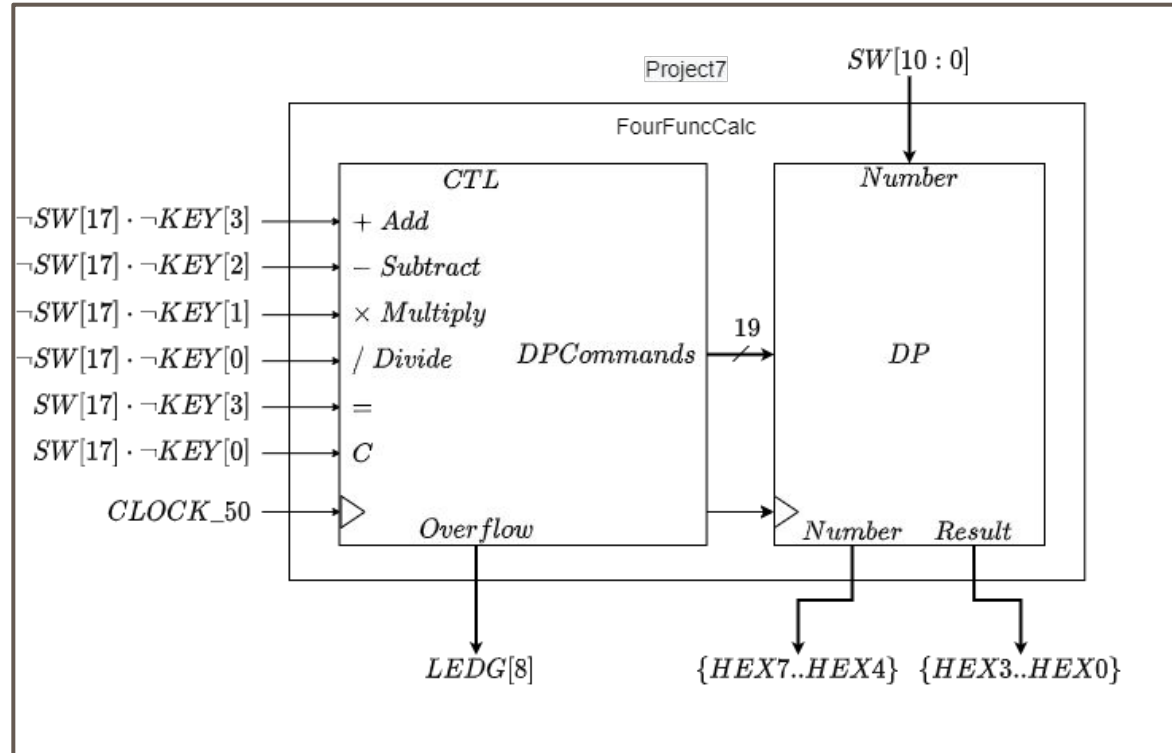- Controller Input
 - **+, -, x, /, =, C**
 - 50 MHz Clock
- Datapath Input
 - DPCOMMANDS
 - Number
- Outputs
 - HEX Displays
 - Overflow bit




FFC Datapath (CP)

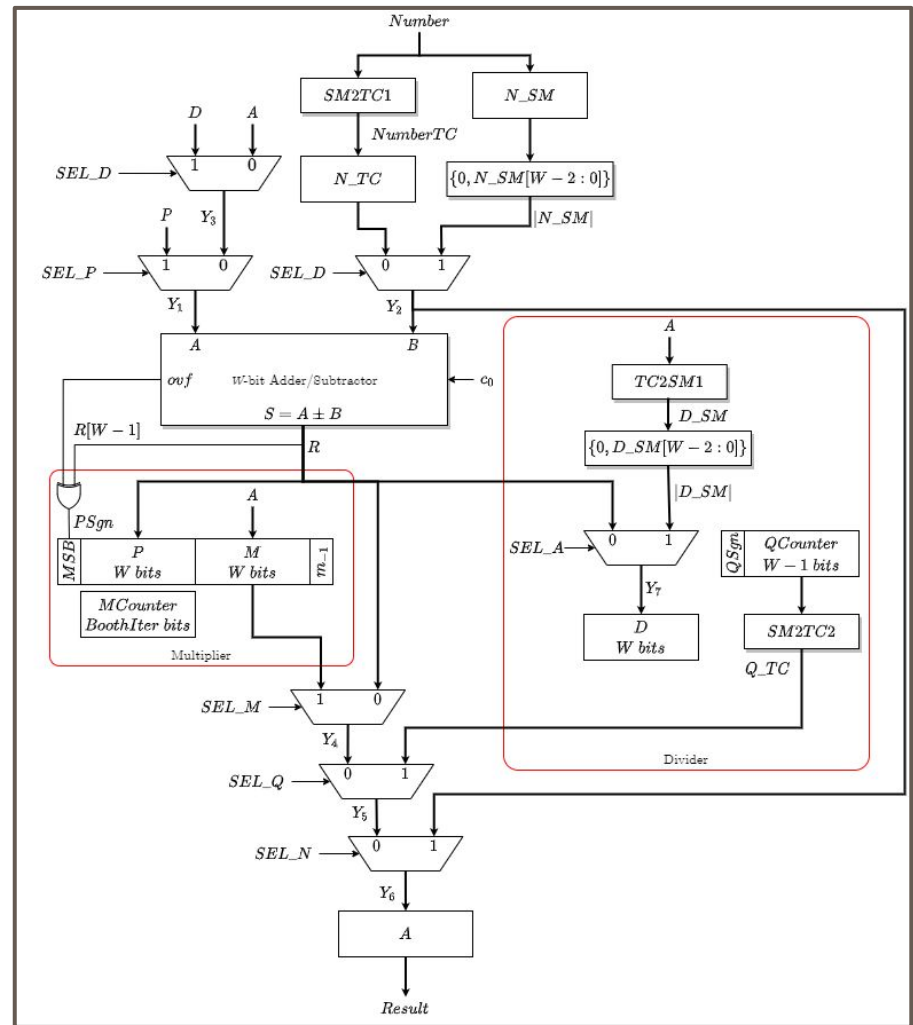- Only need to focus on implementing add/sub datapaths
- NOTE:** Must only have 1 instantiation of the AddSub modules



I/O Interface Notes

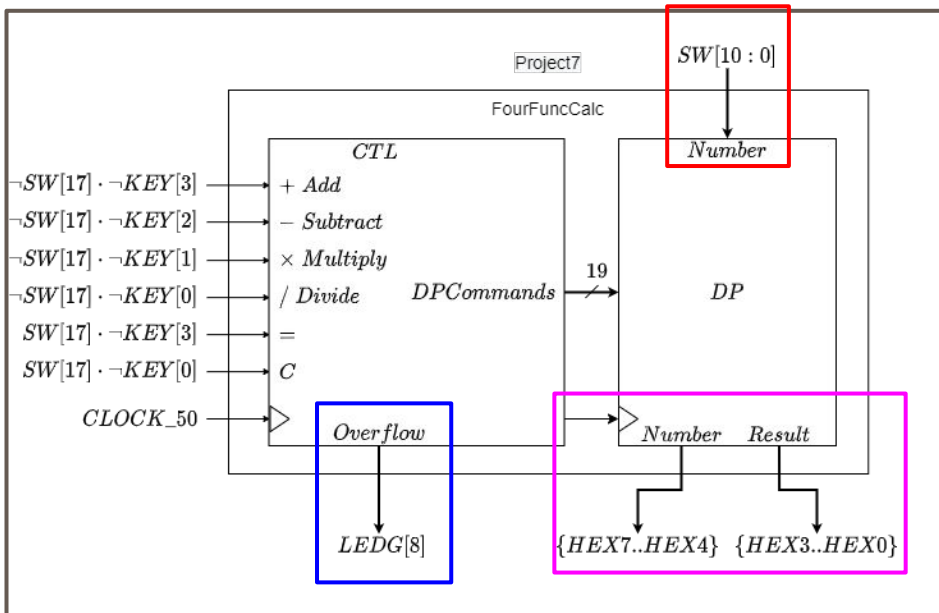- Dealing with 11-bit numbers
- **Number SWs inputted as Signed-Magnitude**
- But computation in datapath assumes 2's complement
- **Overflow - Outside 11-bit 2C range**
 - [-1024, 1023]
- **vs. Display "----" if can't be displayed**
 - [-999, 999]





I/O Interface

Figure 1 shows the datapath/control decomposition and the DE2-115 interface of the calculator.



- **Entering and displaying numbers:** Signed-magnitude numbers, in the range $[-1023, 1023]$, can be entered using SW[10:0] and should be displayed on {HEX7, HEX6, HEX5, HEX4}. Operation results should be displayed on {HEX3, HEX2, HEX1, HEX0}. Numbers outside the range $[-999, 999]$ should be displayed as ---- indicating "can't be displayed".
- **Entering operations:** The four arithmetic operations can be entered by pressing a pushbutton KEY with SW[17] set to 0. Refer to the mapping in Figure1.
- **Entering commands:** Besides entering numbers, two KEYs are used to enter the following commands when SW[17] is set to 1:
 - = (equals): Pressing KEY[3] displays the result of the operation on {HEX3, HEX2, HEX1, HEX0}.
 - C (clear): Pressing KEY[0] clears the result display and returns the calculator to its initial state.
- **Overflow indicator:** Overflow should be indicated by LEDG[8] if any operation result is outside the range of 11-bit two's complement numbers, i.e., $[-1024, 1023]$ (would have been better if this was a red LED because of its location between the HEX displays!)

P7 Example XInit → Loading Value (Ignoring N_TC Reg)

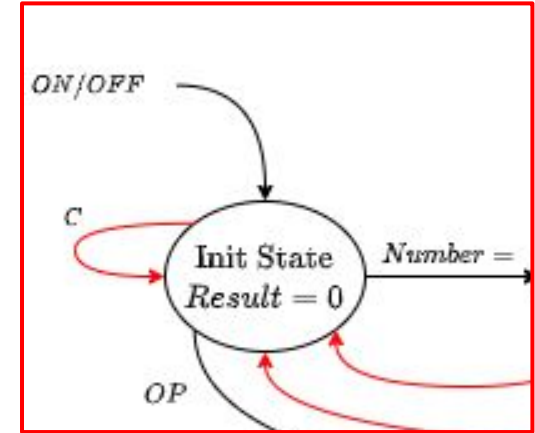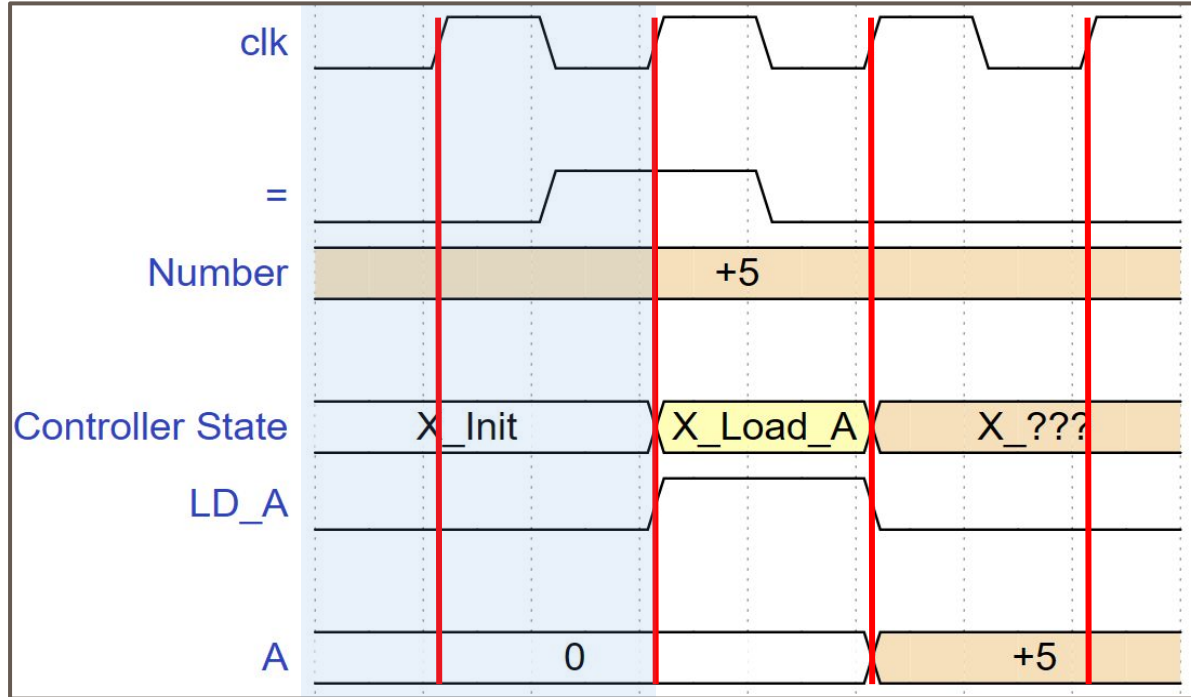1. On Initialization, Should stay Init State



  2. Once '=' Seen on Posedge clk, Begin Loading





NOTES:

Only **CONTROLLER** has seen the '='.

Controller needs to inform datapath.
Controller updates its internal state
→ **Changes command bits**

 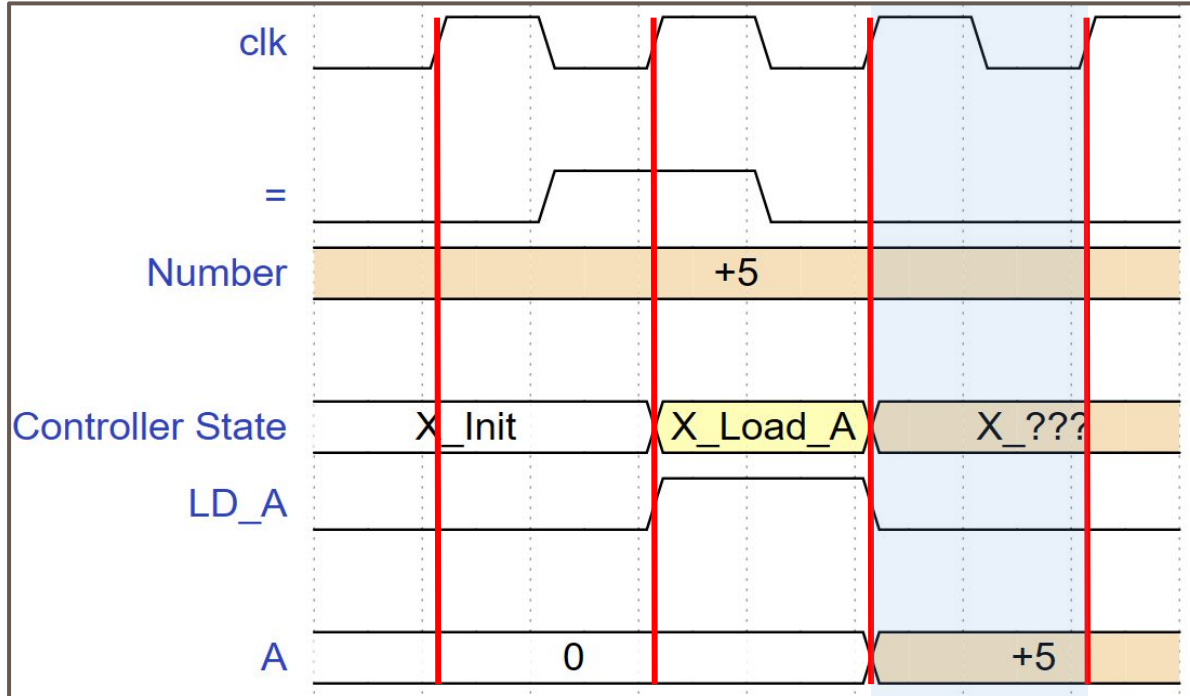3. LD_A Command Seen by Datapath NEXT Cycle





NOTES:

Datapath sees 'LD_A' command
CYCLE AFTER it was set by the
controller.

Controller want to ensure 'A' only
loads for **ONE CYCLE**.

 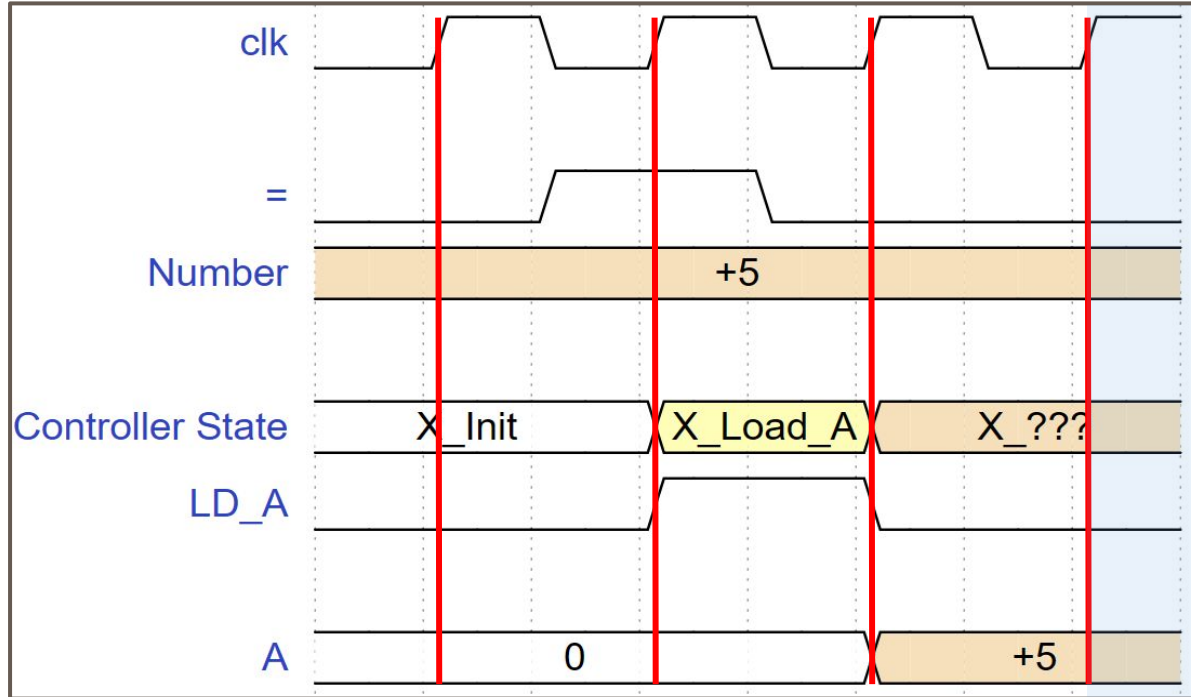4. Accumulator Hold Onto Value Until Next Command



P7 Booth Multiplication

Understanding Booth Multiplication In-depth


- [Watch Lecture Session 19](#)
- [Go through Lecture Slides](#)
- Discussion today is focussed on implementation, not understanding Booth Multiplication

Booth Multiplication in P7

- Optimized W-bit x W-bit multiplication
- Requires multiple cycles to complete (Iterates 'CNT' times)
- **WE PROVIDE YOU WITH A COMPLETED PARAMETERIZED BOOTH MUL**
- Your Job: Integrate Booth Mul with your four function calculator
- **REMEMBER: YOU CAN ONLY USE 1 ADD/SUB MODULE IN FFC**
 - You must integrate Booth Mul with using the same add/sub module


Booth Mul Registers

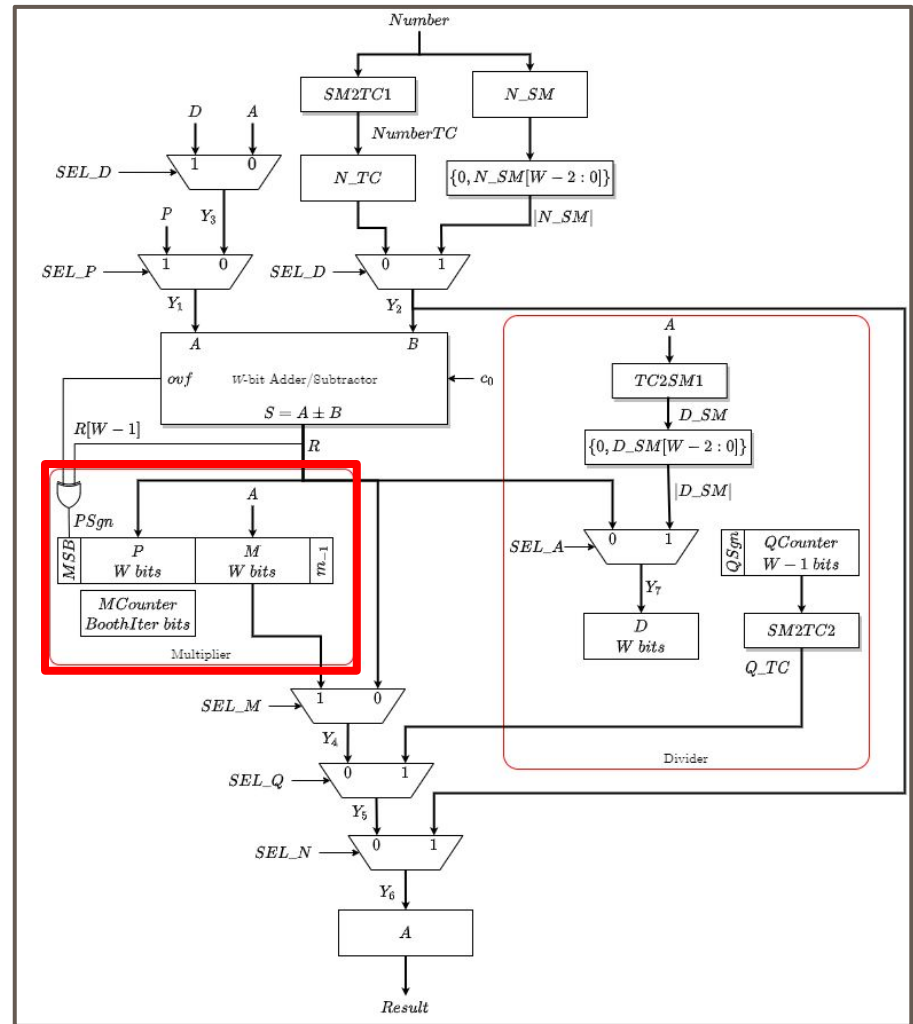- Performing: **$A * \text{Number}$**
 - Both are W -bits wide
 - Both are 2's complement
- W -bit P , M registers
 - Hold final $2W$ -bit result
- Additional 1-bit MSB, m_{-1}
- MCounter register
 - Need to keep track of how many iterations we have left





IMPORTANT: Storing Result & Overflow (Multiplication)

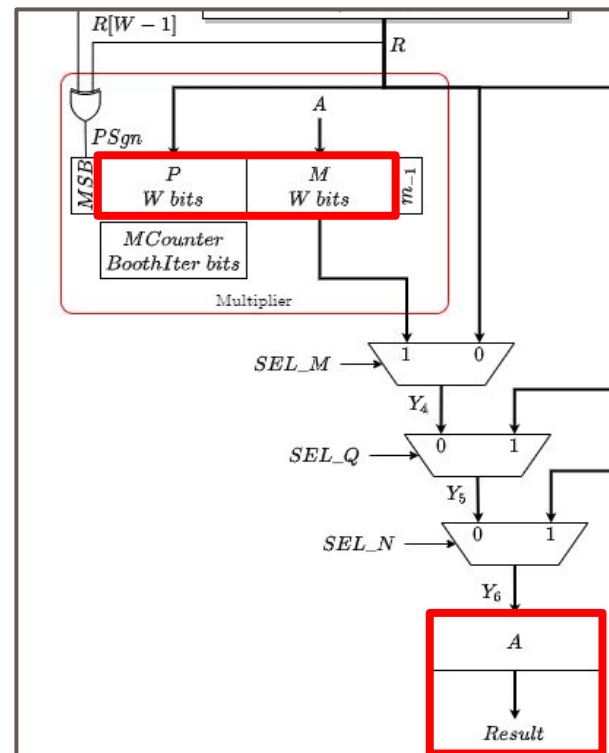- Performing: **$A * \text{Number}$**
 - Both are W -bits wide
 - Both are 2's complement signed
- Your final result is **$2W$ -bits $\{P, M\}$**
- **Problem: Accumulator is only W -bits wide**
- **How can we handle this?**
- **How do we determine if our result can fit in A ?**
- **What do we do if we can't fit our final result in A ?**




Multiplier V2.0 Execution Trace

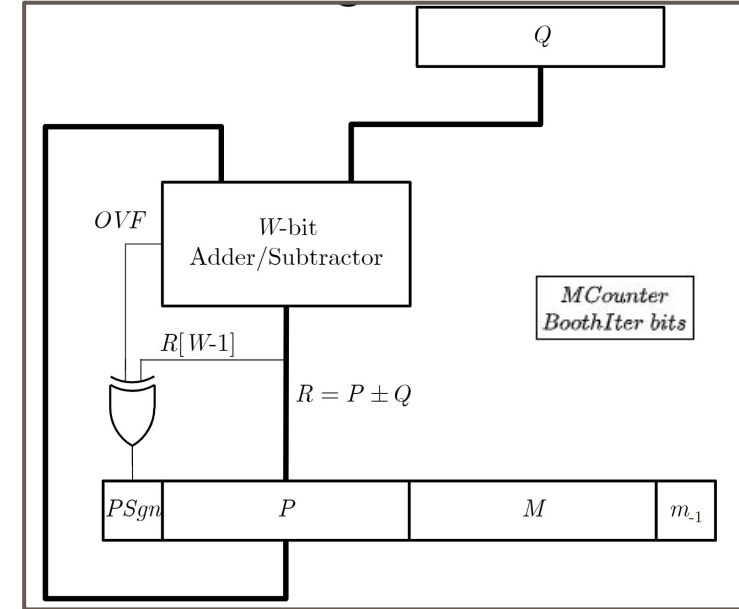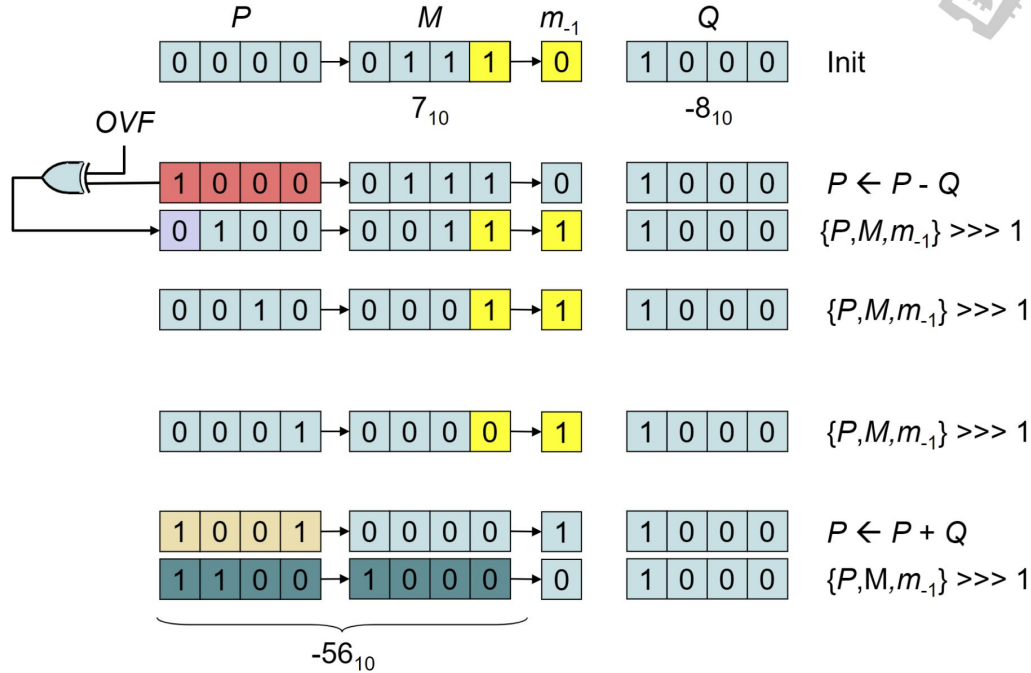

What is an arithmetic vs. logical shift?

Controller State Diagram

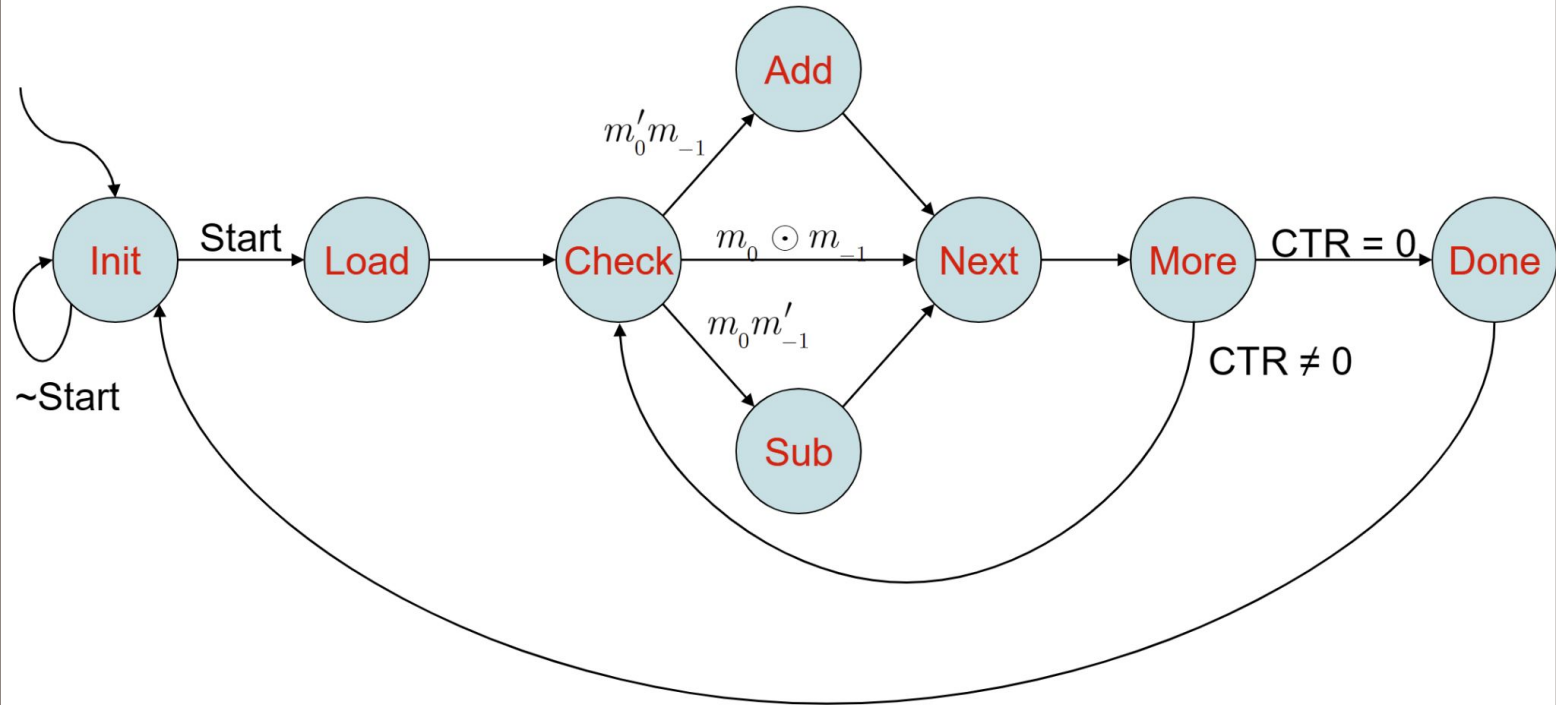

Use of 'signed' in Verilog

```
// Datapath State Update
wire signed[W:0] ZERO;           // (W+1)-bit 0 since `(W+1)'d0 does not work
assign ZERO = 'd0;
always @(posedge Clock)
  if (Reset)
    begin
      PM[WW+1:W+1] <= 'd0;
      PM[0] <= 0;
      CTR <= W;
    end
  else
    begin
      PM <=
        (M_LD ? $signed({ZERO, M, 1'b0}) : // Load M
         (P_LD ? $signed({PSgn, R, PM[W:0]}) : // Add/Sub
          (PM_ASR ? PM >>> 1 : // ASR
           PM // Unchanged
          )
         )
        );
      CTR <= CTR_DN ? CTR - 1 : CTR;
    end
end

// Datapath Output Logic
assign P = AllDone ? PM[WW:1] : 'd0;
endmodule // BoothMul
```

Telling Verilog to treat register as 2C value when doing arithmetic operations.

THE BITS OF THE REGISTER REMAIN UNCHANGED

NOTE: Only operation this pertains to is the arithmetic shifting (>>>)

NOTE: AddSub module does not care that the number is signed as it perform BITWISE operations

ModelSim Demo of Booth Mul

P7 Division

Division in P7


- Will NOT be covering in lecture
- Obtaining **Quotient MAGNITUDE** by repeatedly subtracting the **MAGNITUDE** of the **Divisor** from the **MAGNITUDE** of the **Dividend**
- **Quotient = # Subtraction performed**

| | |
|--------------|-------------------------------|
| | <i>Quotient</i> = 0 |
| $7 - 2 = 5$ | <i>Quotient</i> = $0 + 1 = 1$ |
| $5 - 2 = 3$ | <i>Quotient</i> = $1 + 1 = 2$ |
| $3 - 2 = 1$ | <i>Quotient</i> = $2 + 1 = 3$ |
| $1 - 2 = -1$ | Stop |

Quotient = $\frac{\text{Dividend}}{\text{Divisor}}$. For example $\frac{7}{2} = 3$, $\frac{-11}{5} = -2$, $\frac{-26}{-6} = 4$, and $\frac{15}{-3} = -5$


Obtaining Sign of Quotient

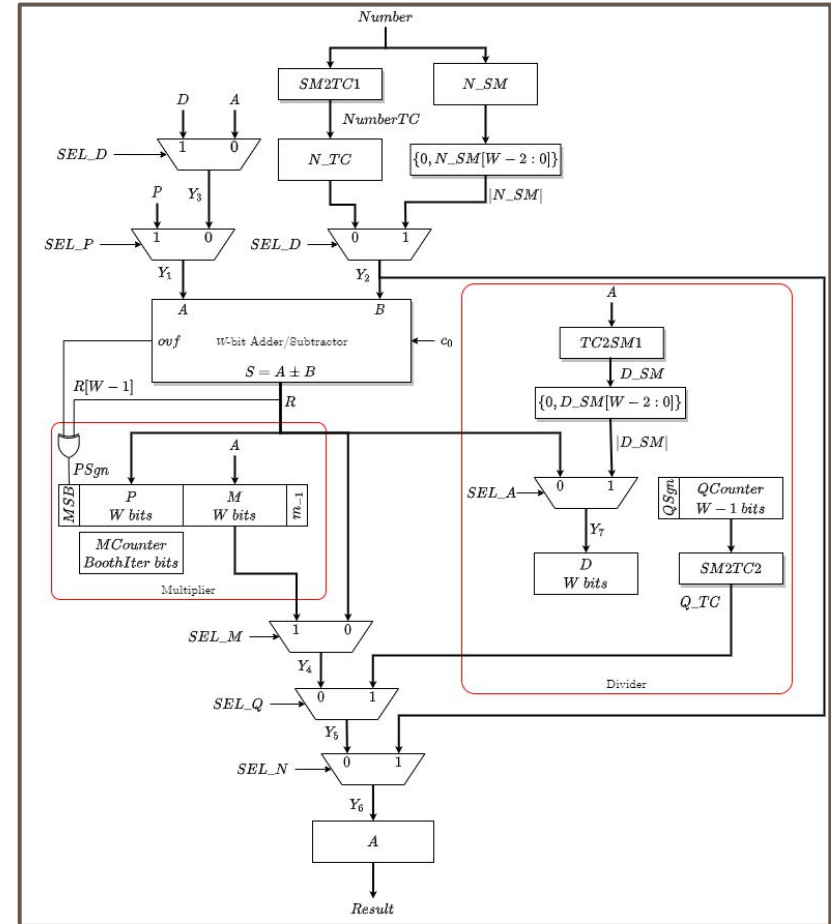- After obtaining magnitude of quotient, need to determine sign
- How can we do that?



Why Bother with Both N_SM and N_TC?

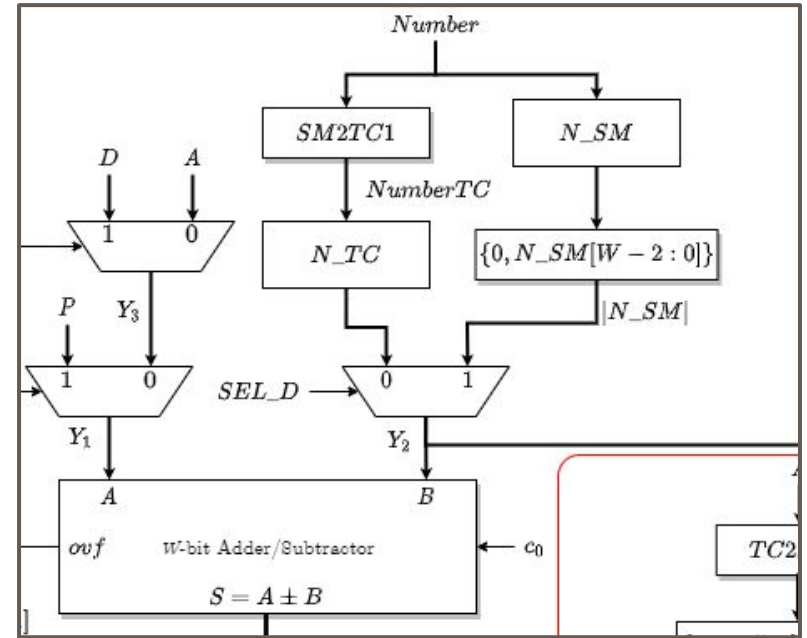- Why not just have one over the other?
- Are there benefits to having both?



THANK YOU

