

# EECS 270 W25

## Discussion 9

March 20th, 2025  
By: Mick Gordinier



## **AGENDA**

1. Recap of Discussion 8 & Project 5
2. Our Processor's Clock
3. Project 6 Overview
4. Team Project/Research!!!
5. Team Presentations

# Recap of Discussion 8 & Project 5

# Sequential Circuit Design Process

1. **Read the specs thoroughly to understand full behavior of system**
2. **BEFORE YOU START CODING ANYTHING, Construct:**
  - a. State assignment
  - b. State diagram
  - c. State / Transition / Output table(s)
3. **Generate logic equations for transition and output terms**
4. **THEN, start your coding in Verilog**



# UpDown Counter (Project 5) Recap

- Your first synchronous sequential circuit!
- Dealt with D Flip-Flops to handle synchronization
- Used the push button as our fake clock

# Our Processor's Clock
  
# Clock Within Our FPGAs

- Our FPGAs come with a built-in 50 MHz Oscillator clock that we can utilize



$$\begin{aligned}\text{Period (s)} &= 1 / f \\ &= 1 / (50 \text{ MHz}) \\ &= 1 / (50 * 10^6 \text{ Hz}) \\ &= ((0.02) * 10^{-6}) \text{ s} \\ &= (2 * 10^{-8}) \text{ s} \\ &= (20 * 10^{-9}) \text{ s} \\ &= \mathbf{20 \text{ ns}}\end{aligned}$$

# How to Interact with the 50 Mhz FPGA Clock

- Declare 'CLOCK\_50' as an input to your **Top-Level module**

```
module Project6
(
    input CLOCK_50,           // Clock
    input [17:0] SW,           // E =
    output [6:0] HEX7, HEX6, // Timer
    output [6:0] HEX3,         // ETL
    output [6:0] HEX2,         // NLTL
    output [6:0] HEX1,         // ELTL
    output [6:0] HEX0          // WTL
);

// Instantiate Clock_Div module

// Instantiate TLC module

endmodule // Project6
```




# Using Clock\_Div to Scale Down Clock

```
// Clock Divider by Powers of 2 (Table of frequ
module Clock_Div
  #(parameter SIZE = 36) // divides by 2^i f
  (
    input CLK_in,
    output [SIZE:0] CLKS_out
  );


  reg [SIZE:1] Counter;
  initial Counter = 'd0;

  always @(posedge CLK_in)
    Counter <= Counter + 1;

 
  assign CLKS_out = {Counter, CLK_in};
endmodule // Clock_Div
```



# Visualization on Clock\_Div Module


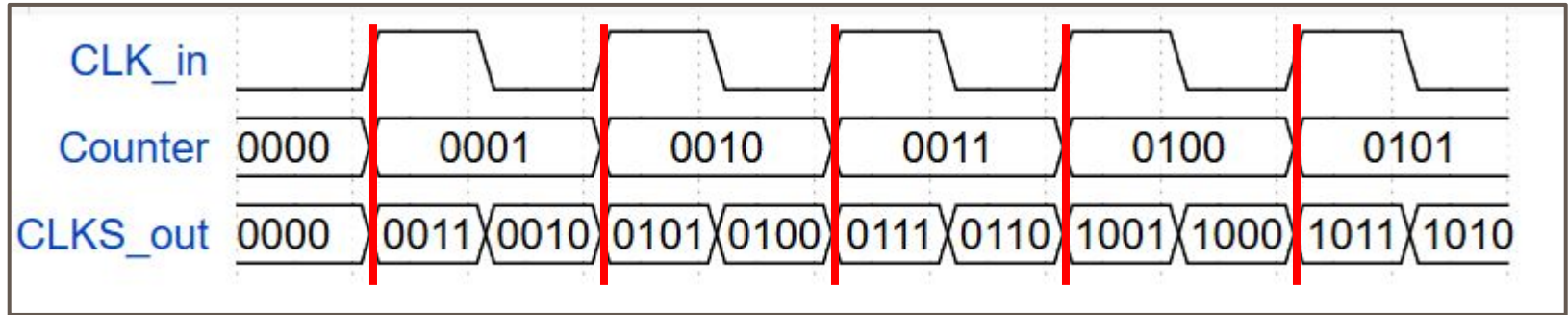

 
```
reg [SIZE:1] Counter;  
initial Counter = 'd0;  
  
always @(posedge CLK_in)  
    Counter <= Counter + 1;  
  
assign CLKS_out = {Counter, CLK_in};  
endmodule // Clock_Div
```



# Project 6 (Traffic Light Controller) Overview

# Project 6: Traffic Light Controller

 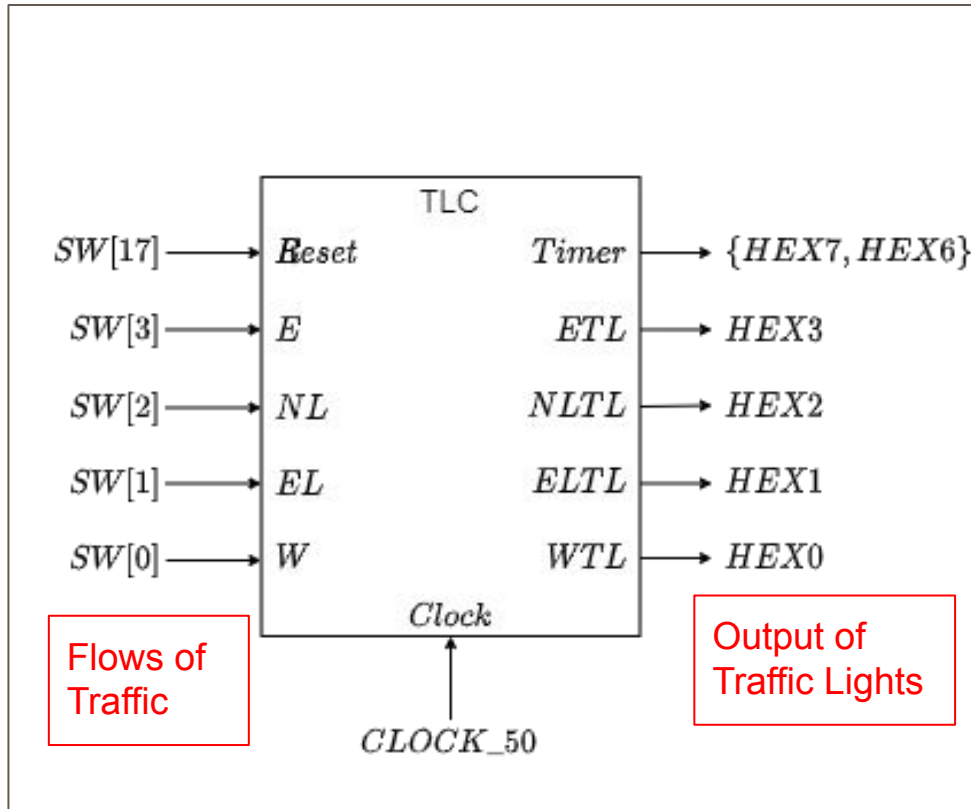

**FLOW A**  
**FLOW B**  
**FLOW C**

# Using the Clock for Project 6

**Rule #1:** A Green light should remain "Green" for intervals that are **multiples of 10 seconds**.


**Rule #5a:** When a light is to change from Green to Red, it **should be Yellow for exactly one second** in between the Green and Red.

**How can you ensure that a light stays on for 1 or 10 seconds using the 50 MHz Clock?**


**How much do you need to scale down the clock?**
 
# Are We Dealing with Moore/Mealy Outputs?


- **Moore Output:**  $\text{output} = g(\text{current state})$



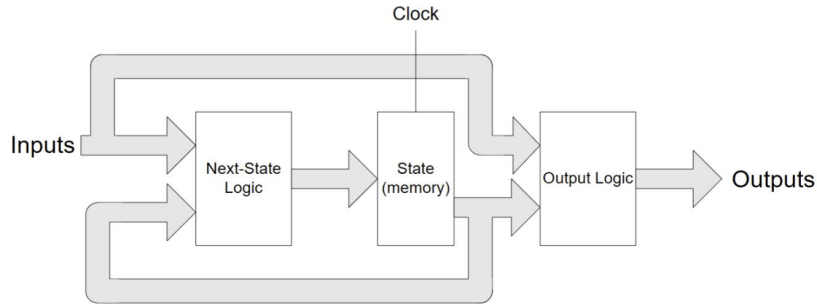- **Mealy Output:**  $\text{output} = g(\text{current state, inputs})$



## States vs. Outputs of TLC

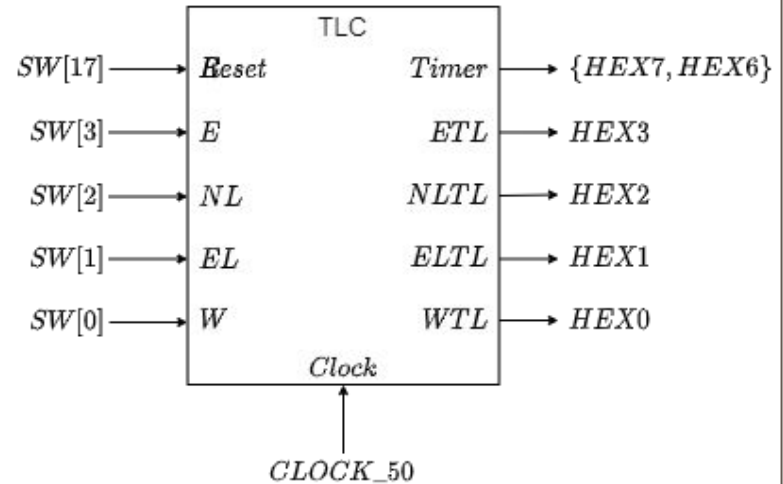

# Starvation and Fairness in Project 6

- Need to ensure there is **no starvation**
  - **What do we mean by starvation?**
  - **How can starvation occur in this project?**
- Would also like to provide some sort of fairness as well

# Starvation and Fairness in Project 6

- Need to ensure there is **no starvation**
  - **What do we mean by starvation?**
  - **How can starvation occur in this project?**
- Would also like to provide some sort of fairness as well

**FLOW A > FLOW B > FLOW C > FLOW A**



# Project 6: Traffic Light Controller

- **WARNING:** This project is extensive (Lots of specification to read)
  - Don't wait to start it to the last day (Pleaseeeeeeee)
- Please read the specification thoroughly
- Refer back to Modelsim tutorials from previous discussion to get better at making your testbenches

Team Project/Research!!!

# Team Project/Research

- **Everyone will be taking over discussion now!**
- Your job for the next 30-45 minutes
  1. Create groups of ~4-5 people (Come up with a team name)
  2. Choose one of the suggested projects/research to build/learn about
  3. Create a short presentation (5-minutes) of around 5-10 slides showcasing your work
- At the end, your group give your 5 minute presentation about the topic you worked on in front of the class

# Possible Team Projects Ideas

- Verilog Projects

- Ripple Counter
- Parallel Counter (w/ Optional Enable, Load, Reset)
- Johnson Counter (w/ Optional Enable, Load, Reset)
- Universal Shift Register
- Linear Feedback Shift Registers (LFSRs)
- Continuous 3/4-bit Stream Sequence Detector
- Continuous 4-bit Stream “Is One-Hot”
- Willing to consider any other reasonable synchronous, sequential project ideas!

- Possible Research / Talks

- The FPGA Design Flow (How does our Verilog code make it to the board?)
- Similarity/Difference/Pros/Cons of another HDL (VHDL, SystemVerilog, ...)
- Where are FPGAs used today in industry and why

# What I am Looking For in Your Project Presentation

- Description of what your project is about
  - What exactly is the behavior of your project?
  - What more could you add to your current implementation?
- Video/Live demonstration of LabsLand
  - **Use of a working clock and synchronous reset**
- (Optional) Clean ModelSim testing of many cases
  - Show snippets of your ModelSim output and label/point stuff out
- (Optional) Give quick related questions for class exercises
  - Ex. Given a counter in state XXXX, what will the next state be given X, X, and X

# What I am Looking For in Your Research Presentation

- Discussion of your research topic
  - The who and what of your research
  - Any history behind the topic of your research
  - Is the product still being used today (if so, how and where)
- **Use of big visuals, the less words on the slides the better**
- Ending slide that cites the main resources you used
  - Allows students (and myself) to learn more about the topic you presented!
- Time for Open-Discussion Topics / Q&A
  - Will be okay with extending 5-minute time to allow for open discussion

# Your Goal

- Make your presentation interesting and fun!!!
- Visuals, visuals, visuals
- Minimize words on your slides as much as possible
- Remember: You only have 5 minutes to present, so be smart about how you do it
  - Don't need to go too in-depth about your topic
  - Have your live demos ready to go, maybe do videos of your demo instead
  - If you have time for a quick Q&A, great!

# Team #1 (The Counters)

(Johnson Counter)

(People in Team)



# Team #2 (Dave)

(Is One-Hot)

(People in Team)

# Team #3 (Ripplers)

(Linear Shift Feedback Register)

(People in Team)

# Team #4 (270 Warriors)

(Universal Shift Register)

(People in Team)