

# EECS 270 W25


## Midterm II Exam Review

March 27th, 2025  
By: Mick Gordinier


 
# Midterm Exam Logistics (Date/Time)

- Midterm Exam Date/Time: **Tuesday April 1st, 6:00 - 8:00 PM**
  - **A - L: 220 CHRYS**
  - **M - R: 1010 DOW**
  - **S - V: 1017 DOW**
  - **W - Z: 1018 DOW**
- SSD Accommodations
  - **Tuesday April 1, 5:00 pm - 8:00 pm, EECS 270 Lab (2322 EECS)**
- Closed book except for **TWO 8.5"x11" sheet**
- No electronics



**DOUBLE CHECK THE CANVAS ANNOUNCEMENT TO CONFIRM / UPDATES**


# Midterm II Exam Logistics (Topics Covered)

1. Exam 1 Coverage (**Watch previous Midterm Review**)
2. Latches & Flip-Flops
3. Sequential Circuit Analysis / Design
4. Two Level Logic Minimization
5. Sequential Building Blocks (Counters/Shift Regs/...)
6. Register Transfer Logic (RTL) Design

Let's Get Started



 
# The 2 Types of Digital Logic Circuits (Combinational vs. Sequential)



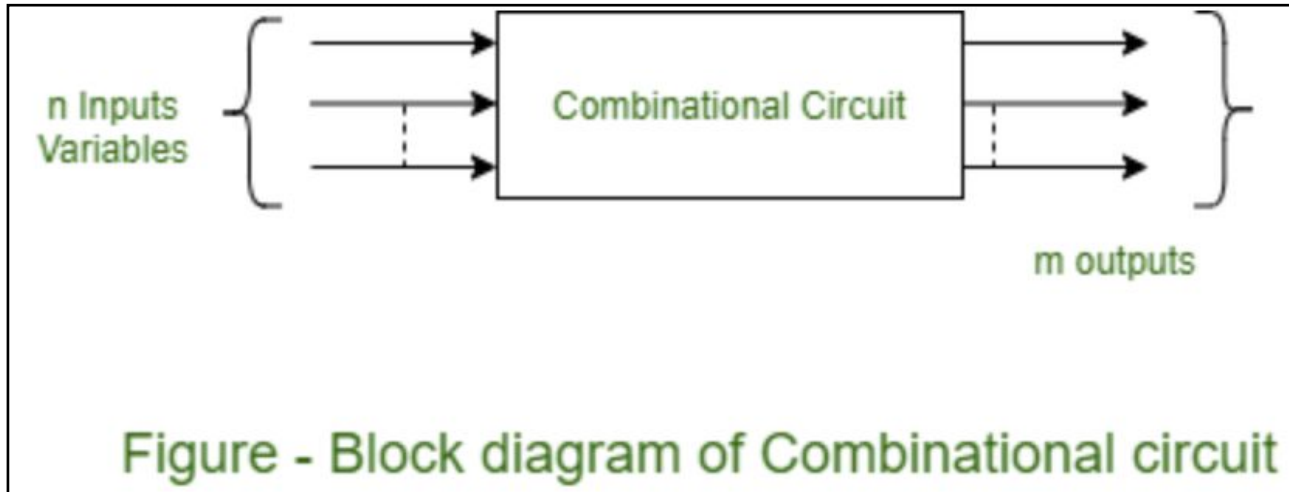
# Combinational Circuits Overview (Projects 1 - 4)

- Outputs depend ONLY on present combination of current inputs
- Stateless / No Memory
- Verilog 'assign' - Continuous assignment to a wire data type
- Verilog 'always @\*' - Procedural “combinational” block


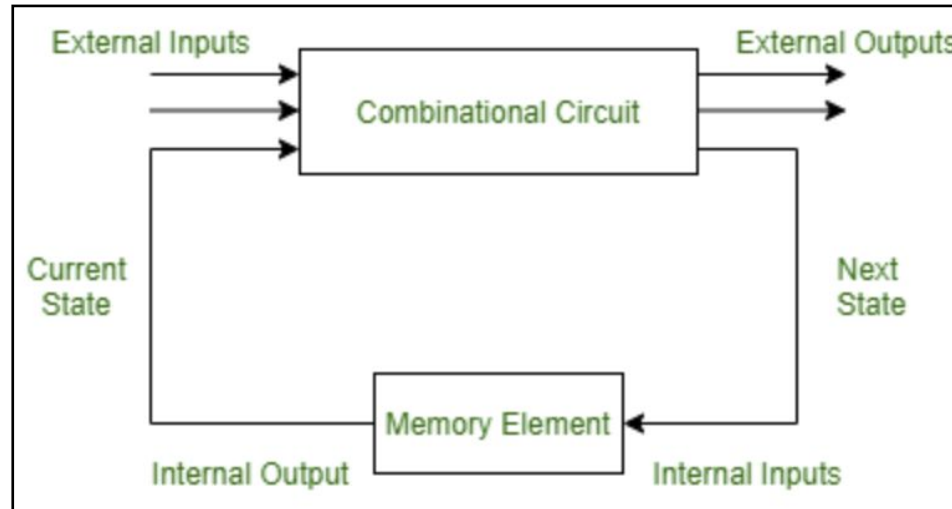
# Sequential Circuits Overview (Project 5 - 7)

- Combinational Circuit + **Memory Element**
- Outputs depend on present combination of inputs and current state
- Use of memory to store previous state/output




# Latches and Flip-Flops (The Memory Element)





 
# Latches Overview

- Basic type of memory storage unit
  - Used as temporary storage elements to store binary information
  - Can hold/store 1 bit of information
- **NO CLOCK === Asynchronous**
  - **Level-Sensitive Devices**
  - **Immediate changes to Output**




Great Visual Example of an SR Latch!!

# Viewing a Set-Reset (SR) Latch

 


S	R	Q	Q'	Name
0	0			
0	1			
1	0			
1	1			

# Viewing a Set-Reset (SR) Latch

 


S	R	Q	Q'	Name
0	0			
0	1			
1	0	1		
1	1			

# Viewing a Set-Reset (SR) Latch

 


S	R	Q	Q'	Name
0	0			
0	1			
1	0	1	0	
1	1			

# Viewing a Set-Reset (SR) Latch

 


S	R	Q	Q'	Name
0	0			
0	1			
1	0	1	0	SET
1	1			

# Viewing a Set-Reset (SR) Latch

 


S	R	Q	Q'	Name
0	0			
0	1	0		
1	0	1	0	SET
1	1			

# Viewing a Set-Reset (SR) Latch

 

S	R	Q	Q'	Name
0	0			
0	1	0	1	
1	0	1	0	SET
1	1			


# Viewing a Set-Reset (SR) Latch

 

S	R	Q	Q'	Name
0	0			
0	1	0	1	RESET
1	0	1	0	SET
1	1			




# Viewing a Set-Reset (SR) Latch

 


S	R	Q	Q'	Name
0	0	Q		
0	1	0	1	RESET
1	0	1	0	SET
1	1			

# Viewing a Set-Reset (SR) Latch

 


S	R	Q	Q'	Name
0	0	<b>Q</b>	<b>Q'</b>	
0	1	<b>0</b>	<b>1</b>	<b>RESET</b>
1	0	<b>1</b>	<b>0</b>	<b>SET</b>
1	1			

# Viewing a Set-Reset (SR) Latch

 


S	R	Q	Q'	Name
0	0	Q	Q'	HOLD
0	1	0	1	RESET
1	0	1	0	SET
1	1			

# Viewing a Set-Reset (SR) Latch

 


S	R	Q	Q'	Name
0	0	Q	Q'	HOLD
0	1	0	1	RESET
1	0	1	0	SET
1	1	0		

# Viewing a Set-Reset (SR) Latch

 

S	R	Q	Q'	Name
0	0	Q	Q'	HOLD
0	1	0	1	RESET
1	0	1	0	SET
1	1	0	0	


# Viewing a Set-Reset (SR) Latch

 

S	R	Q	Q'	Name
0	0	Q	Q'	HOLD
0	1	0	1	RESET
1	0	1	0	SET
1	1	0	0	INVALID
 
# Overall Notes about Set-Reset (SR) Latches

- Simplest form of a latch
  - 2-inputs: Set (S) and Reset (R)
  - + Can now hold a value! (When Set and Reset = 0)
- Forms the basic building blocks of all other types of flip-flops
- ISSUE: Has an “Invalid” state




S	R	Q	Q'	Name
0	0	Q	Q'	HOLD
0	1	0	1	RESET
1	0	1	0	SET
1	1	0	0	INVALID

# Bonus: Building an SR Latch in Verilog

```
module SR_Latch_Assign (  
    input set, reset,  
    output Q, Q_not);  
  
    assign Q = ~(reset | Q_not);  
    assign Q_not = ~(set | Q);  
endmodule
```


Level-Sensitive (Asynchronous)!

```
module SR_Latch_Procedural (  
    input set, reset,  
    output reg Q, Q_not);  
  
    always @(*) begin  
        Q = ~(reset | Q_not);  
        Q_not = ~(set | Q);  
    end  
endmodule
```

 


 
# Bonus: Viewing SR Latch Invalid Behavior!




**Invalid State**  
 $(S, R) = (0, 0)$   
 $\rightarrow (Q, Q') = (0, 0)$

**Hold State**  
 $(S, R) = (0, 0)$   
 $\rightarrow (Q, Q') = \text{OSCILLATION}$

```
module SR_TestBench;  
  reg set, reset;  
  wire Q, Q_not;  
  
  SR_Latch_Assign a(set, reset, Q, Q_not);  
  
  initial begin  
    set = 1'b0; reset = 1'b0; #1;  
    set = 1'b1; #5;  
    reset = 1'b1; #5;  
    set = 1'b0; reset = 1'b0;  
  end  
endmodule
```

```
module SR_Latch_Assign (  
  input set, reset,  
  output Q, Q_not  
);  
  
  assign #1 Q = ~(reset | Q_not);  
  assign #1 Q_not = ~(set | Q);  
endmodule
```


# Moving on to Data (D) Latches

 

D	S	R	Q	Q'	Name
0					
1					




## Moving on to Data (D) Latches

 

D	S	R	Q	Q'	Name
0	0	1	0	1	RESET
1					


## Moving on to Data (D) Latches

 

D	S	R	Q	Q'	Name
0	0	1	0	1	RESET
1	1	0	1	0	SET

What's Good/Bad about D-Latches?


# Moving on to Data (D) Latches

 

D	S	R	Q	Q'	Name
0	0	1	0	1	RESET
1	1	0	1	0	SET

- + No more Invalid State :D
- BUT NO MORE HOLD STATE :O
- → Has no state (Not sequential)

 
## BONUS: JK-Latches (There are many different latches)



SR Latch

J	K	Q	Q'	Name
0	0			
0	1			
1	0			
1	1			
 
## BONUS: JK-Latches (There are many different latches)




SR Latch

J	K	Q	Q'	Name
0	0	Q	Q'	HOLD
0	1	0	1	RESET
1	0	1	0	SET
1	1	Q'	Q	Toggle
 
# (Positive) Enabled Level-Sensitive D-Latch

- Use of a Enable (“Clock”) **(BUT STILL NOT SYNCHRONOUS)**
- Whenever C is high  $\rightarrow Q = D$  (Level-Sensitive to D) **(Set/Reset)**
- Whenever C is low  $\rightarrow Q$  holds **(Hold)**






C	D	S	R	Q	QB	Name
0	0	0	0	Q	QB	HOLD
0	1	0	0	Q	QB	HOLD
1	0	0	1	0	1	RESET
1	1	1	0	1	0	SET


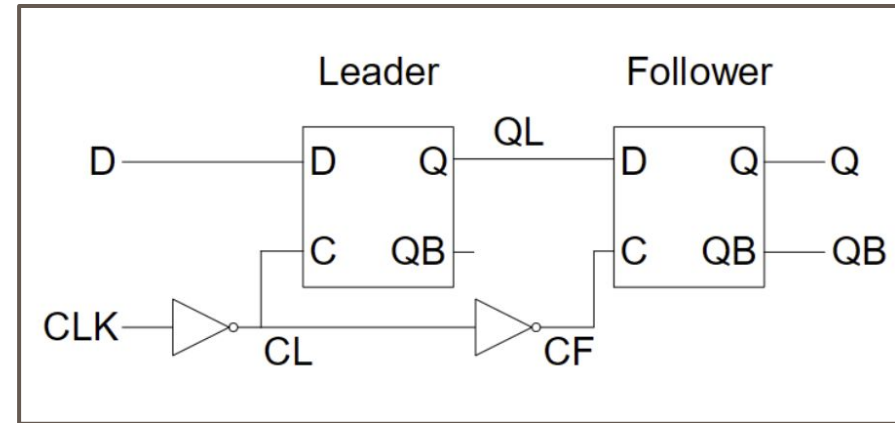 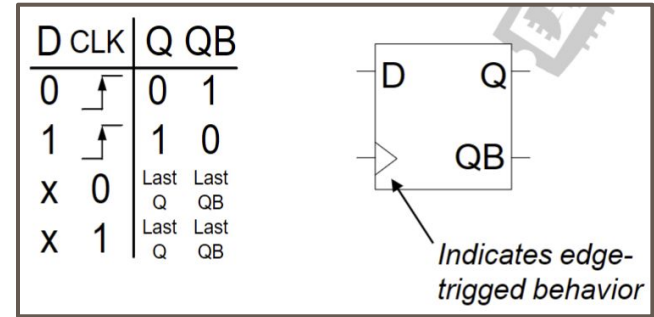
# Asynchronous vs. Synchronous in Logic Design

- Asynchronous Circuits
  - Circuit operates without a clock signal
- Synchronous Circuits
  - Samples inputs only once per clock cycle





Level-Sensitive Asynchronous D-Latch


Edge-Triggered Synchronous D Flip-Flop

# (Positive) Edge-Triggered D Flip-Flop Timing

- When CLK is Low → **Leader is open & Follower is closed**
  - D will be able to affect QL
  - QL WILL NOT be able to affect Q
- When CLK is High → **Leader is closed & Follower is open**
  - D WILL NOT be able to affect QL
  - QL can now affect Q

+ **Clocks D on positive edge of CLK**

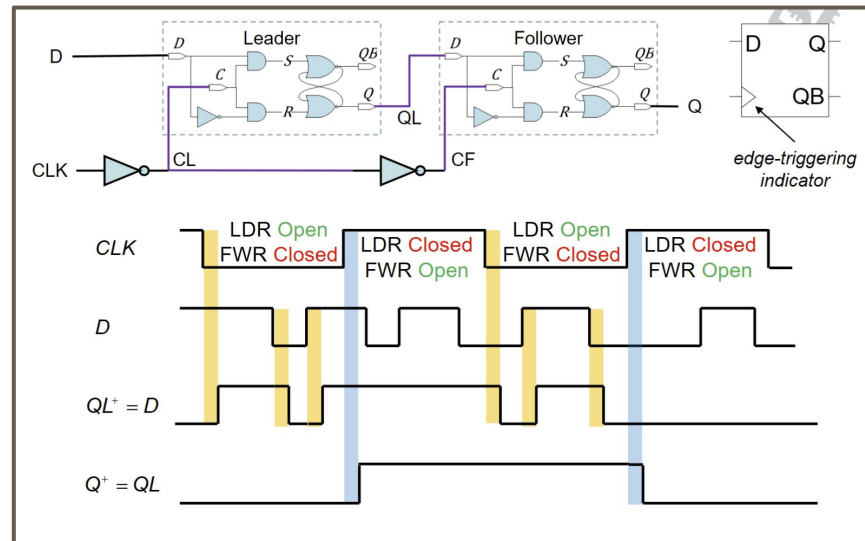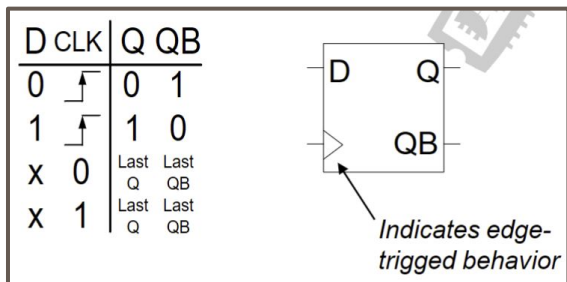

 

# Designing Sequential Circuits (Finite State Machines)

# Finite State Machines Overview



- Mathematical model of *sequential* behavior
- Applications: hardware, software, protocols, etc.
- Specified by two functions:


Next State:  $X^+ = f(X, Y)$

Output:  $Z = g(X)$  or  $g(X, Y)$

where


- $X$  and  $X^+$  are current and next *state* variables
- $Y$  are *input* variables
- $Z$  are *output* variables
- A *state* is a complete assignment to (valuation of) the state variables  $X$
- Next State function specifies the *transitions* between states
- Output function specifies the *observable* outputs of the state machine
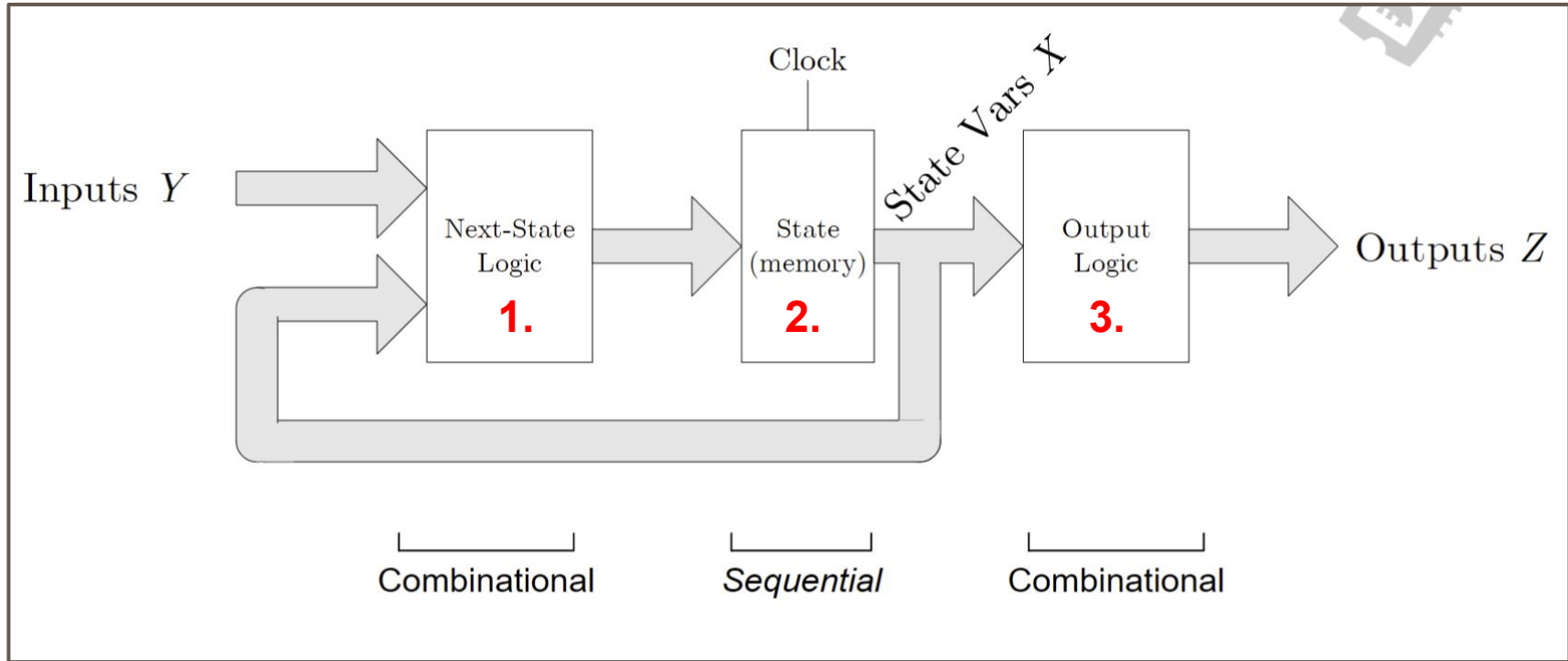
# The 3 Main Components of Sequential Circuits


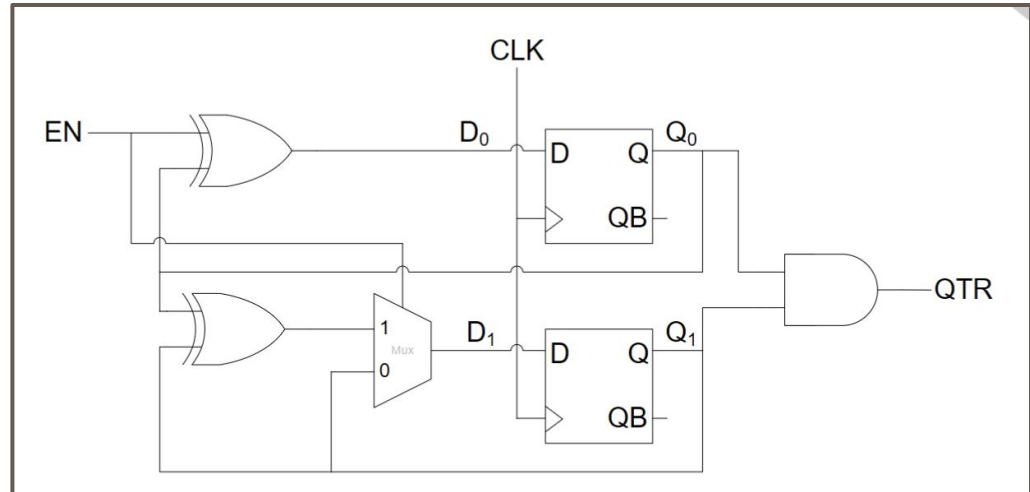
# Component 1. Next State Logic (Combinational)

- Combinationally determining the **next state** = **f(current state, current inputs)**
- Generating excitation equation (Equations for next state D)
- Create excitation equations for the circuit below




# Component 1. Next State Logic (Combinational)

- **Combinationally** determining the next state =  $f(\text{current state, current inputs})$
- Generating excitation equation (Equations for next state D)

$$D_0 = EN \text{ XOR } Q_0$$
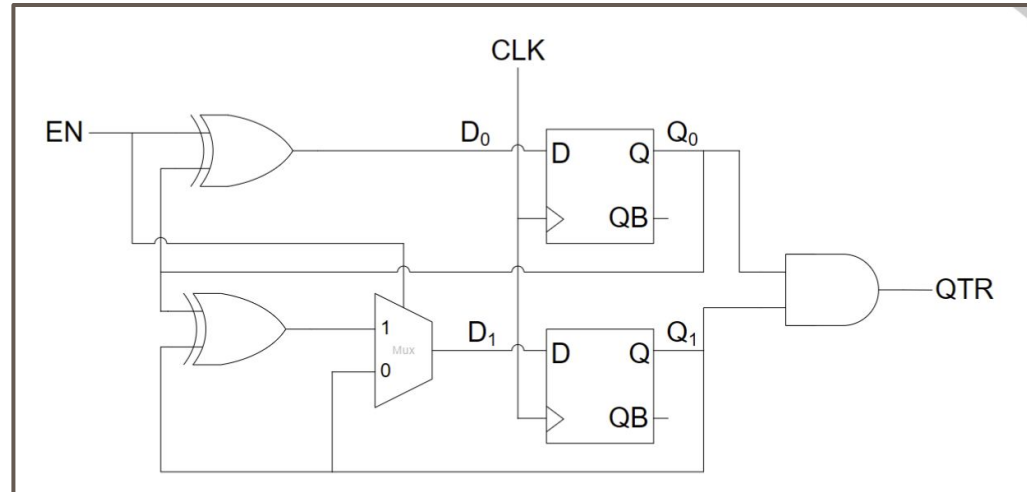
$$D_1 = EN * (Q_0 \text{ XOR } Q_1) + (EN' * Q_1)$$




## Component 2. Memory Logic (Sequential)

- **Sequentially** storing the new state (Generating Transition Equations)
- **NOTE:** This logic should be very minimal
  - In our designs in 270, we treat transition equations = excitation equations

$$Q_0^+ \leq D_0 = EN \text{ XOR } Q_0$$

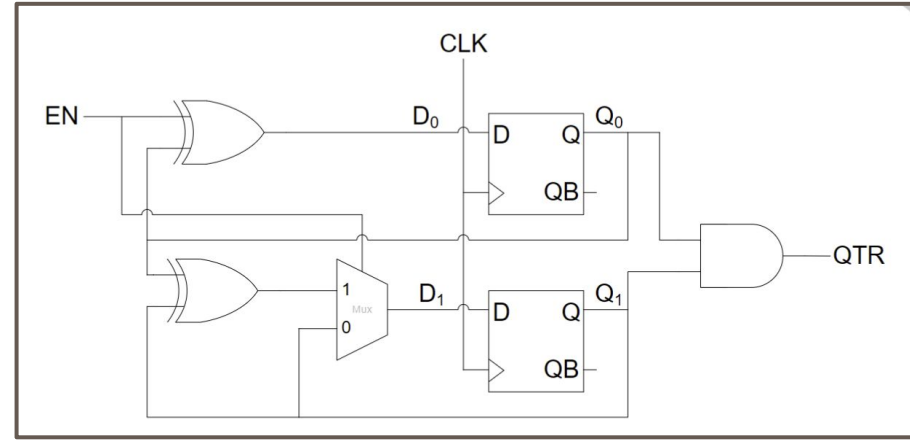
$$Q_1^+ \leq D_1 = EN * (Q_0 \text{ XOR } Q_1) + (EN' * Q_1)$$




 
## Component 3. Output Logic (Combinational)

- **Combinationally** determining the outputs (Generating Output Equations)
- **Is our circuit a moore or a mealy machine?**



# Moore vs. Mealy Machine??

- What do we mean when we call something a Moore/Mealy Machine?



# Moore vs. Mealy Machine??

- Defining how the outputs are determined in our machine
- What's the difference between a Moore and Mealy machine?

# Moore vs. Mealy Machine??


- Defining how the outputs are determined in our machine
- Moore Machine - Outputs can be determine from just the current state of our system
- Mealy Machine - Outputs are determined by both the current state **and current combination of inputs into the system**

# Moore vs. Mealy Machine??

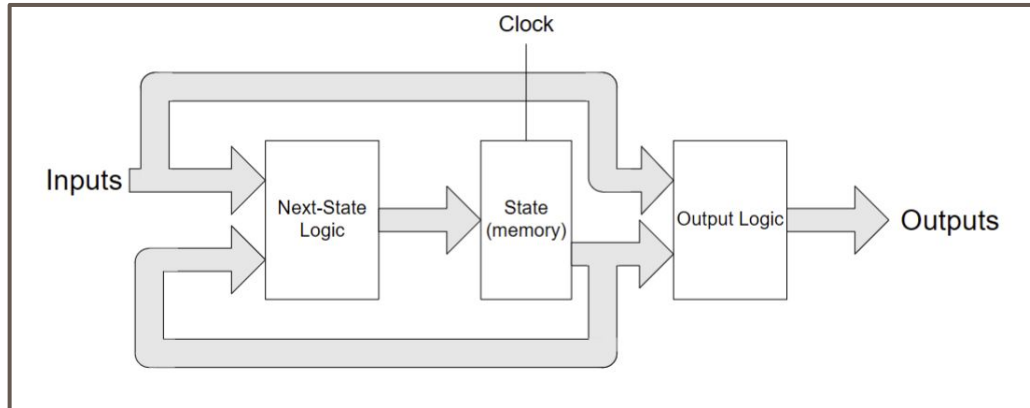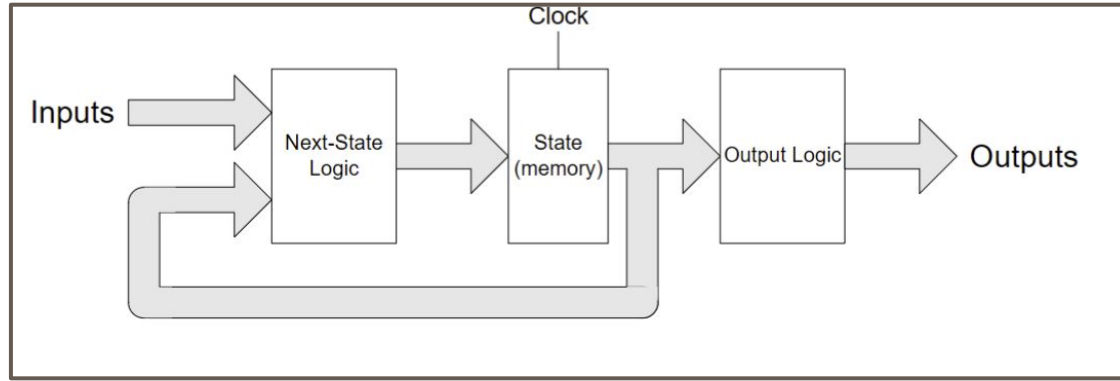

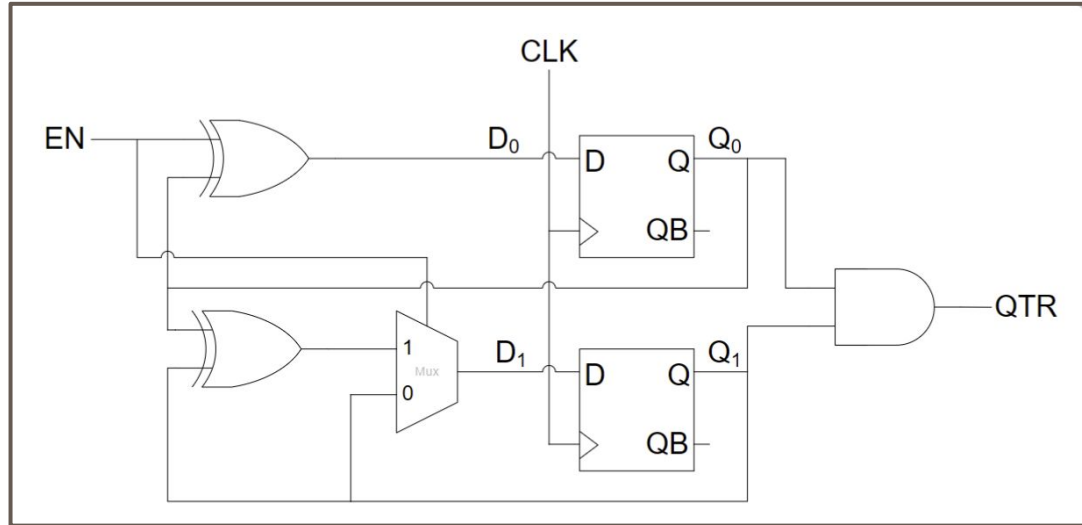
## Component 3. Output Logic (Combinational)

- **Combinationally** determining the outputs (Generating Output Equations)
- **Is our circuit a moore or a mealy machine?**


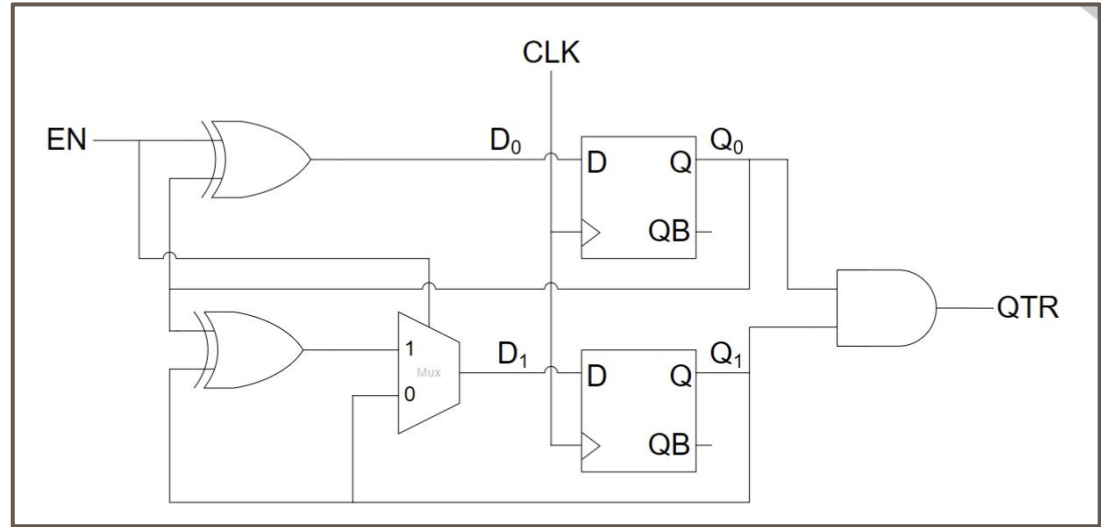
## Component 3. Output Logic (Combinational)


- **Combinationally** determining the outputs (Generating Output Equations)
- **Moore Machine - Output QTR only dependent on current state Q**



## Component 3. Output Logic (Combinational)


- **Combinationally** determining the outputs (Generating Output Equations)
- **Moore Machine - Output QTR only dependent on current state Q**

$$QTR = Q_0 \& Q_1$$

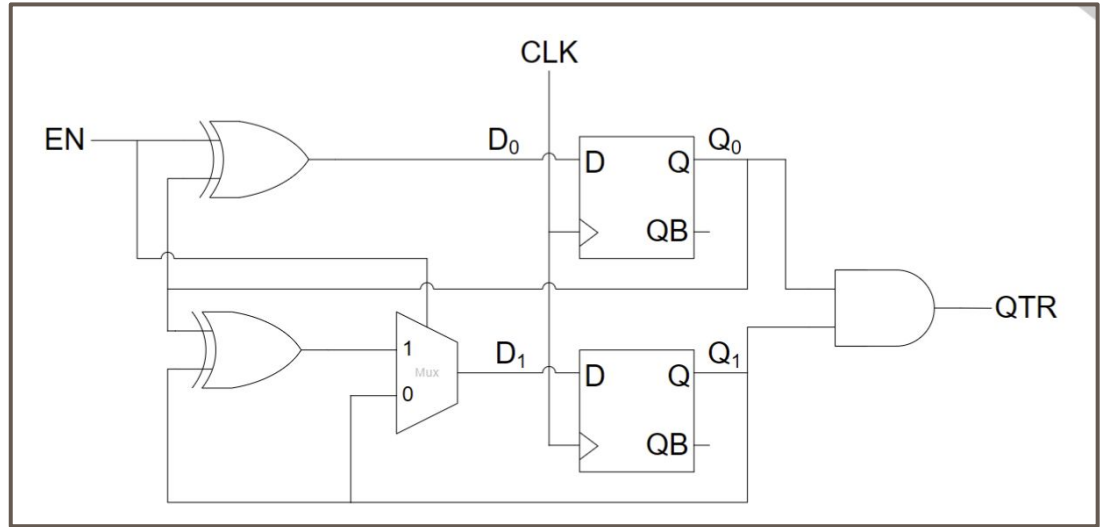


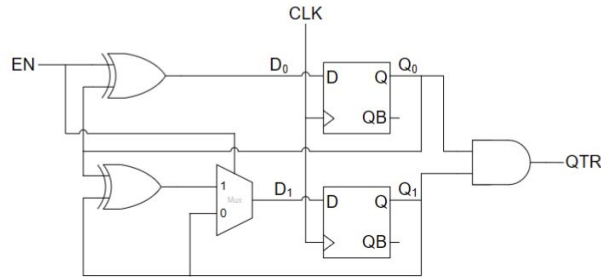
# Putting it all together (From Circuit → Tables/Equations)



*Transition Equations:*

$$Q_0^+ = D_0 = EN \oplus Q_0$$

$$Q_1^+ = D_1 = EN \cdot (Q_0 \oplus Q_1) + \overline{EN} \cdot Q_1$$

*Output Equation:*

$$QTR = Q_0 \cdot Q_1$$

*Transition/Output Table:*

current state		input		output
		EN		
Q <sub>1</sub>	Q <sub>0</sub>	0	1	QTR
0	0	00	01	0
0	1	01	10	0
1	0	10	11	0
1	1	11	00	1
		$\overline{Q_1^+} \quad Q_0^+$		
		next state		

# State Assignment

Creating a one-to-one mapping from state encoding to state names


$Q_1$	$Q_0$	State name
0	0	A
0	1	B
1	0	C
1	1	D

*Transition/Output Table:*

$Q_1$	$Q_0$	EN		QTR
		0	1	
0	0	00	01	0
0	1	01	10	0
1	0	10	11	0
1	1	11	00	1
$Q_1^+ Q_0^+$				

*State Assignments*

$Q_1$	$Q_0$	State name
0	0	A
0	1	B
1	0	C
1	1	D



?

# Moving from V1 $\rightarrow$ V2 (State Labelling)

$Q_1$	$Q_0$	State name
0	0	A
0	1	B
1	0	C
1	1	D

*Transition/Output Table:*

$Q_1$	$Q_0$	EN		QTR
		0	1	
0	0	00	01	0
0	1	01	10	0
1	0	10	11	0
1	1	11	00	1
		$Q_1^+$	$Q_0^+$	

*State Assignments*

$Q_1$	$Q_0$	State name
0	0	A
0	1	B
1	0	C
1	1	D

*State/Output Table:*

S	EN		QTR
	0	1	
A	A	B	0
B	B	C	0
C	C	D	0
D	D	A	1
			$S^+$

# Creating State Diagram

S	EN		QTR
	0	1	
A	A	B	0
B	B	C	0
C	C	D	0
D	D	A	1


$S^+$

What would the state diagram look like?

# Creating State Diagram

S	EN		QTR
	0	1	
A	A	B	0
B	B	C	0
C	C	D	0
D	D	A	1


            
 $S^+$

 


# Creating State Diagram

S	EN		QTR
	0	1	
A	A	B	0
B	B	C	0
C	C	D	0
D	D	A	1

$S^+$

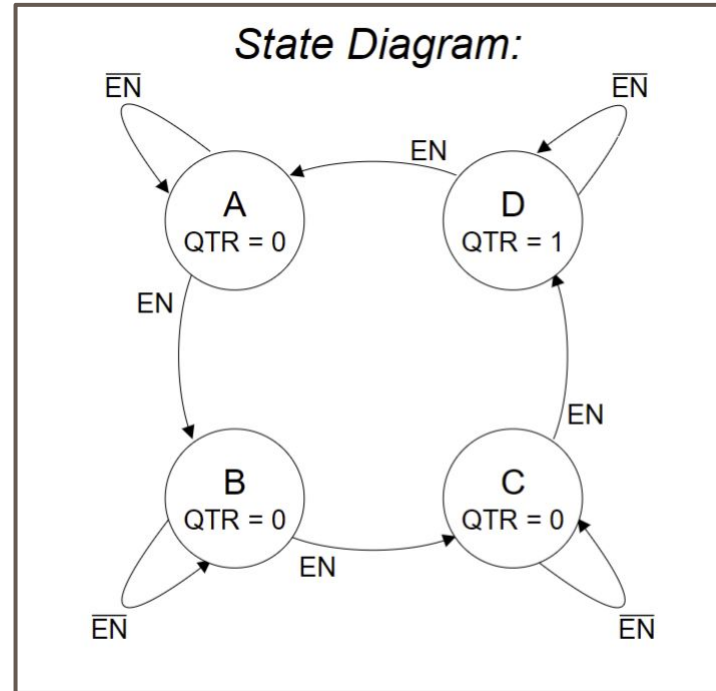

# Common Sequential Building Blocks

 

# Common Sequential Building Blocks Overview

- Registers
- Counters
  - Ripple Counter
  - Parallel Count
- Shift Registers
  - Parallel Shift Registers
  - Universal Shift Registers
- Shift Register Counters
  - Ring Counter
  - Johnson Counter
  - Linear Feedback Shift Registers





# Registers



- Collection of D Flip-Flops
- All share a common clock
- **Used to store collection of bits**

**always @(posedge clk) begin**

**if (EN) Q <= D**

**Else   Q <= Q**

**end**

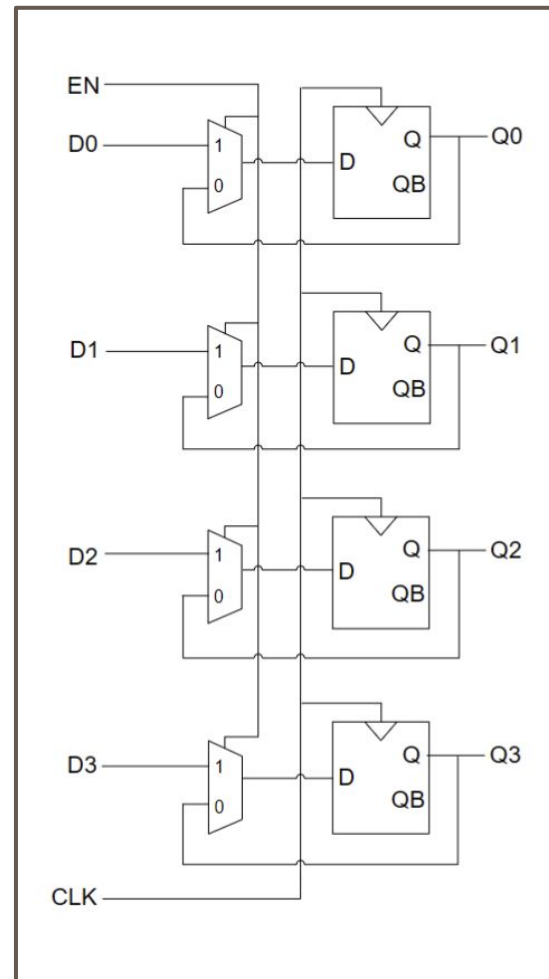 

# Modulo Counter

- No real physical counters are infinite
- Typically count through a series of finite states, then repeats
- Modulus - Number of states in counter's sequence

Ex. Counter Sequence =  $\{1, 2, 3, 4, 5, 6, 1, \dots\} \rightarrow$

Ex. Counter Sequence =  $\{5, 7, 2, 1, 6, 4, 5, \dots\} \rightarrow$

# Modulo Counter

- No real physical counters are infinite
- Typically count through a series of finite states, then repeats
- Modulus - Number of states in counter's sequence

Ex. Counter Sequence =  $\{1, 2, 3, 4, 5, 6, 1, \dots\} \rightarrow$  **Modulus = 6**

Ex. Counter Sequence =  $\{5, 7, 2, 1, 6, 4, 5, \dots\} \rightarrow$

# Modulo Counter

- No real physical counters are infinite
- Typically count through a series of finite states, then repeats
- Modulus - Number of states in counter's sequence


Ex. Counter Sequence =  $\{1, 2, 3, 4, 5, 6, 1, \dots\} \rightarrow \text{Modulus} = 6$

Ex. Counter Sequence =  $\{5, 7, 2, 1, 6, 4, 5, \dots\} \rightarrow \text{Modulus} = 6!!$

**BOTH HAVE THE SAME AMOUNT OF UNIQUE STATES**

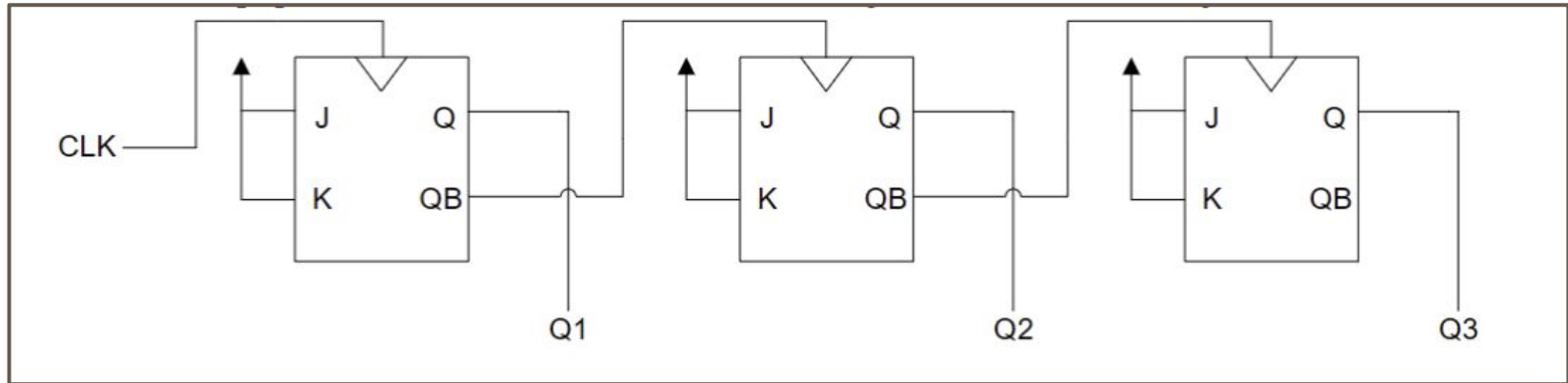
# Ripple Counters (An Implementation of a Modulo Counter)

- What are the states of the counter below? What is the counter's modulus?
  - HINT: You can assume we start at state  $(Q_3, Q_2, Q_1) = (0, 0, 0)$
  - HINT:  $Q_1$  represents the LSD of the number  $\{Q_3, Q_2, Q_1\}$
  - HINT: When using JK Flip-Flops, **If  $(J, K) == (1, 1) \rightarrow Q \leftrightarrow QB$  (Toggle Q)**



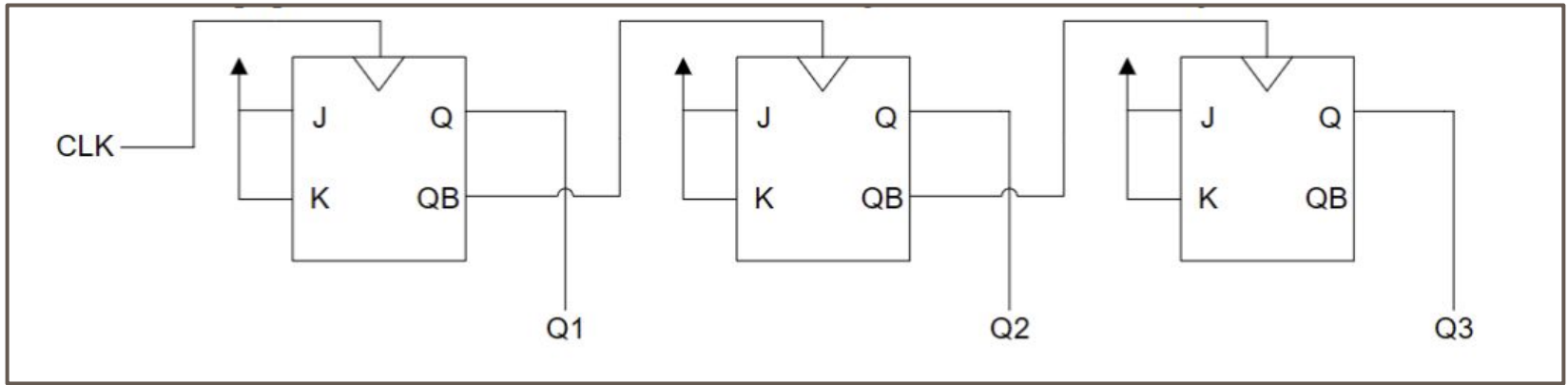
# Ripple Counters (An Implementation of a Modulo Counter)

- Unique States of Counter =  $\{0, 1, 2, 3, 4, 5, 6, 7, 0, \dots\} \rightarrow \text{Modulus} = 8$
- What are the Pros/Cons of using this method?


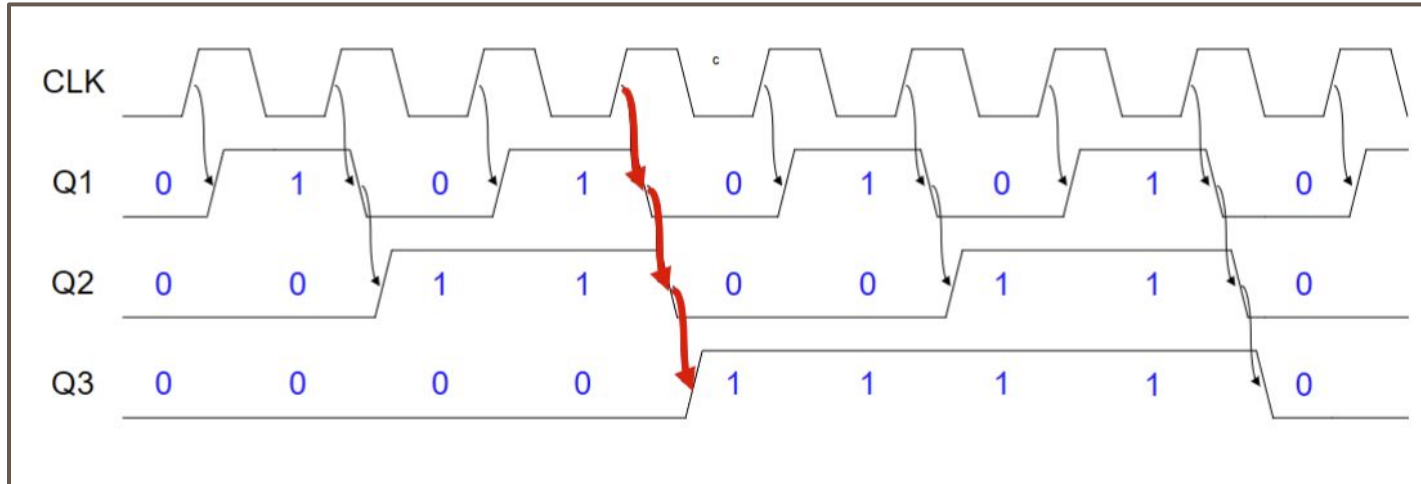
# Ripple Counters (An Implementation of a Modulo Counter)

- Unique States of Counter =  $\{0, 1, 2, 3, 4, 5, 6, 7, 0, \dots\} \rightarrow \text{Modulus} = 8$
- + **Very straightforward approach of a modulo counter**
- **State needs to ripple through the circuit**
  - **Output doesn't change at the same time**



# Parallel Counters (Better Modulo Counter Implementation)

- + Outputs are seen right after posedge clk
  - + No more ripple
- + Able to do Enable, Load, and Reset
- + **Can create unique modulus/states combos**

**always @(posedge clk) begin**

**If (RESET) Q <= 0**


**If (LOAD) Q <= {L3, L2, L1, L0}**

**If (EN) Q <= {Q+1}**

**Else Q <= Q**

**end**

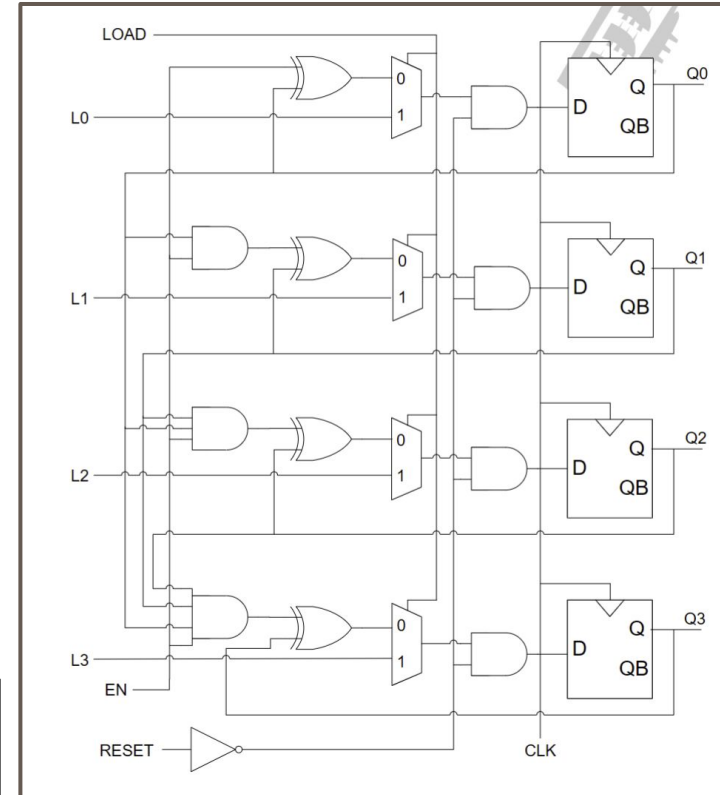**Note: If going through all states, will automatically handle the modulus**







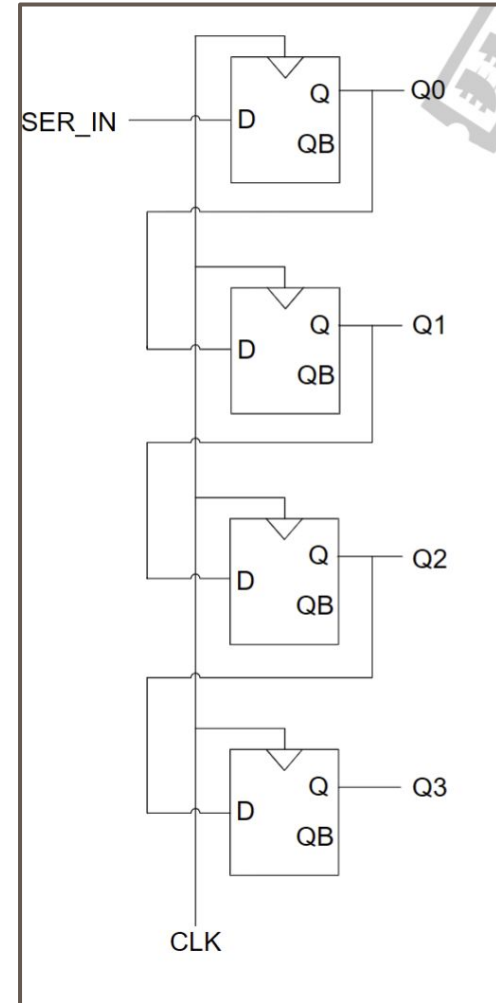  
# Shift Registers (Serial-In)

- Allowing the bits to be shifted left by one
- Specify “Serial In” bit to put in place for new Q0
- + NOTE: NOT A RIPPLE. Shifting is synchronous w/ CLK

```
always @(posedge clk) begin
    Q <= {Q2, Q1, Q0, Serial_In};
end
```



# Shift Registers (Parallel-In)


- Giving the ability to load all register bits on CLK
- **Serial-In Shift Register + Load logic**

**always @(posedge clk) begin**

**If (LOAD) Q <= {L3, L2, L1, L0};**

**Else       Q <= {Q2, Q1, Q0, Serial\_In};**

**end**

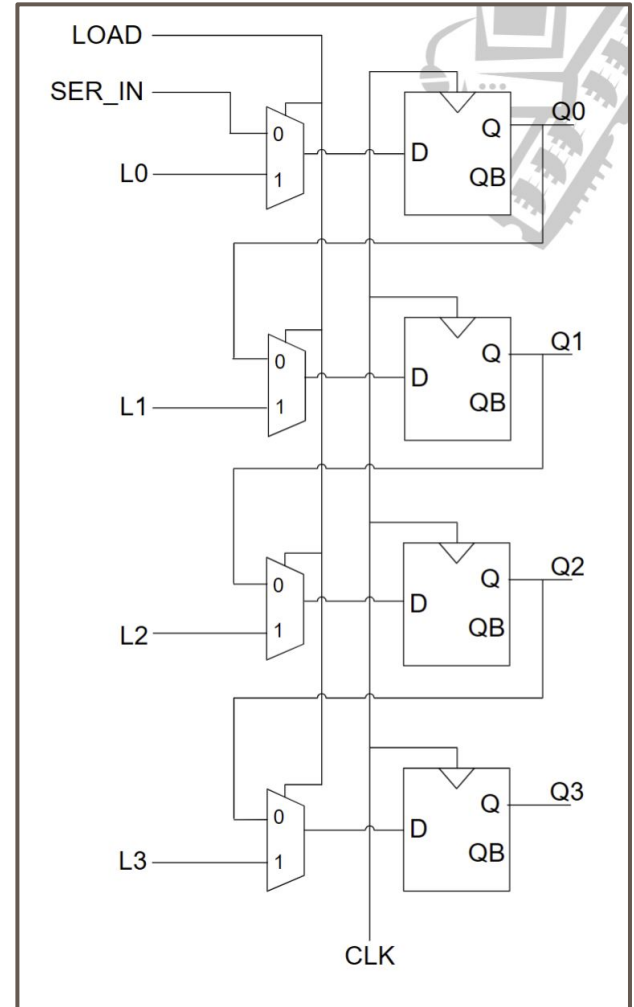

# Universal Shift Registers

- **Shift register that can**

- **Parallel Load**
- **Hold**
- **Shift Left**
- **Shift Right**

**always @(posedge clk) begin**


**If (MODE == LOAD) Q <= {L3, L2, L1, L0};**

**If (MODE == HOLD) Q <= Q;**

**If (MODE == SL)     Q <= {Q2, Q1, Q0, S\_In\_L};**

**If (MODE == SR)     Q <= {S\_In\_R, Q3, Q2, Q1};**

**end**

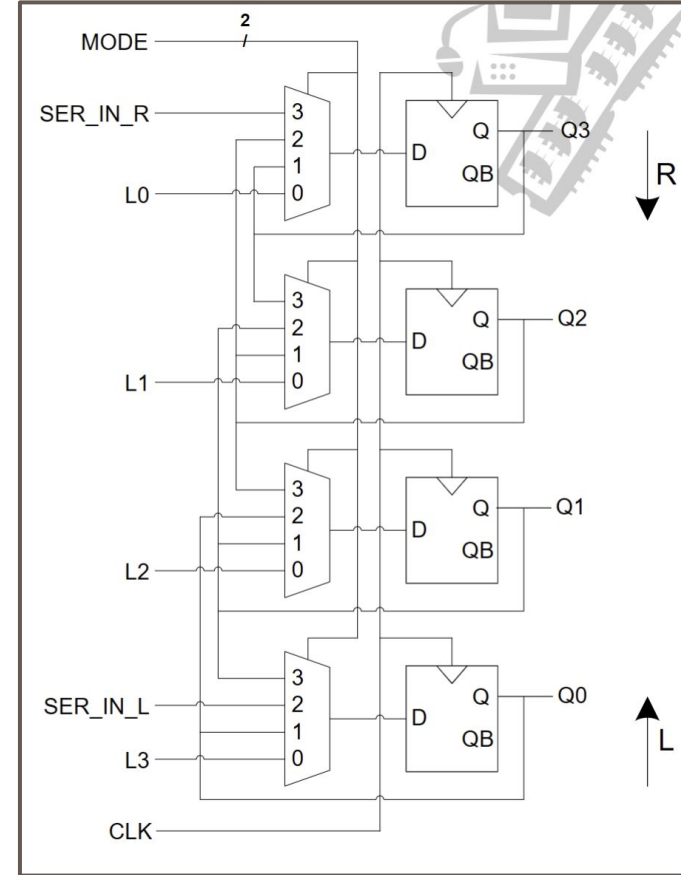


# Ring Counter

- Each Flip Flop value propagates down the chain
- One-hot encoding scheme
- Check which Flip-Flop is high to find the count number

```
always @(posedge clk) begin
    If (RESET) Q <= 4'b0001;
    Else      Q <= {Q[2:0], Q3};
end
```

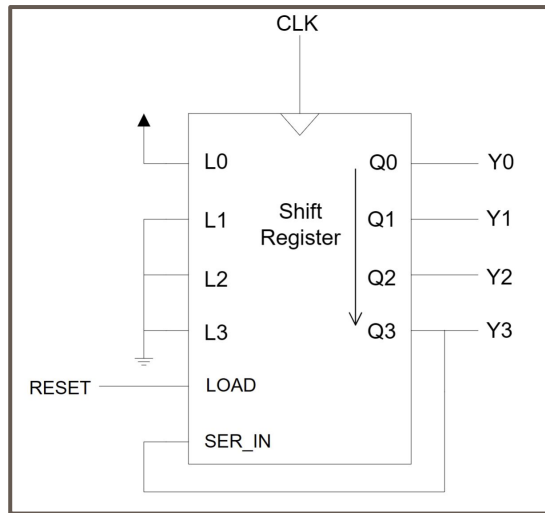- How many states exist in an n-bit ring counter?



Straight ring counter				
State	Q0	Q1	Q2	Q3
0	1	0	0	0
1	0	1	0	0
2	0	0	1	0
3	0	0	0	1
0	1	0	0	0
1	0	1	0	0
2	0	0	1	0
3	0	0	0	1
0	1	0	0	0

# Johnson Counter



- Very similar to a ring counter
- **MSB is inverted and chained to the first input**


always @(posedge clk) begin

  If (RESET) Q <= 4'b0000;

  Else       Q <= {Q[2:0], ~Q3};

end

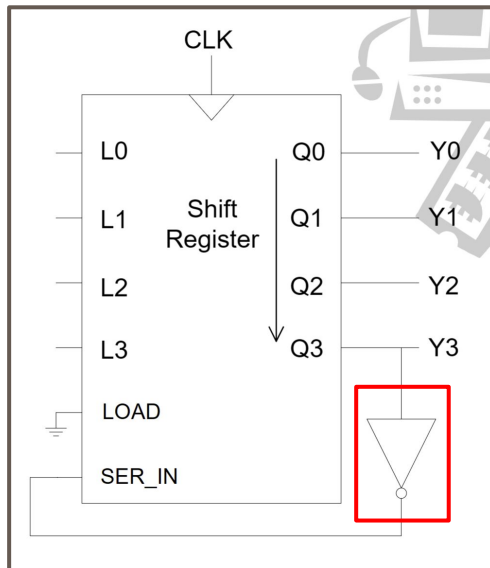
- **How many states exist in an n-bit Johnson counter?**



Johnson counter				
State	Q0	Q1	Q2	Q3
0	0	0	0	0
1	1	0	0	0
2	1	1	0	0
3	1	1	1	0
4	1	1	1	1
5	0	1	1	1
6	0	0	1	1
7	0	0	0	1
0	0	0	0	0
 
# Linear Feedback Shift Registers

- Modification of ring counter
- First input is a function of LFSR value
- **Can cover  $2^n - 1$  states!**



LFSR Example				
State	Q0	Q1	Q2	Q3
0	0	0	0	0
1	1	0	0	0
2	0	1	0	0
3	1	0	1	0
4	1	1	0	1
5	1	1	1	0
6	1	1	1	1
7	0	1	1	1
0	1	0	1	1

# Register Transfer Level (RTL) Design




# RTL Design Overview

- Splitting up design in Controller and Datapath
- **Controller** - Controls and orchestrates the Datapath operations
- **Datapath** - Computation on the signals
  - Arithmetic - Add/Subtract/Multiple/Count/...
  - Logical - Shift Left / Shift Right / Arithmetic Shift / bitwise Ops
  - Other - Clear / Load / Hold





# RTL Sequential Circuit

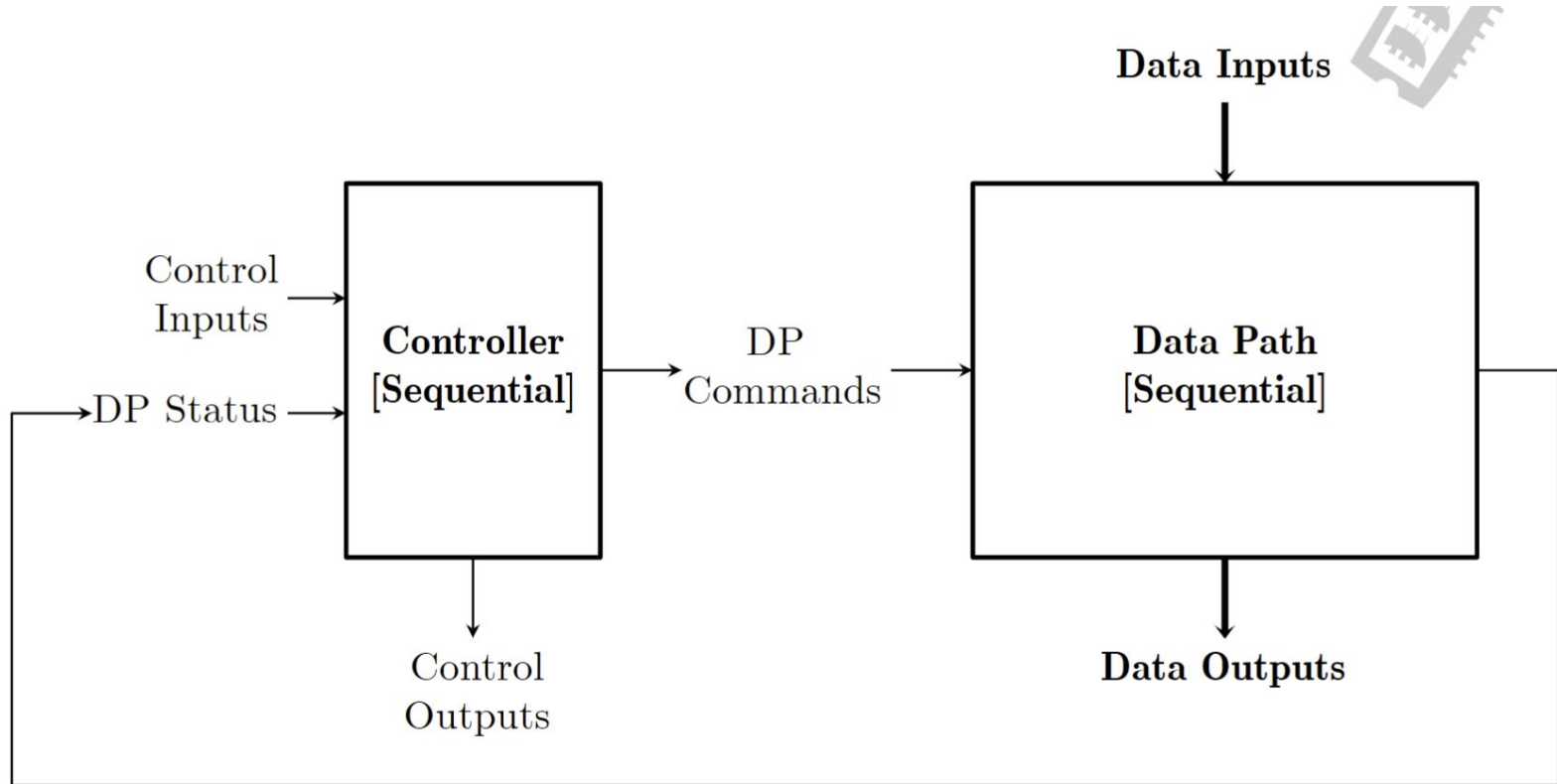

# Karnaugh Maps (K-Maps) (Logic Minimization)



# K-Maps Overview

- Minterm: AND of every variable as itself or its complement(used to form SOP)
- Maxterm: OR of every variable as itself or its complement (used to form POS)
- K-Maps: A 2D representation of a Truth Table that visualizes which minterms/maxterms we can combine to make simpler expressions

A	B	C	F
0	0	0	m <sub>0</sub>
0	0	1	m <sub>1</sub>
0	1	0	m <sub>2</sub>
0	1	1	m <sub>3</sub>
1	0	0	m <sub>4</sub>
1	0	1	m <sub>5</sub>
1	1	0	m <sub>6</sub>
1	1	1	m <sub>7</sub>






		AB			
		00	01	11	10
C	0	m <sub>0</sub>	m <sub>2</sub>	m <sub>6</sub>	m <sub>4</sub>
	1	m <sub>1</sub>	m <sub>3</sub>	m <sub>7</sub>	m <sub>5</sub>

A yellow star is placed above the m<sub>6</sub> cell in the K-map.

# K-Map Rules

   1. Only cover cells that have a 1  
(only include 'don't cares' if it helps to enlarge a group)
2. Only circle groups that are powers of 2
3. Only circle adjacent cells



# Important K-Map Terminology (Prime & Ess. Prime Impl.)

- **Implicant:** A rectangle that covers any high outputs
- **Prime implicant:** The largest single implicant that can fully cover a set of high outputs
- **Essential prime implicant:** A prime implicant that cannot be completely covered by any combination of other prime implicants



# K-Map Minimization Procedure

1. Identify all of your prime implicants
2. Determine which of the prime implicants are essential
  - a. Include those EPIS into your minimal SOP
3. Remove any “dominated” prime implicants
4. Find secondary Essential Prime Implicants (Repeat)



# Let's Try Out a Few

YZ \ WX				
	00	01	11	10
00	0	X	0	X
01	X	1	X	1
11	0	X	1	0
10	0	1	1	X

YZ \ WX				
	00	01	11	10
00	0	1	1	0
01	X	0	0	1
11	X	0	0	1
10	0	1	1	X

Have a cute pet? See it featured on the next exam review!



<https://forms.gle/ZS4YfU8RH4iJaa626>