

Forgiving Lock Part 1

Forgiving Lock Motivation


- You are an innovative lockmaker with a passion for craftsmanship, determined to create the next groundbreaking electronic lock!
- **ISSUE:** Sometimes people type in their password wrong!!



Me when I type my password wrong →



 - **MY SOLUTION:** Loosen the password “constraints”
 - **Make it easier for user to give correct password!!!**



Me when I type my password RIGHT!!! →




Forgiving Lock Design Problem


- Allowing users to provide a 4-bit continuous input stream password
 - 0000 **-(1)→** 000**1** **-(0)→** 001**0** **-(1)→** 010**1** **-(1)→** 101**1** **-(0)→** 011**0**
 - User must push button to enter new bit into the stream
- User will also have ability to flush password with a priority reset
 - XXXX **-(Reset)→** 0000
 - Priority Reset - If reset detected, ignore incoming additional user input
- **Example Loosened Password Constraint**
 - **Allow user to unlock if the current code has alternating numbers in at least 3 digits**
 - **Ex. 010x, 101x, x010, ...**

Forgiving Lock Design Diagram

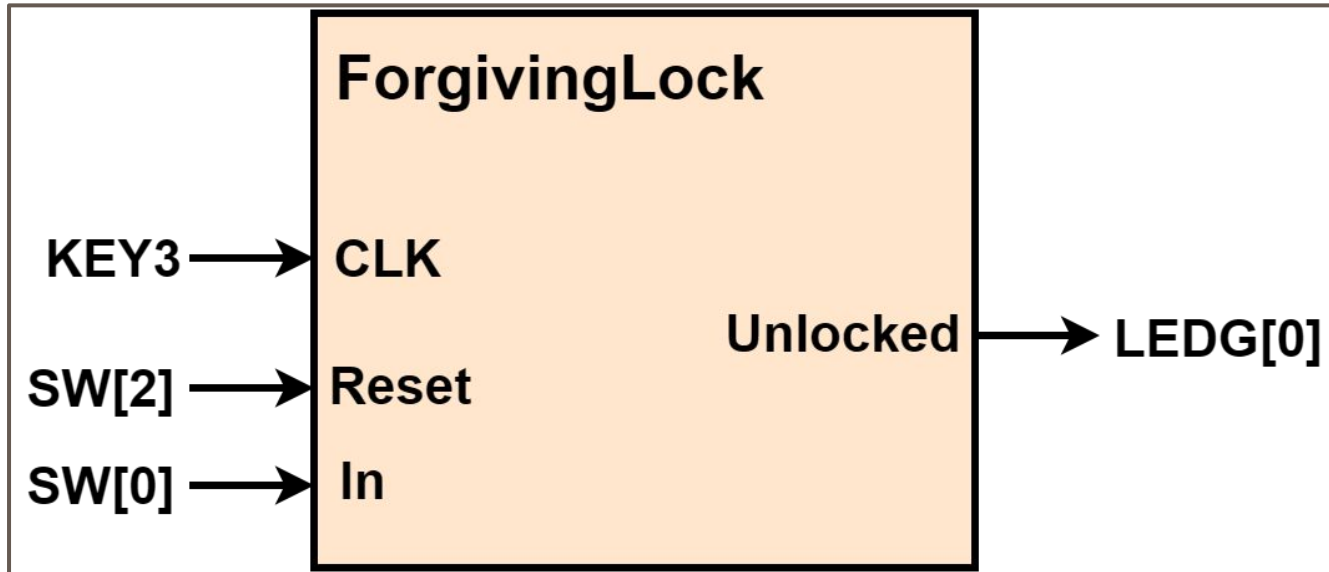- Will be fully synchronous with a negatively edge triggered active-low button
- Allows 2 input switches: One for Reset, another for Input
- Output: If code is unlocked, light up LEDG[0]




Some Questions

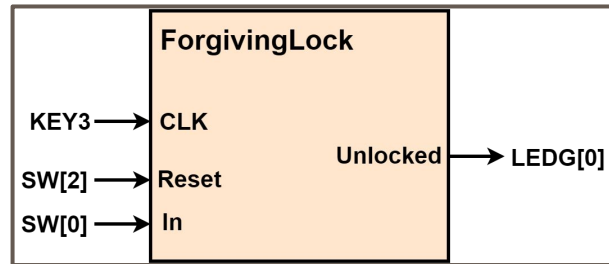

 
1. Is this a Moore/Mealy Machine?
2. How many internal states exist in this machine?
3. For synchronization, should we be using a latch or a FF? Why?
4. What does it mean for our machine to be synchronized?
 - a. If our reset was 'asynchronous', what changes?
 - b. Why might we choose one over the other?

Review: Sequential Circuit Components

- **Next state logic** (*combinational*) next state = $f(\text{current state}, \text{inputs})$
- **Memory** (*sequential*): stores state in terms of state variables
- **Output logic** (*combinational*):
 - **Moore Output**: output = $g(\text{current state})$



 - **Mealy Output**: output = $g(\text{current state}, \text{inputs})$



Construct Transition/Output Table

Code	Input (In)		Unlocked
	0	1	

Code⁺
(Next_Code)

Code	Input (In)		Unlocked
	0	1	

Code⁺
(Next_Code)

Construct Transition/Output Table

Code	Input (In)		Unlocked
	0	1	
0000			
0001			
0010			
0011			
0100			
0101			
0110			
0111			

Code⁺
(Next_Code)

Code	Input (In)		Unlocked
	0	1	
1000			
1001			
1010			
1011			
1100			
1101			
1110			
1111			

Code⁺
(Next_Code)

Construct Transition/Output Table

Code	Input (In)		Unlocked
	0	1	
0000	0000	0001	
0001			
0010			
0011			
0100			
0101			
0110			
0111			

Code⁺
(Next_Code)

Code	Input (In)		Unlocked
	0	1	
1000			
1001			
1010			
1011			
1100			
1101			
1110			
1111			

Code⁺
(Next_Code)

Construct Transition/Output Table

Code	Input (In)		Unlocked
	0	1	
0000	0000	0001	
0001	0010	0011	
0010			
0011			
0100			
0101			
0110			
0111			

Code⁺
(Next_Code)

Code	Input (In)		Unlocked
	0	1	
1000			
1001			
1010			
1011			
1100			
1101			
1110			
1111			

Code⁺
(Next_Code)

Construct Transition/Output Table

Code	Input (In)		Unlocked
	0	1	
0000	0000	0001	
0001	0010	0011	
0010	0100	0101	
0011			
0100			
0101			
0110			
0111			

Code⁺
(Next_Code)

Code	Input (In)		Unlocked
	0	1	
1000			
1001			
1010			
1011			
1100			
1101			
1110			
1111			

Code⁺
(Next_Code)

Construct Transition/Output Table

Code	Input (In)		Unlocked
	0	1	
0000	0000	0001	
0001	0010	0011	
0010	0100	0101	
0011	0110	0111	
0100			
0101			
0110			
0111			

Code⁺
(Next_Code)

Code	Input (In)		Unlocked
	0	1	
1000			
1001			
1010			
1011			
1100			
1101			
1110			
1111			

Code⁺
(Next_Code)

Construct Transition/Output Table

Code	Input (In)		Unlocked
	0	1	
0000	0000	0001	
0001	0010	0011	
0010	0100	0101	
0011	0110	0111	
0100	1000	1001	
0101	1010	1011	
0110	1100	1101	
0111	1110	1111	

Code⁺
(Next_Code)

Code	Input (In)		Unlocked
	0	1	
1000			
1001			
1010			
1011			
1100			
1101			
1110			
1111			

Code⁺
(Next_Code)

Construct Transition/Output Table

Code	Input (In)		Unlocked
	0	1	
0000	0000	0001	
0001	0010	0011	
0010	0100	0101	
0011	0110	0111	
0100	1000	1001	
0101	1010	1011	
0110	1100	1101	
0111	1110	1111	

Code⁺
(Next_Code)

Code	Input (In)		Unlocked
	0	1	
1000	0000	0001	
1001	0010	0011	
1010	0100	0101	
1011	0110	0111	
1100	1000	1001	
1101	1010	1011	
1110	1100	1101	
1111	1110	1111	

Code⁺
(Next_Code)

Construct Transition/Output Table

Code	Input (In)		Unlocked
	0	1	
0000	0000	0001	0
0001	0010	0011	0
0010	0100	0101	1
0011	0110	0111	0
0100	1000	1001	1
0101	1010	1011	1
0110	1100	1101	0
0111	1110	1111	0

Code⁺
(Next_Code)

Code	Input (In)		Unlocked
	0	1	
1000	0000	0001	0
1001	0010	0011	0
1010	0100	0101	1
1011	0110	0111	1
1100	1000	1001	0
1101	1010	1011	1
1110	1100	1101	0
1111	1110	1111	0

Code⁺
(Next_Code)

Construct Transition/Output Table

Code	Input (In)		Unlocked
	0	1	
0000	0000	0001	0
0001	0010	0011	0
0010	0100	0101	1
0011	0110	0111	0
0100	1000	1001	1
0101	1010	1011	1
0110	1100	1101	0
0111	1110	1111	0


Code⁺
(Next_Code)

Code	Input (In)		Unlocked
	0	1	
1000	0000	0001	0
1001	0010	0011	0
1010	0100	0101	1
1011	0110	0111	1
1100	1000	1001	0
1101	1010	1011	1
1110	1100	1101	0
1111	1110	1111	0

Code⁺
(Next_Code)

Creating Next State (Transition) Equations

 - Need to write equation(s) for Next_Code
 - **Hint: Focus on each bit at a time (How many bits are there?)**
 - **What is Next_Code dependent on?**
- Don't worry about writing code yet




Creating Next State (Transition) Equations

Next_Code[3] = Code[2]

Next_Code[2] = Code[1]


Next_Code[1] = Code[0]

Next_Code[0] = In

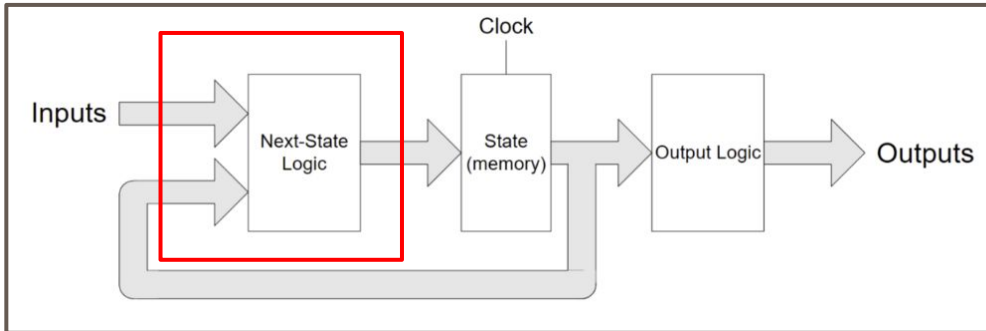

Creating Output Equations

 - Need to write an equation for Unlocked
 - **Use a K-Map to get a minimal SOP!!!!**
 - **Remember: We are dealing with a Moore machine**



Creating Output Equations (K-Map Approach)

{Code[3], Code[2]} / {Code[1], Code[0]}				

Creating Output Equations (K-Map Approach)

{Code[3], Code[2]} / {Code[1], Code[0]}	00	01	11	10
00				
01				
11				
10				

Creating Output Equations (K-Map Approach)

{Code[3], Code[2]} / {Code[1], Code[0]}	00	01	11	10
00	0			
01				
11				
10				

Creating Output Equations (K-Map Approach)

{Code[3], Code[2]} / {Code[1], Code[0]}	00	01	11	10
00	0	0		
01				
11				
10				

Creating Output Equations (K-Map Approach)

{Code[3], Code[2]} / {Code[1], Code[0]}	00	01	11	10
00	0	0	0	
01				
11				
10				

Creating Output Equations (K-Map Approach)

{Code[3], Code[2]} / {Code[1], Code[0]}	00	01	11	10
00	0	0	0	1
01				
11				
10				

Creating Output Equations (K-Map Approach)

{Code[3], Code[2]} / {Code[1], Code[0]}	00	01	11	10
00	0	0	0	1
01	1	1	0	0
11				
10				

Creating Output Equations (K-Map Approach)

{Code[3], Code[2]} / {Code[1], Code[0]}	00	01	11	10
00	0	0	0	1
01	1	1	0	0
11	0	1	0	0
10	0	0	1	1

Creating Output Equations (K-Map Approach)

{Code[3], Code[2]} / {Code[1], Code[0]}	00	01	11	10
00	0	0	0	1
01	1	1	0	0
11	0	1	0	0
10	0	0	1	1

Creating Output Equations (K-Map Approach)

$\{\text{Code}[3], \text{Code}[2]\} / \{\text{Code}[1], \text{Code}[0]\}$	00	01	11	10
00	0	0	0	1
01	1	1	0	0
11	0	1	0	0
10	0	0	1	1

1. Find all Prime Implicants!

Creating Output Equations (K-Map Approach)

$\{\text{Code}[3], \text{Code}[2]\} / \{\text{Code}[1], \text{Code}[0]\}$	00	01	11	10
00	0	0	0	1
01	1	1	0	0
11	0	1	0	0
10	0	0	1	1

1. Find all Prime Implicants!

Creating Output Equations (K-Map Approach)

$\{\text{Code}[3], \text{Code}[2]\} / \{\text{Code}[1], \text{Code}[0]\}$	00	01	11	10
00	0	0	0	1
01	1	1	0	0
11	0	1	0	0
10	0	0	1	1

1. Find all Prime Implicants!
2. Indicate which PI are Essential (EPI)

Creating Output Equations (K-Map Approach)

$\{\text{Code}[3], \text{Code}[2]\} / \{\text{Code}[1], \text{Code}[0]\}$	00	01	11	10
00	0	0	0	1
01	1	1	0	0
11	0	1	0	0
10	0	0	1	1

1. Find all Prime Implicants!
2. Indicate which PI are Essential (EPI)

Creating Output Equations (K-Map Approach)

$\{\text{Code}[3], \text{Code}[2]\} / \{\text{Code}[1], \text{Code}[0]\}$	00	01	11	10
00	0	0	0	1
01	1	1	0	0
11	0	1	0	0
10	0	0	1	1

1. Find all Prime Implicants!
2. Indicate which PI are Essential (EPI)
3. Remove all EPIs and remove any dominated PIs

Unlocked =

Creating Output Equations (K-Map Approach)

$\{\text{Code}[3], \text{Code}[2]\} / \{\text{Code}[1], \text{Code}[0]\}$	00	01	11	10
00				1
01	1	1		
11		1		
10			1	1

Unlocked =

1. Find all Prime Implicants!
2. Indicate which PI are Essential (EPI)
3. Remove all EPIs and remove any dominated PIs

Creating Output Equations (K-Map Approach)

$\{\text{Code}[3], \text{Code}[2]\} / \{\text{Code}[1], \text{Code}[0]\}$	00	01	11	10
00				1
01				
11		1		
10			1	1

1. Find all Prime Implicants!
2. Indicate which PI are Essential (EPI)
3. Remove all EPIs and remove any dominated PIs

Unlocked = ($\sim\text{Code}[3]$ & $\text{Code}[2]$ & $\text{Code}[1]$)

Creating Output Equations (K-Map Approach)

$\{\text{Code}[3], \text{Code}[2]\} / \{\text{Code}[1], \text{Code}[0]\}$	00	01	11	10
00				1
01				
11				
10			1	1

1. Find all Prime Implicants!
2. Indicate which PI are Essential (EPI)
3. Remove all EPIs and remove any dominated PIs

$$\text{Unlocked} = (\sim\text{Code}[3] \ \& \ \text{Code}[2] \ \& \ \sim\text{Code}[1]) \mid (\text{Code}[2] \ \& \ \sim\text{Code}[1] \ \& \ \text{Code}[0])$$

Creating Output Equations (K-Map Approach)

$\{\text{Code}[3], \text{Code}[2]\} / \{\text{Code}[1], \text{Code}[0]\}$	00	01	11	10
00				1
01				
11				
10				

1. Find all Prime Implicants!
2. Indicate which PI are Essential (EPI)
3. Remove all EPIs and remove any dominated PIs

$$\text{Unlocked} = (\sim\text{Code}[3] \& \text{Code}[2] \& \sim\text{Code}[1]) \mid (\text{Code}[2] \& \sim\text{Code}[1] \& \text{Code}[0]) \mid (\text{Code}[3] \& \sim\text{Code}[2] \& \text{Code}[1])$$

Creating Output Equations (K-Map Approach)

$\{\text{Code}[3], \text{Code}[2]\} / \{\text{Code}[1], \text{Code}[0]\}$	00	01	11	10
00				
01				
11				
10				

1. Find all Prime Implicants!
2. Indicate which PI are Essential (EPI)
3. Remove all EPIs and remove any dominated PIs

$$\text{Unlocked} = (\sim\text{Code}[3] \& \text{Code}[2] \& \sim\text{Code}[1]) \mid (\text{Code}[2] \& \sim\text{Code}[1] \& \text{Code}[0]) \mid (\text{Code}[3] \& \sim\text{Code}[2] \& \text{Code}[1]) \mid (\sim\text{Code}[2] \& \text{Code}[1] \& \sim\text{Code}[0])$$

Creating Output Equations (K-Map Approach)

**Unlocked = ($\sim\text{Code}[3] \& \text{Code}[2] \& \sim\text{Code}[1]$) |
($\text{Code}[2] \& \sim\text{Code}[1] \& \text{Code}[0]$) |
($\text{Code}[3] \& \sim\text{Code}[2] \& \text{Code}[1]$) |
($\sim\text{Code}[2] \& \text{Code}[1] \& \sim\text{Code}[0]$)**

1. Find all Prime Implicants!
2. Indicate which PI are Essential (EPI)
3. Remove all EPIs and remove any dominated PIs
4. DONE in 1 round!!

Starter Code Template (Code to Copy on Right)

```
module ForgivingLock(  
    // TODO: What are the inputs/outputs?  
);  
  
    // TODO: What registers/wires should we declare?  
  
    // TODO: Should we have any initialization?  
  
    // TODO: Next State Logic (Combinational or Sequential?)  
  
    // TODO: Memory Logic (Combinational or Sequential?)  
  
    // TODO: Output Logic (Combinational or Sequential?)  
  
endmodule
```

```
module ForgivingLock(  
    // TODO: What are the inputs/outputs?  
);  
  
    // TODO: What registers/wires should we declare?  
  
    // TODO: Should we have any initialization?  
  
    // TODO: Next State Logic (Combinational or Sequential?)  
  
    // TODO: Memory Logic (Combinational or Sequential?)  
  
    // TODO: Output Logic (Combinational or Sequential?)  
  
endmodule
```


Top-Level Module and Testbench Code

```
module ForgivingTopLevel(
    input [3:3] KEY,
    input [1:0] SW,
    output [0:0] LEDG
);

    ForgivingLock i(.CLK(KEY[3]), .Reset(SW[1]), .In(SW[0]), .Unlocked(LEDG[0]));

endmodule
```

[illegible]

```
module ForgivingLock(  
    // TODO: What are the inputs/outputs?  
);  
  
    // TODO: What registers/wires should we declare?  
  
    // TODO: Should we have any initialization?  
  
    // TODO: Next State Logic (Combinational or Sequential?)  
  
    // TODO: Memory Logic (Combinational or Sequential?)  
  
    // TODO: Output Logic (Combinational or Sequential?)  
  
endmodule
```




```
module ForgivingLock(  
    input CLK,  
    input Reset,  
    input In,  
    output Unlocked  
);  
  
    // TODO: What registers/wires should we declare?  
  
    // TODO: Should we have any initialization?  
  
    // TODO: Next State Logic (Combinational or Sequential?)  
  
    // TODO: Memory Logic (Combinational or Sequential?)  
  
    // TODO: Output Logic (Combinational or Sequential?)  
  
endmodule
```



```

module ForgivingLock(
  input CLK,
  input Reset,
  input In,
  output Unlocked
);
  // TODO: What registers/wires should we declare?
  // TODO: Should we have any initialization?
  // TODO: Next State Logic (Combinational or Sequential?)
  // TODO: Memory Logic (Combinational or Sequential?)
  // TODO: Output Logic (Combinational or Sequential?)
endmodule

```

 

```

module ForgivingLock(
    input CLK,
    input Reset,
    input In,
    output Unlocked
);

// Declaring all memory as register
/* NOTE: All variables modified in procedural blocks
   need to be reg as well */
reg [3:0] Code, Next_Code;

// TODO: Should we have any initialization?


// TODO: Next State Logic (Combinational or Sequential?)

// TODO: Memory Logic (Combinational or Sequential?)

// TODO: Output Logic (Combinational or Sequential?)

endmodule

```

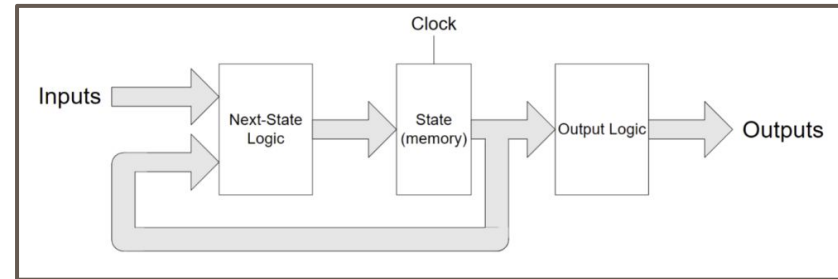

```

module ForgivingLock(
    input CLK,
    input Reset,
    input In,
    output Unlocked
);

// Declaring all memory as register
/* NOTE: All variables modified in procedural blocks
   need to be reg as well */
reg [3:0] Code, Next_Code;

// Not needed as we have a reset, but doesn't hurt
// REMEMBER: initial is synthesizable for FPGAs!
initial Code = 4'b0000;


// TODO: Next State Logic (Combinational or Sequential?)

// TODO: Memory Logic (Combinational or Sequential?)

// TODO: Output Logic (Combinational or Sequential?)

endmodule

```

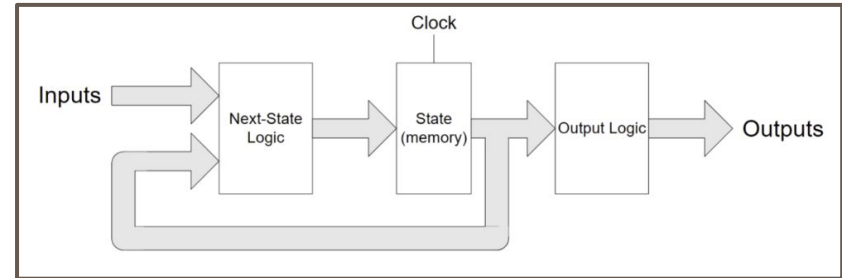

```

module ForgivingLock(
    input CLK,
    input Reset,
    input In,
    output Unlocked
);

// Declaring all memory as register
/* NOTE: All variables modified in procedural blocks
   need to be reg as well */
reg [3:0] Code, Next_Code;

// Not needed as we have a reset, but doesn't hurt
// REMEMBER: initial is synthesizable for FPGAs!
initial Code = 4'b0000;

// TODO: Next State Logic (Combinational or Sequential?)


// TODO: Memory Logic (Combinational or Sequential?)

// TODO: Output Logic (Combinational or Sequential?)

endmodule

```

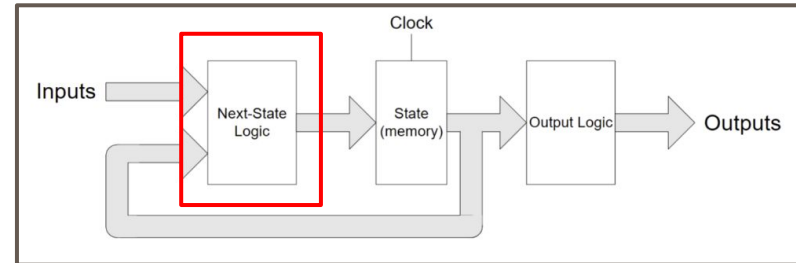Next_Code[3] = Code[2]
Next_Code[2] = Code[1]
Next_Code[1] = Code[0]
Next_Code[0] = In



```

module ForgivingLock(
    input CLK,
    input Reset,
    input In,
    output Unlocked
);

// Declaring all memory as register
/* NOTE: All variables modified in procedural blocks
   need to be reg as well */
reg [3:0] Code, Next_Code;

// Not needed as we have a reset, but doesn't hurt
// REMEMBER: initial is synthesizable for FPGAs!
initial Code = 4'b0000;

// Next State Logic (Combinational)
// always @* - Sensitivity list covers ALL inputs
// If any input changes --> Block gets executed
always @* begin
    Next_Code[3] = Code[2];
    Next_Code[2] = Code[1];
    Next_Code[1] = Code[0];
    Next_Code[0] = In;

    // Another way with concatenation
    // Next_Code = {Code[2:0], In};
end

```


```

// TODO: Memory Logic (Combinational or Sequential?)

// TODO: Output Logic (Combinational or Sequential?)

endmodule

```

 


```

module ForgivingLock(
  input CLK,
  input Reset,
  input In,
  output Unlocked
);

// Declaring all memory as register
/* NOTE: All variables modified in procedural blocks
   need to be reg as well */
reg [3:0] Code, Next_Code;

// Not needed as we have a reset, but doesn't hurt
// REMEMBER: initial is synthesizable for FPGAs!
initial Code = 4'b0000;

// Next State Logic (Combinational)
// always @* - Sensitivity list covers ALL inputs
// If any input changes --> Block gets executed
always @* begin
  Next_Code[3] = Code[2];
  Next_Code[2] = Code[1];
  Next_Code[1] = Code[0];
  Next_Code[0] = In;

  // Another way with concatenation
  // Next_Code = {Code[2:0], In};
end

```


```

// Memory Logic (Sequential)
// --> Sensitivity is clocked on CLK
// Code only changes on negedge of CLK
always @(negedge CLK) begin
  Code = (Reset) ? 4'b0000 : Next_Code;
end

// TODO: Output Logic (Combinational or Sequential?)

endmodule

```

 

Unlocked = (\sim Code[3] & Code[2] & \sim Code[1]) |
(Code[2] & \sim Code[1] & Code[0]) |
(Code[3] & \sim Code[2] & Code[1]) |
(\sim Code[2] & Code[1] & \sim Code[0])

```

module ForgivingLock(
    input CLK,
    input Reset,
    input In,
    output Unlocked
);

// Declaring all memory as register
/* NOTE: All variables modified in procedural blocks
   need to be reg as well */
reg [3:0] Code, Next_Code;

// Not needed as we have a reset, but doesn't hurt
// REMEMBER: initial is synthesizable for FPGAs!
initial Code = 4'b0000;

// Next State Logic (Combinational)
// always @* - Sensitivity list covers ALL inputs
// If any input changes --> Block gets executed
always @* begin
    Next_Code[3] = Code[2];
    Next_Code[2] = Code[1];
    Next_Code[1] = Code[0];
    Next_Code[0] = In;

    // Another way with concatenation
    // Next_Code = {Code[2:0], In};
end

```

```

// Memory Logic (Sequential)
// --> Sensitivity is clocked on CLK
// Code only changes on negedge of CLK
always @(negedge CLK) begin
    Code = (Reset) ? 4'b0000 : Next_Code;
end

// Output Logic (Combinational)
assign Unlocked = (~Code[3] & Code[2] & ~Code[1]) |
                  (Code[2] & ~Code[1] & Code[0]) |
                  (Code[3] & ~Code[2] & Code[1]) |
                  (~Code[2] & Code[1] & ~Code[0]);

endmodule

```

(Optional) Try to simply the Unlocked equation above using your theorems!

Try to further simply using XORs!

Final Code for Forgiving Lock

```
"timescale 1ns/1ns
```

```
module ForgivingTopLevel(
    input [3:0] KEY,
    input [1:0] SW,
    output [0:0] LEDG
);
```

```
    ForgivingLock (,CLK(KEY[3]),.Reset(SW[1]),.In(SW[0]),.Unlocked(LEDG[0]));
```

```
endmodule
```

```
module ForgivingTestBench;

    reg [3:0] KEY;
    reg [1:0] SW;
    wire [0:0] LEDG;

    ForgivingLock dut(,CLK(KEY[3]),.Reset(SW[1]),.In(SW[0]),.Unlocked(LEDG[0]));

    reg correct_LEDG;

    // Task for inserting 0
    task Resetting_Task;
    begin
        SW = 2'b10;
        #5;
        KEY[3] = 1'b0;
        correct_LEDG = 1'b0;
        #5;
        KEY[3] = 1'b1;
    end
endtask

    // Task for inserting 0
    task Inserting_0_Task;
    input correct_LEDG_val;
    begin
        SW = 2'b00;
        #5;
        KEY[3] = 1'b0;
        correct_LEDG = correct_LEDG_val;
        #5;
        KEY[3] = 1'b1;
    end
endtask

    // Task for inserting 1
    task Inserting_1_Task;
    input correct_LEDG_val;
    begin
        SW = 2'b01;
        #5;
        KEY[3] = 1'b0;
        correct_LEDG = correct_LEDG_val;
        #5;
        KEY[3] = 1'b1;
    end
endtask

    initial begin

        // Resetting
        KEY[3] = 1'b1;
        correct_LEDG = 1'b0;
        #5;
        Resetting_Task;

        // Inserting 0
        Inserting_0_Task(1'b0);

        // Cycling through all of the states
        Inserting_1_Task(1'b0); // 0001
        Inserting_0_Task(1'b1); // 0010
        Inserting_1_Task(1'b1); // 0101
        Inserting_0_Task(1'b1); // 1010
        Inserting_0_Task(1'b1); // 0100
        Inserting_1_Task(1'b0); // 1001
        Inserting_1_Task(1'b0); // 0011
        Inserting_0_Task(1'b0); // 0110
        Inserting_1_Task(1'b1); // 1011
        Inserting_1_Task(1'b1); // 1011
        Inserting_0_Task(1'b0); // 0110
        Inserting_0_Task(1'b0); // 1000
        Inserting_0_Task(1'b0); // 0001
        Inserting_1_Task(1'b0); // 0011
        Inserting_1_Task(1'b0); // 0111
        Inserting_1_Task(1'b1); // 1011
        Inserting_1_Task(1'b1); // 0111
        Inserting_1_Task(1'b0); // 1111

    end

endmodule
```

```
module ForgivingLock(
    input CLK,
    input Reset,
    input In,
    output Unlocked
);
```

```
// Declaring all memory as register
// NOTE: All variables modified in procedural blocks
// need to be reg as well */
reg [3:0] Code, Next_Code;
```

```
// Not needed as we have a reset, but doesn't hurt
// REMEMBER: initial is synthesizable for FPGAs!
initial Code = 4'b0000;
```

```
// Next State Logic (Combinational)
// always @* - Sensitivity list covers ALL inputs
// If any input changes --> Block gets executed
always @* begin
    Next_Code[3] = Code[2];
    Next_Code[2] = Code[1];
    Next_Code[1] = Code[0];
    Next_Code[0] = In;
```

```
// Another way with concatenation
// Next_Code = {Code[2:0], In};
end
```

```
// Memory Logic (Sequential)
// --> Sensitivity is clocked on CLK
// Code only changes on negedge of CLK
always @(negedge CLK) begin
    Code = (Reset) ? 4'b0000 : Next_Code;
end
```

```
// Output Logic (Combinational)
assign Unlocked = (~Code[3] & Code[2] & ~Code[1]) |
    (Code[2] & ~Code[1] & Code[0]) |
    (Code[3] & ~Code[2] & Code[1]) |
    (~Code[2] & Code[1] & ~Code[0]);
```

```
// Another way to write after theorem simplifications
// assign Unlocked = (Code[2] & ~Code[1] & (~Code[3] | Code[0])) |
//    (~Code[2] & Code[1] & (Code[3] | ~Code[0]));
```

```
// Going beyond with conceptual and using XOR statements
// assign Unlocked = ((Code[3] ^ Code[2]) & (Code[2] ^ Code[1])) |
//    ((Code[2] ^ Code[1]) & (Code[1] ^ Code[0]));
```

```
endmodule
```